

EE2029 – Introduction to Electrical Energy Systems
Tutorial # 1 Transformers


- Find the turns ratio of a single-phase transformer that transforms the primary voltage 15,000 V of a power line to the secondary voltage 240 V supplied to a house.

(Answer: 62.5)

- The output stage of an audio system has an output resistance of 2 k Ω . An output transformer provides resistance matching with a 6 Ω speaker. If this transformer has 400 primary turns, how many secondary turns does it have?


(Answer: 22 turns)

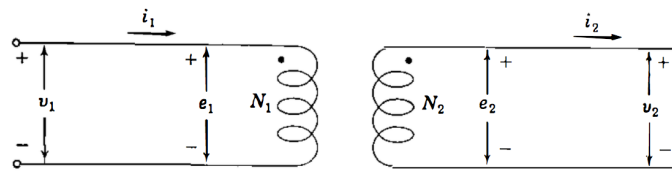- Referring to the equivalent circuit of a transformer shown below, $N_1 = 2000$, and $N_2 = 500$. Suppose $V_1 = 1200\angle 0^\circ$ V and $I_1 = 5\angle -30^\circ$ A at the primary side with an impedance Z_2 connected across the secondary side. Compute V_2 , I_2 , Z_2 , and Z'_2 . Note that Z'_2 refers to the impedance Z_2 reflected to the primary side of the transformer.



(Answer: $V_2 = 300\angle 0^\circ$ V, $I_2 = 20\angle -30^\circ$ A, $Z_2 = 15\angle 30^\circ \Omega$, $Z'_2 = 240\angle 30^\circ \Omega$)

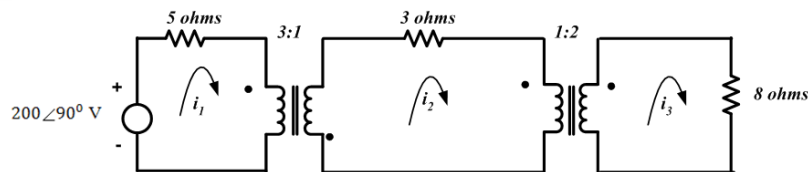- Find i_1 , i_2 and i_3 for the circuit shown below. The transformers are ideal.



(Answer: $i_1 = 4\angle 90^\circ$, $i_2 = 12\angle 270^\circ$, $i_3 = 6\angle 270^\circ$)


- Three transformers, each rated at 25 MVA, 66/3.81 kV, have a Wye-Delta connection and is connected to a balanced load of three 0.6 Ω Wye-connected resistors. Choose a base of 75 MVA, 66 kV for the high-voltage side of the transformer, and specify the base for the low-voltage side. Determine the per unit resistance of the load on the base for the low-voltage side. Then, determine the load resistance R_L in ohms referred to the high-voltage side and per unit value of this resistance on the chosen base.

(Answer: $R_{L,LV} = 3.10$ p. u., $R_{L,HV} = 3.10$ p. u.)

6. A Three-phase transformer is rated 400 MVA, and 220/22 (Wye-Delta) kV. The Wye equivalent short-circuit impedance measured on the low-voltage side of the transformer is 0.121Ω . Determine the per unit reactance of the transformer and the per unit value to represent this transformer in a system whose base values on the high-voltage side is 100 MVA, 230 kV.

(Answer: 0.01 p.u., 0.0228 p.u.)

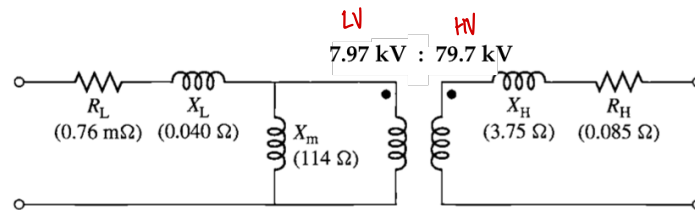7. The equivalent circuit for a 100 MVA, 7.97/79.7 kV transformer is shown below. The parameters of the transformers are: $X_L = 0.040 \Omega$, $X_H = 3.75 \Omega$, $X_M = 114 \Omega$, $R_L = 0.76 m\Omega$, and $R_H = 0.085 \Omega$. Note the magnetising inductance is referred to the low-voltage side of the equivalent circuit. Convert the equivalent circuit parameters to per unit using the transformer rating as the base.



(Answer: $X_L = 0.0630$ p.u., $X_H = 0.0591$ p.u., $X_m = 180$ p.u., $R_L = 0.0012$ p.u., $R_H = 0.0013$ p.u.)

8. A three-phase load is supplied from a 2400/460 V, 250 kVA transformer whose equivalent series impedance is $0.026 + j0.12$ per unit on its own base. The load voltage is observed to be 438 V line-to-line, and is drawing 95 kW at unity power factor. Calculate the voltage at the high-voltage side of the transformer. Perform the calculations on a 460 V at 100 kVA base.

(Answer: $V_H = 2313$ V, line-to-line)

1.

$$a = \frac{N_1}{N_2} = \frac{I_2}{I_1} = \frac{V_1}{V_2}$$

$$= \frac{15000}{240} = 62.5 //$$

2.

$$Z_1 = a^2 Z_2 = \left(\frac{N_1}{N_2}\right)^2 Z_2$$

$$\Rightarrow N_2 = \sqrt{\frac{N_1^2 \cdot Z_2}{Z_1}} = \sqrt{\frac{400^2 (6)}{2 \times 10^3}}$$

$$= 21.9 \approx 22 \text{ turns} //$$

3.

$$a = \frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{I_2}{I_1} = \frac{2000}{500} = 4$$

$$\Rightarrow V_2 = \frac{V_1}{a} = \frac{1200 \angle 0^\circ}{4} = 300 \angle 0^\circ \text{ V} //$$

$$\Rightarrow I_2 = a \cdot I_1 = 4(5 \angle -30^\circ) = 20 \angle -30^\circ \text{ A} //$$


$$Z_2 = \frac{V_2}{I_2} = \frac{300 \angle 0^\circ}{20 \angle -30^\circ}$$

$$= 15 \angle 30^\circ \Omega //$$

$$Z_2' = a^2 Z_2$$

$$= 4^2 (15 \angle 30^\circ) = 240 \angle 30^\circ \Omega //$$

4.

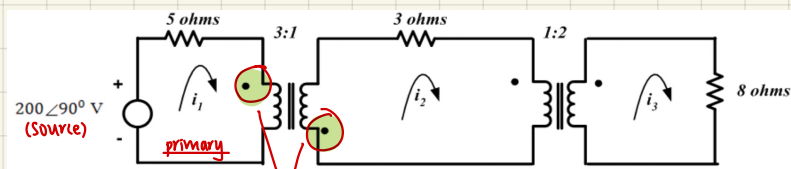

change in phase!

$$R_{\text{right}}' = a_{\text{right}}^2 R_{\text{right}} = \left(\frac{1}{2}\right)^2 (8) = 2 \Omega \quad (\text{right referred to mid})$$

$$R_{\text{mid}} + R_{\text{right}}' = 3 + 2 = 5 \Omega$$

$$R_{\text{mid}}' = a_{\text{left}}^2 R_{\text{mid}} = 3^2 (5) = 45 \Omega \quad (\text{mid referred to right})$$

$$R_E = R_{\text{left}} + R_{\text{mid}}' = 5 + 45 = 50 \Omega$$

$$i_1 = \frac{V_s}{R_E} = \frac{200 \angle 90^\circ}{50}$$

$$= 4 \angle 90^\circ \text{ A} //$$

$$a_{\text{left}} = \frac{N_1}{N_2} = \frac{i_1}{i_2} = 3$$

$$\Rightarrow |i_2| = 3(4) = 12 \text{ A}$$

$$\therefore i_2 = 12 \angle (90^\circ + 180^\circ) = 12 \angle 270^\circ //$$

opposite phase!

$$a_{\text{right}} = \frac{N_2}{N_3} = \frac{i_2}{i_3} = 0.5$$

$$\Rightarrow |i_3| = 0.5(12) = 6 \text{ A}$$

$$\therefore i_3 = 6 \angle 270^\circ \text{ A} //$$

5.

Transformer Rating: 25MVA, 66Y/3.81Δ kV

HV Base: 75MVA, 66kV (Y) (primary: HV)

LV Base: 75MVA, 3.81 kV (Δ)

Same!

$$Z_{LV, base} = \frac{V_{base, LV}^2}{S_{base}} = \frac{(3.81 \times 10^3)^2}{75 \times 10^6} = 0.1935 \Omega$$

$$R_{LV, pu} = \frac{R_{LV, actual}}{Z_{LV, base}} = \frac{0.6}{0.1935} = 3.10 \text{ p.u.}$$

$$R_{actual, LV}' = a^2 R_{actual, LV} \text{ (referred to primary)}$$

$$= \left(\frac{V_1}{V_2}\right)^2 R_{actual, LV}$$

$$= \left(\frac{66}{3.81}\right)^2 (0.6) = 180.05 \Omega$$

$$Z_{HV, base} = \frac{V_{base, HV}^2}{S_{base}} = \frac{(66 \times 10^3)^2}{75 \times 10^6} = 58.08 \Omega$$

$$\therefore R_{pu, HV} = R_{pu, LV}' = \frac{R_{actual, HV}}{Z_{HV, base}} = \frac{180.05}{58.08} = 3.10 \text{ p.u.}$$

6.

Transformer Rating: 400MVA, 220Y/22Δ kV

HV Base: 400MVA, 220kV (Y) (primary)

LV Base: 400MVA, 22kV (Δ)

$$Z_{actual, LV} = 0.121 \Omega$$

$$Z_{LV, base} = \frac{V_{base, LV}^2}{S_{base}} = \frac{(22 \times 10^3)^2}{400 \times 10^6} = 1.21 \Omega$$

$$X_{LV, pu} = \frac{Z_{LV, actual}}{Z_{LV, base}} = \frac{0.121}{1.21} = 0.10 \text{ p.u.}$$

Old HV Base: 400MVA, 220kV

New HV Base: 100MVA, 230kV

$$Z_{HV, base, old} = \frac{V_{base, HV, old}^2}{S_{base, old}} = \frac{(220 \times 10^3)^2}{400 \times 10^6} = 121 \Omega$$

$$Z_{HV, base, new} = \frac{V_{base, HV, new}^2}{S_{base, new}} = \frac{(230 \times 10^3)^2}{100 \times 10^6} = 529 \Omega$$

$$X_{pu, new} = X_{pu, old} \left[\frac{Z_{base, old, HV}}{Z_{base, new, HV}} \right] \text{ only works for } X \& Z!$$

$$= 0.10 \left[\frac{121}{529} \right] = 0.0229 \text{ p.u.}$$

7.

Transformer Rating: 100 MVA, 7.97/79.7 kV

HV Base: 100 MVA, 79.7 kV

LV Base: 100 MVA, 7.97 kV (primary)

At the LV-side:

$$Z_{\text{base, LV}} = \frac{V_{\text{LV, base}}^2}{|S|_{\text{base}}} = \frac{(7.97 \times 10^3)^2}{100 \times 10^6}$$

$$= 0.635 \Omega$$

$$X_{\text{L, pu}} = \frac{X_{\text{L, actual}}}{Z_{\text{LV, base}}} = \frac{0.040}{0.635}$$

$$= 0.0630 \text{ p.u.} //$$

$$R_{\text{L, pu}} = \frac{R_{\text{L, actual}}}{Z_{\text{LV, base}}} = \frac{0.76 \times 10^{-3}}{0.635}$$

$$= 0.00120 \text{ p.u.} //$$

$$X_{\text{m, pu}} = \frac{X_{\text{m, actual}}}{Z_{\text{LV, base}}} = \frac{114}{0.635}$$

$$= 179.53 \text{ p.u.} //$$

At the HV-side:

$$Z_{\text{base, HV}} = \frac{V_{\text{HV, base}}^2}{|S|_{\text{base}}} = \frac{(79.7 \times 10^3)^2}{100 \times 10^6}$$

$$= 63.5 \Omega$$

$$X_{\text{H, pu}} = \frac{X_{\text{H, actual}}}{Z_{\text{HV, base}}} = \frac{3.75}{63.5}$$

$$= 0.0591 \text{ p.u.} //$$

$$R_{\text{H, pu}} = \frac{R_{\text{H, actual}}}{Z_{\text{HV, base}}} = \frac{0.085}{63.5}$$

$$= 0.0134 \text{ p.u.} //$$

8.

$$Z_{\text{pu, old}} = 0.026 + j0.12 \text{ p.u.}$$

$$V_{\text{L, actual}} = 438 \text{ V} \rightarrow \text{actual values remain constant regardless of base!!}$$

$$P_{\text{L, actual}} = 95 \text{ kW}$$

Old LV Base: 250 kVA, 460 V

New LV Base: 100 kVA, 460 V

$$Z_{\text{LV, base, old}} = \frac{V_{\text{LV, base, old}}^2}{|S|_{\text{base, old}}} = \frac{460^2}{250 \times 10^3}$$

$$= 0.846 \Omega$$

$$Z_{\text{LV, base, new}} = \frac{V_{\text{LV, base, new}}^2}{|S|_{\text{base, new}}} = \frac{460^2}{100 \times 10^3}$$

$$= 2.116 \Omega$$

$$V_{\text{L, HV, pu, new}} = V_{\text{L, LV, pu, new}} + V_{\text{losses, pu, new}}$$

$$= V_{\text{L, LV, pu, new}} + I_{\text{L, pu, new}} \cdot Z_{\text{pu, new}} \quad \text{--- (1)}$$

$$V_{\text{L, pu, new}} = \frac{V_{\text{L, actual}}}{V_{\text{base, LV, new}}} = \frac{438}{460} = 0.9522 \text{ p.u.} \quad \text{--- (2)}$$

$$P_{\text{L, pu, new}} = \frac{P_{\text{L, actual}}}{|S|_{\text{base, new}}} = \frac{95 \times 10^3}{100 \times 10^3} = 0.95 \text{ p.u.} \quad \text{--- (3)}$$

$$I_{L, pu, new} = \frac{P_{L, pu, new}}{V_{L, pu, new}} = \frac{0.95}{0.9522} = 0.9977 \text{ p.u.} \quad (4)$$

$$Z_{pu, new} = Z_{pu, old} \left(\frac{Z_{base, LV, old}}{Z_{base, LV, new}} \right) = (0.026 + j0.12) \left[\frac{0.846}{2.116} \right]$$

only works for X & Z!

$$= 0.0104 + j0.048 \text{ p.u.} \quad (5)$$

Sub. into (1):

$$\begin{aligned} V_{L, HV, pu, new} &= V_{L, LV, pu, new} + I_{L, pu, new} \cdot Z_{pu, new} \\ &= 0.9522 + 0.9977 (0.0104 + j0.048) \\ &= 0.9626 + j0.0479 \text{ p.u.} \end{aligned}$$

$$\begin{aligned} V_{L, HV, actual, new} &= V_{L, HV, pu, new} \cdot V_{L, HV, base, new} \\ &= (0.9626 + j0.0479) (2400) \\ &= 2313 \angle 2.85^\circ \text{ V} \end{aligned}$$