

**EE2029 – Introduction to Electrical Energy Systems**  
**(Solution for Tutorial #2 on AC Power)**

**Solution Q.1**

$$Z_R = 25 \, \Omega$$

$$Z_C = -j \frac{1}{377 \times 100 \times 10^{-6}} = -j26.52 \, \Omega$$

$$Z_{Load} = \left( \frac{1}{25} + \frac{1}{-j26.52} \right)^{-1} = 18.19 \angle -43.31^\circ$$

$$\text{Total impedance seen by the source } Z_{total} = 1 + 18.19 \angle -43.31^\circ = 18.93 \angle -41.23^\circ \, \Omega$$

$$\text{Current drawn from the source } I = \frac{230 \angle 0^\circ}{18.93 \angle -41.23^\circ} = 12.15 \angle 41.23^\circ \, A$$

$$\text{Load voltage } V_{load} = V_s - I \times Z_{line} = 230 \angle 0^\circ - 12.15 \angle 41.23^\circ \times 1 = 221 \angle -2.075^\circ \, V$$

$$\text{Complex power delivered to the load } S_{load} = V_{load} I^* = 221 \angle -2.075^\circ \times 12.15 \angle -41.23^\circ = 2685.15 \angle -43.31^\circ \, VA$$

$$\text{Apparent power delivered to load } |S_{load}| = 2685.15 \, VA$$

$$\text{Power factor of the load} = \cos(-43.31^\circ) = 0.728 \text{ leading}$$

$$\text{Apparent power supplied by the source} = 230 \times 12.15 = 2794.5 \, VA$$

### Solution Q.2

$$\text{Current drawn by the load } |I_{old}| = \frac{P}{|V| \times (\text{Power factor})} = \frac{25000}{500 \times 0.5} = 100 \text{ A}$$

$$\cos \theta = 0.5 \rightarrow \theta = \cos^{-1}(0.5) = 60^\circ$$

$$\text{Current phasor } I = 100 \angle -60^\circ \text{ A}$$

$$\text{Complex power of the load } S_{old} = VI^* = 500 \times 100 \angle 60^\circ = 50000 \angle 60^\circ \text{ VA}$$

$$Q_{old} = 50000 \sin(60^\circ) = 43301 \text{ VAr}$$

After connecting the capacitor in parallel, new power factor = 0.95 lagging

$$\text{Current drawn from source } |I_{new}| = \frac{P}{|V| \times (\text{Power factor})} = \frac{25000}{500 \times 0.95} = 52.63 \text{ A}$$

$$\cos \theta' = 0.95 \rightarrow \theta' = \cos^{-1}(0.95) = 18.19^\circ$$

$$\text{Complex power drawn from the source } S_{new} = VI_{new}^* = 500 \times 52.63 \angle 18.19^\circ = 24999.95 + j8214.73 \text{ VA}$$


$$Q_{new} = 8214.73 \text{ VAr}$$

$$\text{Reactive power supplied by the capacitor } Q_C = 8214.73 - 43301 = -35086.27 \text{ VAr}$$

$$\text{The required capacitor value } C = \frac{Q_C}{\omega |V|^2} = \frac{35086.27}{2\pi \times 50 \times 500^2} = 446.73 \mu\text{F}$$

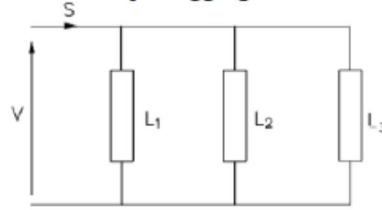**Solution Q3:**

L1: 5 kW at 0.8 p.f. lagging, L2: 10 kW at 0.6 p.f. lagging and L3: 15 kW at 0.8 p.f. leading



The complex power consumption of the loads are computed as follows:

$$P_1 = |S_1| \times 0.8$$

$$|S_1| = 6250 \text{ VA}$$

$$S_1 = 6250 \angle 36.87^\circ = 5000 + j3750$$

$$P_2 = |S_2| \times 0.6$$

$$|S_2| = 16666.67 \text{ VA}$$

$$S_2 = 16666.67 \angle 53.13^\circ = 10000 + j13333.33$$

$$P_3 = |S_3| \times 0.8$$

$$|S_3| = 18750 \text{ VA}$$

$$S_3 = 18750 \angle -36.87^\circ = 15000 - j11250$$

Hence, overall power factor as seen by the source can be calculated as:

$$S = S_1 + S_2 + S_3$$

$$= 30000 + j5833.33$$

$$= 30561.87 \angle 11^\circ \text{ VA}$$

$$\text{p.f.} = \cos 11^\circ = 0.982 \text{ lagging}$$

**Solution Q4:**

As the power delivered is 10kW at 0.5 p.f. lagging,

$$|I| = \frac{P}{V \cos \phi} = \frac{10000}{200 \times 0.5} = 100 \text{ A}$$

$$I = 100 \angle 60^\circ = 50 - j86.6 \text{ A}$$

When a capacitor of  $1000 \mu F$  is connected across the supply, the capacitor current is

$$I_C = j\omega CV = j314 \times 1000 \times 10^{-6} \times 200 = j62.8 \text{ A}$$

So the total current drawn from the supply is

$$I_T = I + I_C = 50 - j23.8 = 55.38 \angle -25.45^\circ$$

The power factor as seen by the source is

$$\text{p.f.} = \cos ( - 25.45^\circ ) = 0.902 \text{ lagging}$$

**Solution Q5:**

Current drawn from the substation is

$$|I_1| = \frac{P}{|V| \cos \theta} = \frac{1500 \times 10^3}{500 \times 0.6} = 5000 \text{ A}$$

If the power factor could be improved to unity, then current drawn would be

$$|I_2| = \frac{P}{|V| \cos \theta} = \frac{1500 \times 10^3}{500 \times 1.0} = 3000 \text{ A}$$

The transmission line losses in both the cases are

$$P_{loss1} = R |I_1|^2 = 0.005 \times 5000^2 = 125 \text{ kW}$$

$$P_{loss2} = R |I_2|^2 = 0.005 \times 3000^2 = 45 \text{ kW}$$

So, cost of energy wasted will be high in the first case.

This example illustrates that for the same real power demand, if the power factor of the load decreases, then  $|I|$  increases, resulting in heavy transmission line losses.

A poor power factor results in higher current and hence higher power loss.