

Transformer Tutorial

1. Primary side : 15000 V
Secondary side : 240 V

$$\frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{15000}{240} = \underline{62.5}$$

2. $\frac{R_1}{R_2} = \left(\frac{N_1}{N_2}\right)^2 \Rightarrow \left(\frac{400}{N_2}\right)^2 = \frac{2000}{6}$
 $N_2 = 22 \text{ turns.}$

3. $V_2 = \frac{N_2}{N_1} V_1 = \frac{500}{2000} \times 1200 \angle 0^\circ$
 $V_2 = 300 \angle 0^\circ \text{ V}$

$$I_2 = \frac{N_1}{N_2} I_1 = \frac{2000}{500} \times 5 \angle -30^\circ$$

 $I_2 = 20 \angle -30^\circ \text{ A}$

$$Z_2 = \frac{V_2}{I_2} = \frac{300 \angle 0^\circ}{20 \angle -30^\circ}$$

 $Z_2 = 15 \angle 30^\circ \Omega$

$$Z_2' = \left(\frac{N_1}{N_2}\right)^2 Z_2 = \left(\frac{2000}{500}\right)^2 \times 15 \angle 30^\circ$$

 $Z_2' = 240 \angle 30^\circ \Omega$

4. Reflect all impedance to the source side. In this case, there will be two conversion stages due to two transformers.

$$R'_{\text{mid}} = \left(\frac{N_2}{N_3}\right)^2 R_{\text{right}} = \left(\frac{1}{2}\right)^2 \times 8 = 2 \Omega$$

$$R_{\text{mid}} = R + R'_{\text{mid}} = 3 + 2 = 5 \Omega$$

$$R'_{\text{left}} = \left(\frac{N_1}{N_2}\right)^2 R_{\text{mid}} = \left(\frac{3}{1}\right)^2 \times 5 = 45 \Omega$$


$$\Rightarrow R_{\text{tot}} = 45 + 5 = 50 \Omega$$

$$I = \frac{V_1}{R_{\text{tot}}} = \frac{200 \angle 90^\circ}{50} = \underline{4 \angle 90^\circ \text{ A}}$$

$$I_2 = \left(\frac{N_2}{N_1}\right) I_1 = \frac{3}{1} \times 4 \angle (90^\circ + 180^\circ) = \underline{12 \angle 270^\circ \text{ A}}$$

$$I_3 = \left(\frac{N_2}{N_3}\right) I_2 = \frac{1}{2} \times 12 \angle 270^\circ = \underline{6 \angle 270^\circ \text{ A}}$$

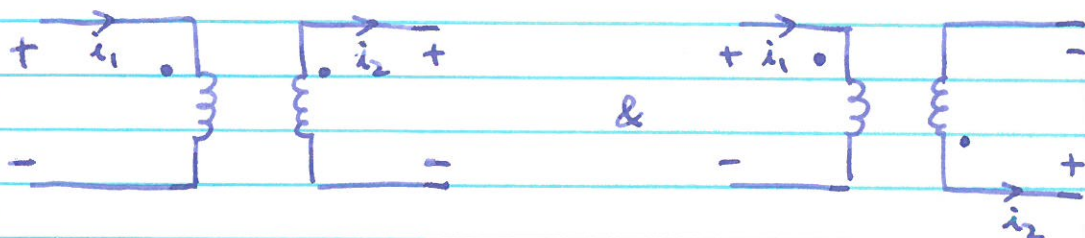Note. The dot on the transformer coil indicates the direction of current flowing out of the coil.



Flip of coil current due to load connection results to 180° phase shift.

5. 38.1 kV (Y) - 3.81 kV (Δ) Transformer.

38.1 kV is phase voltage \Rightarrow line (rated) voltage is $\sqrt{3} \times 38.1 \text{ kV} = \underline{66 \text{ kV}}$.

\Rightarrow 38.1 kV is the base of HV side when line-neutral.

$$Z_{\text{base}}^{\text{LV}} = \frac{(V_{\text{LV,B}})^2}{\text{MVA}_B} = \frac{(3.81 \text{ kV})^2}{75 \text{ MVA}} = 0.1935 \Omega$$

$$R_L = \frac{0.6}{0.1935} = \underline{3.10 \text{ p.u.}}$$

$$Z_{\text{base}}^{\text{HV}} = \frac{(V_{\text{HV,B}})^2}{\text{MVA}_B} = \frac{(66 \text{ kV})^2}{75 \text{ MVA}} = 58.1 \Omega$$

$$R_L = 0.6 \cdot \left(\frac{66}{3.81} \right)^2 = \underline{180 \Omega}$$

$$\Rightarrow R_L = \frac{180}{58.1} = \underline{3.10 \text{ p.u.}}$$

Ans: R_L is same in per unit when reflected to HV and LV.

6. $R_{e,LV} = 0.121 \Omega$.

Using 400 MVA as its base:

$$R_e = 0.121 / \frac{(22 \text{ kV})^2}{400 \text{ MVA}} = \underline{0.10 \text{ p.u.}}$$

$$R_e' = 0.1 \left(\frac{220}{230} \right)^2 \times \frac{100}{400} = \underline{0.0228 \text{ p.u.}}$$

\Rightarrow change from one base to another base.

7. LV side: $V_{AB} = 100 \text{ MVA}$, $V_B = 7.97 \text{ kV}$
 $\Rightarrow R_B^{LV} = X_B^{LV} = \frac{(V_B)^2}{V_{AB}} = \frac{(7.97 \text{ kV})^2}{100 \text{ MVA}} = 0.635 \Omega$

HV side: $V_{AB} = 100 \text{ MVA}$, $V_B = 79.7 \text{ kV}$
 $\Rightarrow R_B^{HV} = X_B^{HV} = \frac{(79.7 \text{ kV})^2}{100 \text{ MVA}} = 63.5 \Omega$


$$\Rightarrow X_L = \frac{0.040 \Omega}{0.635 \Omega} = \underline{0.0630 \text{ p.u.}}$$

$$X_H = \frac{3.75 \Omega}{63.5 \Omega} = \underline{0.0591 \text{ p.u.}}$$

$$X_m = \frac{114 \Omega}{0.635 \Omega} = \underline{180 \text{ p.u.}}$$

$$R_L = \frac{0.76 \text{ m}\Omega}{0.635 \Omega} = \underline{0.0012 \text{ p.u.}}$$
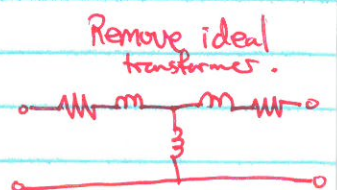
$$R_H = \frac{0.085 \Omega}{63.5 \Omega} = \underline{0.0013 \text{ p.u.}}$$



Note. Normalize turn ratio: $\left(\frac{7.97 \text{ kV}}{7.97 \text{ kV}} \right) : \left(\frac{79.7 \text{ kV}}{79.7 \text{ kV}} \right) = 1 : 1$

8. LV side: $Z_B^L = \frac{(460V)^2}{250 \text{ kVA}} = 0.846 \Omega$.

But the common base is 100 kVA at 460 V

$$Z_{B,100\text{kVA}}^L = \frac{460^2}{100 \times 10^3} = 2.12 \Omega$$

* Need to convert to transformer base then to common base.

$$\Rightarrow Z_{\text{transformer}} = (0.026 + j0.12) \cdot \left(\frac{0.846}{2.12} \right) \\ = 0.0106 + j0.0489 \text{ p.u. (at 100 kV base).}$$

$$V_{\text{load}} = \frac{438 \text{ V}}{460 \text{ V}} = 0.952 \angle 0^\circ \text{ p.u.}$$

$$I_{\text{load}} = \frac{P}{V} = \frac{95 \text{ kVA} / 100 \text{ kVA}}{0.952 \angle 0^\circ} = 0.998 \angle 0^\circ \text{ p.u.}$$

HV side:

$$V_{\text{HV}} = V_{\text{load}} + I_{\text{load}} Z_{\text{transformer}}$$

$$= 0.952 \angle 0^\circ + 0.998 \angle 0^\circ \times (0.0106 + j0.0489)$$

$$V_{\text{HV}} = 0.963 + j0.0488$$

$$= 0.964 \angle 29.0^\circ \text{ p.u.}$$

$$\Rightarrow V_{\text{HV}}^{\text{act}} = 0.964 \angle 29.0^\circ \times 2400 = \underline{2313 \text{ V}} \text{ (rated) l-l.}$$

