

EE2029 INTRODUCTION TO ELECTRICAL ENERGY SYSTEMS
(Solution for Tutorial #1 Transmission Lines)

4.

Using the short length model, $l = 16 \text{ km}$, $Z = 16 \times (0.125 + j0.4375) = 2 + j7 \Omega$. Per phase equivalent model is shown in Fig. 1.

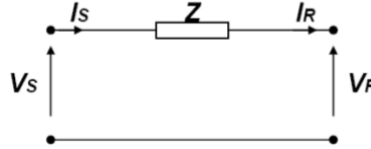


Fig.1

The voltage and current at sending and receiving end can be found from the following.

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} 1 & 2 + j7 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

The receiving end voltage is given as 64 kV line-to-line. Let the voltage at the load be reference angle, we can find the voltage per phase as follows.

$$V_R = \frac{64 \times 10^3}{\sqrt{3}} \angle 0^\circ = 36.95 \angle 0^\circ \text{ kV}.$$

The receiving end current, I_R , can be found from the complex power consumed by the load at the receiving end, denoted by $S_{3\phi,R}$, of 70 MVA, 0.8 lagging.

$$|I_R| = \frac{|S_{1\phi,R}|}{|V_R|} = \frac{|S_{3\phi,R}|}{3|V_R|} = \frac{70 \times 10^6}{3 \times 36.95 \times 10^3} = 631.48 \text{ A}$$

The angle of receiving end current is found from power factor. The angle is negative because power factor is lagging.

$$\angle I_R = -\cos^{-1}(0.8) = -36.87^\circ$$

Sending end voltage is found below.

$$V_S = V_R + (2 + j7) \times I_R = 36950.42 \angle 0^\circ + (2 + j7) \times (631.48 \angle -36.87^\circ) = 40.71 \angle 3.91^\circ \text{ kV}.$$

Note that the no load voltage for short transmission line model is the same as sending end voltage at full load.

$$\text{Voltage regulation} = \frac{|V_{R,NL}| - |V_{R,FL}|}{|V_{R,FL}|} \times 100\% = \frac{40.71 - 36.95}{36.95} \times 100\% = 10.17\%$$

The complex power delivered at the load is given as 70 MVA, 0.8 lagging. Thus, real power delivered at the load is

$$P_{3\phi,R} = |S_{3\phi}| \times p.f. = 70 \times 0.8 = 56 \text{ MW}.$$

We then find real power at the sending end. For a short transmission line, sending end current is the same as receiving end current, $I_S = I_R = 631.48 \angle -36.87^\circ$.

The sending end three-phase complex power is found from $S_{3\phi,S} = 3V_S I_S^*$,

$$S_{3\phi,S} = 3 \times 40707.94 \angle 3.91^\circ \times 631.48 \angle 36.87^\circ = 58.39 + j50.37 \text{ MVA}$$

Three-phase real power at sending end $P_{3\phi,S} = 58.39 \text{ MW}$. The transmission efficiency is found below.

$$\eta = \frac{P_{R,3\phi}}{P_{S,3\phi}} \times 100\% = \frac{56}{58.39} \times 100\% = 95.91 \%$$

5.

The nominal pi-circuit is a medium-length line model, which is shown in Fig. 2.

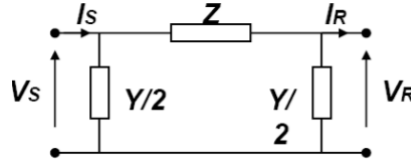


Fig.2

Given per phase series impedance per km and shunt admittance per km, the total impedance and admittances are found.

$$Z = 200 \times (0.08 + j0.48) = 16 + j96 \Omega$$

$$Y = 200 \times (j3.33 \times 10^{-6}) = (j6.66 \times 10^{-4}) \text{ siemens}$$

The ABCD parameters in the medium-length model can be found from below.

$$A = D = \frac{ZY}{2} + 1 = 0.9680 + j0.0053$$

$$B = Z = 16 + j96 \Omega$$

$$C = Y \left(1 + \frac{ZY}{4} \right) = (-1.7742 \times 10^{-6} + j6.5535 \times 10^{-4}) S$$

At full load, the line delivers 250 MW at 0.99 p.f. lagging at 220 kV (line-to-line). We first find the receiving end voltage per phase.

$$V_R = \frac{220 \times 10^3}{\sqrt{3}} \angle 0^\circ = 127.02 \angle 0^\circ \text{ kV.}$$

The receiving end current, I_R , can be found from the complex power consumed by the load at the receiving end, denoted by $P_{3\phi,R}$, of 250 MW, 0.99 lagging.

$$|I_R| = \frac{|P_{3\phi,R}|}{3|V_R| \times \text{p.f.}} = \frac{250 \times 10^6}{3 \times 127.02 \times 10^3 \times 0.99} = 662.69 \text{ A.}$$

The angle of receiving end current is found from power factor. The angle is negative because power factor is lagging.

$$\angle I_R = -\cos^{-1}(0.99) = -8.11^\circ$$

Using ABCD parameters found earlier, together with receiving end voltage and current, the sending end voltage and current is found.

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} 155.40 \angle 23.58^\circ \text{ kV} \\ 635.38 \angle -0.34^\circ \text{ A} \end{bmatrix}$$

6.

This is a medium length line as shown in Fig. 2.

Given per phase series impedance per km and shunt admittance per km, the total impedance and admittances are found.

$$Z = 130 \times (0.036 + j \times 100 \Pi \times 0.8 \times 10^{-3}) = 4.68 + j32.67 \Omega$$

$$Y = 130 \times (j \times 100 \Pi \times 0.0112 \times 10^{-6}) = (j4.57 \times 10^{-4}) \text{ Siemens}$$

The ABCD parameters in the medium-length model are found below.

$$A = D = \frac{ZY}{2} + 1 = 0.9925 + j0.0011$$

$$B = Z = 4.68 + j32.67$$

$$C = Y \left(1 + \frac{ZY}{4}\right) = (-0.2448 \times 10^{-8} + j0.4557 \times 10^{-5})$$

The receiving end load is 270 MVA with 0.8 lagging power factor at 325 kV. $V_R = \frac{325}{\sqrt{3}} \angle 0^\circ \text{ kV}$,

Find the receiving end current, I_R ,

$$|I_R| = \frac{|S_{3\Phi,R}|}{3|V_R|} = \frac{270 \times 10^6}{3 \times 187.64 \times 10^3} = 479.65 \text{ A.}$$

When power factor is 0.8, lagging.

$$I_R = |I_R| \angle -\cos^{-1}0.8 = 479.64 \angle -36.87^\circ \text{ A}$$

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} 187.64 \times 10^3 \angle 0^\circ \\ 479.64 \angle -36.87^\circ \end{bmatrix} = \begin{bmatrix} 197764 \angle 3.30^\circ \text{ V} \\ 430.27 \angle -27.66^\circ \text{ A} \end{bmatrix}$$

At full load, $|V_{R,FL}| = 187.64 \text{ kV}$.

$$\text{At no load, } I_R = 0, |V_{R,NL}| = \left| \frac{V_S}{A} \right| = \left| \frac{197764 \angle 3.30^\circ}{(0.9925 + j0.0011)} \right| = 199.25 \text{ kV}$$

$$\% \text{ Regulation} = \frac{|V_{R,NL}| - |V_{R,FL}|}{|V_{R,FL}|} \times 100\% = \frac{199.25 - 187.64}{187.64} \times 100\% = 6.19\%.$$

Transmission line efficiency:

$$S_{3\Phi,S} = 3V_S I_S^* = 3 \times 197764 \angle 3.30^\circ \times 430.27 \angle -27.66^\circ = 218.9 + j131.3 \text{ MVA.}$$

$$\eta = \frac{P_{R,3\Phi}}{P_{S,3\Phi}} \times 100\% = \frac{270 \times 0.8}{218.9} \times 100\% = 98.7\%$$

When power factor is 0.95, lagging.

$$I_R = |I_R| \angle -\cos^{-1}p.f. = 479.64 \angle -18.19^\circ \text{ A}$$

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} 187.64 \times 10^3 \angle 0^\circ \\ 479.64 \angle -18.19^\circ \end{bmatrix} = \begin{bmatrix} 193796 \angle 4.26^\circ \text{ V} \\ 456.70 \angle -7.88^\circ \text{ A} \end{bmatrix}$$

At full load, $|V_{R,FL}| = 187.64 \text{ kV}$.

$$\text{At no load, } I_R = 0, |V_{R,NL}| = \left| \frac{V_S}{A} \right| = \left| \frac{193796 \angle 4.26^\circ}{(0.9925 + j0.0011)} \right| = 195.26 \text{ kV}$$

$$\% \text{ Regulation} = \frac{|V_{R,NL}| - |V_{R,FL}|}{|V_{R,FL}|} \times 100\% = \frac{195.26 - 187.64}{187.64} \times 100\% = 4.06\%.$$

Transmission line efficiency:

$$S_{3\Phi,S} = 3V_S I_S^* = 3 \times 193796 \angle 4.26^\circ \times 456.70 \angle -7.88^\circ = 259.58 + j55.84 \text{ MVA.}$$

$$\eta = \frac{P_{R,3\Phi}}{P_{S,3\Phi}} \times 100\% = \frac{270 \times 0.95}{259.58} \times 100\% = 98.8\%$$

When the power factor is close to one, the transmission line efficiency and voltage regulation is improved.