



EE2029: Introduction to Electrical Energy Systems

AC Power


Lecturer : Dr. Sangit Sasidhar (elesang)
Department of Electrical and Computer Engineering

Impedance Triangle




$$Z_{RL} = R + j\omega L$$
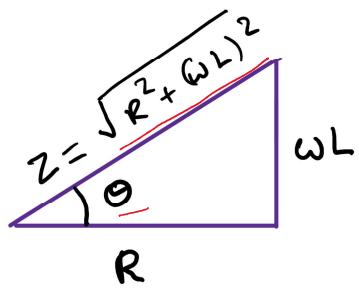
$$\theta = \tan^{-1} \frac{\omega L}{R}$$




$\theta \nearrow +ve$
 $\nwarrow -ve$

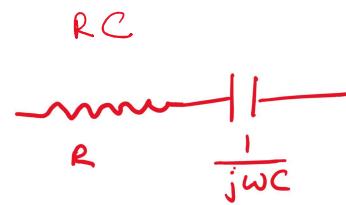


$$Z_{RC} = R - \frac{j}{\omega C}$$
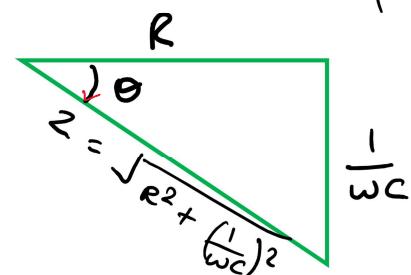
$$\theta = \tan^{-1} \left(\frac{1/\omega C}{R} \right)$$



2

Power in Inductor and Capacitor

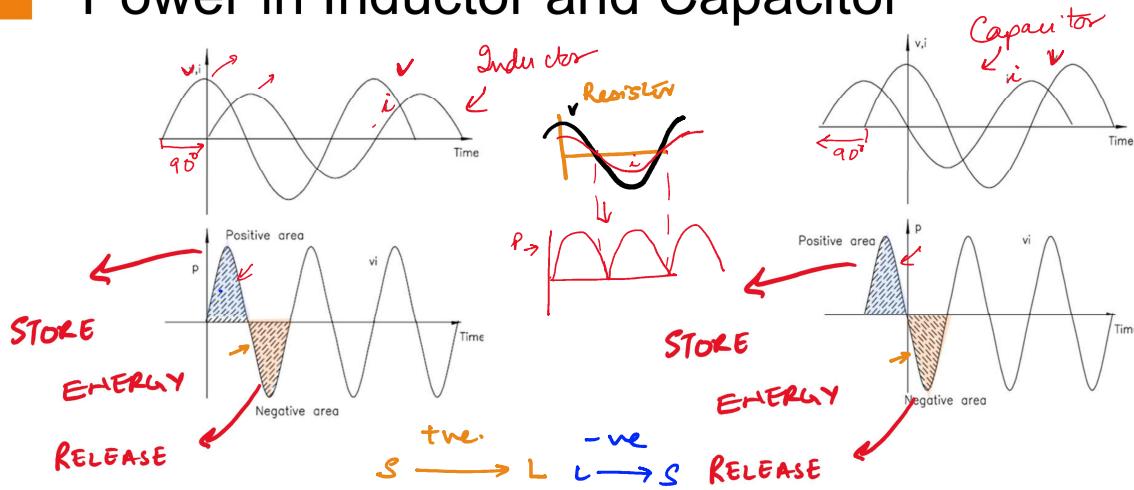


Both inductor and capacitor store and release energy during the AC cycle. When both the voltage and current are of the same sign, the element (L or C) draws energy equivalent to the area under the positive half cycle of $p(t)$ from the source and stores it. When they are of opposite signs, it is returning the energy to the source.

$P_{dc} \rightarrow V_{dc} I_{dc}$
 $\rightarrow P_{ac (e)} \rightarrow V_{rms} I_{rms}$

$X \rightarrow$ Reactive component
 L or C

Power in AC Circuits

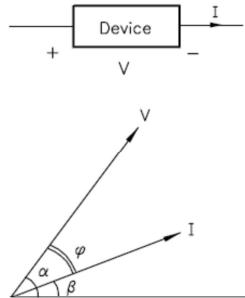

$Z \rightarrow$ IMPEDANCE OF DEVICE

$$Z = R + jX = |Z| \angle \theta - \textcircled{1}$$

$$|Z| = \sqrt{R^2 + X^2}$$

$$Z = \frac{V}{I} = \frac{|V| \angle \alpha}{|I| \angle \beta} = \left| \frac{V}{I} \right| \angle (\alpha - \beta) = \left| \frac{V}{I} \right| \angle \phi - \textcircled{2}$$

$$\Rightarrow \theta = \phi = \alpha - \beta = \text{IMPEDANCE ANGLE}$$


$$V = |V| \angle \alpha$$

$$I = |I| \angle \beta$$

REAL POWER


$$P = |I|^2 R$$

$$= |I| |I| R$$

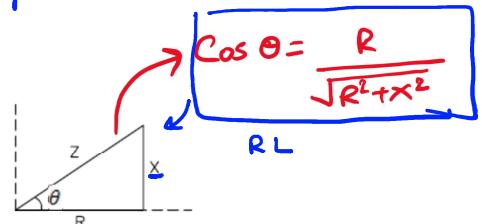

$$P = \frac{|V| |I| R}{|Z|} = \frac{|V| |I|}{\sqrt{R^2 + X^2}} \cdot |I| R$$

$$P = |V| |I| \frac{R}{\sqrt{R^2 + X^2}} = \boxed{|V| |I| \cos \theta}$$

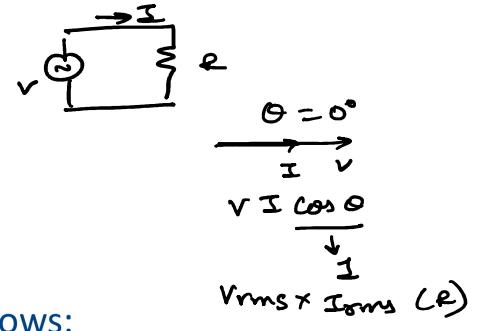

Apparent Power

- We express power in d.c. and a.c. circuits as follows:

$$P_{dc} = V_{dc} I_{dc} \text{ WATTS}$$

$$\underline{P_{ac} = V_{rms} I_{rms} \cos \theta \text{ WATTS}}$$

- In a.c. circuits an additional term $\cos \theta$ has occurred in the expression for **Real** power
- Define Apparent Power $\rightarrow |S| = V_{rms} I_{rms}$
- Units of Apparent Power $\rightarrow \text{VA (VOLT AMPERES)}$
- So, the **Real** power in a.c. circuit may also be expressed in terms of apparent power as


$$|P| = |S| \cos \theta$$

Reactive Power

- Real Power \rightarrow Power in the Resistor
- Average power in inductor or capacitor = 0
- Define Reactive Power (Q) \rightarrow Power stored/released by the inductor or capacitor.

REACTIVE POWER

$$\begin{aligned} Q &= I^2 X \\ &= |I| |I| X \\ &= \frac{|V| |I|}{|Z|} X \\ &= |V| |I| \frac{X}{\sqrt{R^2 + X^2}} \end{aligned}$$

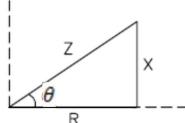

$$Q = j\omega L$$

$$\frac{X}{\sqrt{R^2 + X^2}} = \sin \theta$$

$$Q = -j \frac{1}{\omega C}$$

$$\frac{X}{\sqrt{R^2 + X^2}} = -\sin \theta$$

$$Q_{RL} = V_{rms} I_{rms} \sin \theta$$

$$Q_{RC} = -V_{rms} I_{rms} \sin \theta$$

P, Q, S





Power Triangle

- P – Real (or active) Power: Power consumed in the resistive part of the circuit
- Q – Reactive Power: Power stored in the inductor or capacitor
- $|S|$ – Apparent Power: Combines P and Q in one quantity
 - Indication of Current the System can support

$$P = V_{\text{rms}} I_{\text{rms}} \cos\theta$$

$$S = V_{\text{rms}} I_{\text{rms}}$$
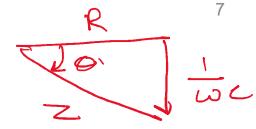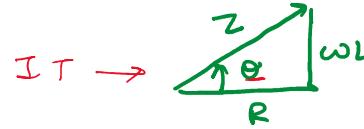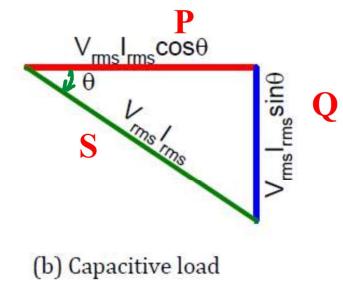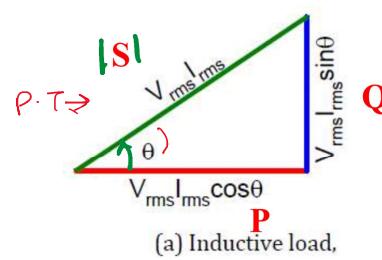
$$Q = V_{\text{rms}} I_{\text{rms}} \sin\theta$$



Complex Power

- Define Complex Power

$$S = |S| \angle \theta$$

IMPEDANCE
 $z = r + jx = |z| \angle \theta$

$$S = V_{rms} I_{rms} \angle \theta \Rightarrow S = V_{rms} I_{rms} \angle \alpha - \beta$$

$$\Rightarrow S = V_{rms} \angle \alpha \cdot I_{rms} \angle \beta$$



I^* = COMPLEX CONJUGATE OF $I = I_{rms} \angle -\beta$

$$\Rightarrow S = V I^* = P + jQ$$

COMPLEX POWER


$$I \rightarrow |I| \angle \beta$$

$$\rightarrow I^* \rightarrow |I| \angle -\beta$$

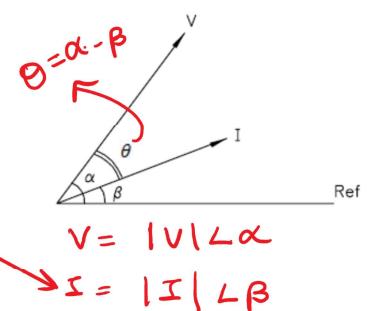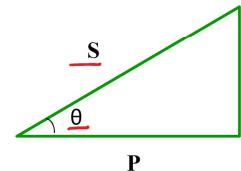

Power in an Inductor
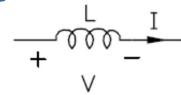
$$\text{IMPEDANCE OF AN INDUCTOR} = Z_L = j\omega L = \omega L L 90^\circ \angle$$



$$I = \frac{V}{Z_L} = \frac{|V| L 90^\circ}{\omega L L 90^\circ} = \left| \frac{V}{\omega L} \right| L 90^\circ = |I| L 90^\circ$$

$$V = |V| L 0^\circ$$


$$\begin{aligned}\text{COMPLEX POWER IN AN INDUCTOR } S_L &= VI^* = V L 0^\circ \cdot I L 90^\circ \\ &= Z_L I \cdot I^* = j\omega L |I|^2\end{aligned}$$

$$\text{REAL POWER CONSUMED BY INDUCTOR} = |V||I| \cos 90^\circ = 0$$

$$\text{REACTIVE POWER CONSUMED BY INDUCTOR} = |V||I| \sin 90^\circ = |V||I| = \omega L |I|^2$$

Power in a Capacitor
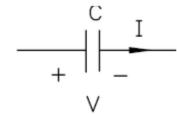
$$\text{IMPEDANCE OF A CAPACITOR} = Z_C = \frac{1}{j\omega C} = \frac{1}{\omega C} \angle -90^\circ$$



$$I = \frac{V}{Z_C} = \frac{|V| \angle 0^\circ}{\frac{1}{\omega C} \angle -90^\circ} = |V| \omega C \angle 90^\circ = |I| \angle 90^\circ$$

$$V = |V| \angle 0^\circ$$

$$\text{COMPLEX POWER IN A CAPACITOR} \quad S_C = V I^* = Z_C I \cdot I^* = -j \frac{|I|^2}{\omega C}$$

$$\text{REAL POWER CONSUMED BY CAPACITOR} = |V||I| \cos(-90^\circ) = 0$$

$$\begin{aligned} \text{REACTIVE POWER CONSUMED BY CAPACITOR} &= |V||I| \sin(-90^\circ) = -|V||I| = -\frac{|I|^2}{\omega C} \\ &= -\underline{\omega C |V|^2} \end{aligned}$$

INDUCTANCE \rightarrow +ve REACTIVE POWER

CAPACITANCE \rightarrow -ve REACTIVE POWER

Complex Power of Series and Parallel Connected Loads

• Series Connected Loads


$$S = V_s I^*$$

$$V_s = V_1 + V_2$$

$$\Rightarrow S = (V_1 + V_2) I^*$$

$$= V_1 I^* + V_2 I^*$$

$$= S_1 + S_2$$

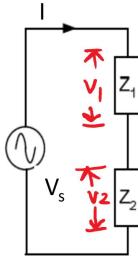

$$|S| \neq |S_1| + |S_2|$$

© Copyright National University of Singapore. All Rights Reserved.

• Parallel Connected Loads


$$S = V I^*$$

$$I = I_1 + I_2$$

$$\Rightarrow S = V (I_1 + I_2)^*$$

$$= V I_1^* + V I_2^*$$

$$= \underline{S_1 + S_2}$$

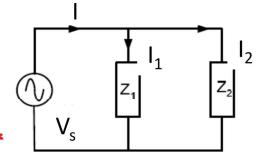

$$|S| \neq |S_1| + |S_2|$$

11

$$P_1 + P_2 = P$$


$$Q_1 + Q_2 = Q$$

$$S_1 + S_2 = S$$

$$|S_1| + |S_2| \neq |S|$$



$$P = P_1 + P_2$$

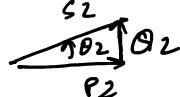

$$Q = Q_1 + Q_2$$

Complex Power Summary

Units			
\underline{S}	Complex power	VA	$\underline{VI}^* = P + jQ = S \angle \theta$
$ S $	Apparent power	VA	$ S = V I = \sqrt{P^2 + Q^2}$
P	Active power Average power, Real power	W	$P = \text{Re}(S) = V I \cos \theta$ $= S \cos \theta$
Q	Reactive power	VAR	$Q = \text{Im}(S) = V I \sin \theta$ $= S \sin \theta$

$$\theta = +ve \rightarrow R L$$

$$\theta = -ve \rightarrow R C$$

$$P = IS \cos \theta$$


$$\cos \theta = \frac{P}{IS} \rightarrow \text{Power Factor}$$

Power Factor


- Let us define Power Factor of an AC circuit as the ratio of the real power to the apparent power

- Power Factor = $\frac{P}{S} = \frac{P}{|V||I|} = \cos \theta$

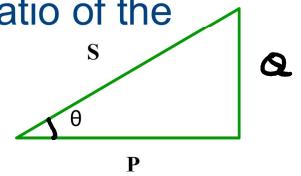- If ' θ ' is larger, power factor ($\cos \theta$) is smaller



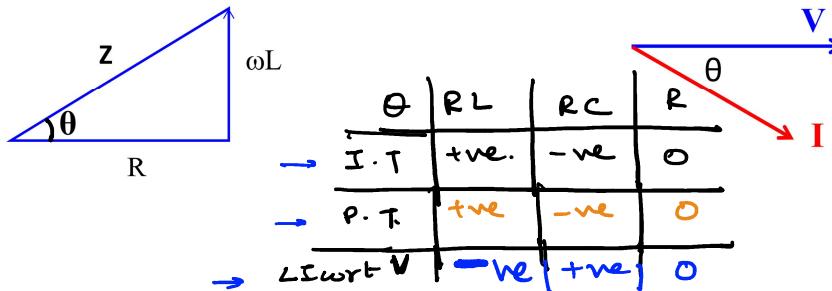- Power factor angle (θ) is the same in the power triangle, impedance triangle and the angle between the voltage and the current




13

$I \text{ wrt } V \rightarrow -30^\circ \rightarrow (\text{lagging})$

$RL \rightarrow P.T \rightarrow +30^\circ$

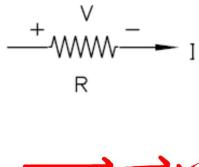Power Factor for Resistive, Inductive and Capacitive Load



$$|S| = VI$$

$P = VI \cos \theta$

$\theta = 0^\circ$


$S = VI, P = VI$

power factor = $\frac{P}{S} = 1$

UNITY POWER FACTOR

RL

$$Z = R + j\omega L = R + jX_L = |Z| \angle \theta$$

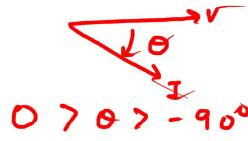

$$|S| = VI$$

$$P = VI \cos \theta$$

Power factor = $\cos \theta$

Range (0 to 1)

lagging

↓

I wrt V

RC

$$Z = R - j\frac{1}{\omega C} = R - jX_C = |Z| \angle -\theta$$



$$0 < \theta < 90^\circ$$

$$|S| = VI$$

$$P = VI \cos \theta$$

Power factor = $\cos \theta$

Range (0 to 1)

leading

↓

I wrt V

© Copyright National University of Singapore. All Rights Reserved.

■ How do we Improve Poor Power Factor?

$I \rightarrow$ Heat (R)

$I \rightarrow$ Charging (C or L)

P

Unity P.F \rightarrow Current $\rightarrow R$ (Heat)

$$0.9 \rightarrow \frac{R}{Z} \propto \frac{1}{C}$$

$$0.8 \rightarrow$$


$$0.7$$

Poor Power Factor

- If the power factor is poor (i.e., very low), current drawn by the load will be high.




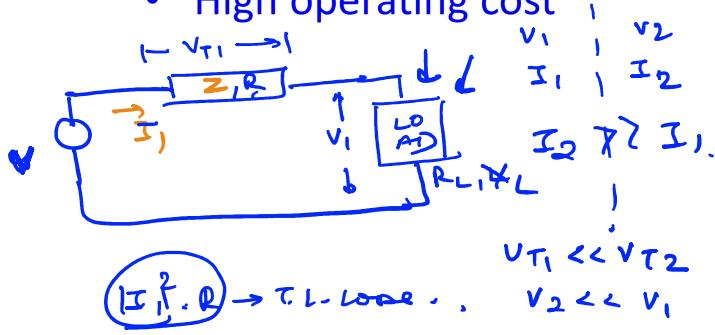
- Poor voltage regulation at the load
- Heavy transmission lines losses
- High operating cost



$$V_1 = V - V_{T_1}$$

$$V_{T_1} = I_1 \cdot Z$$

$$V_{C_2} = I_2 \cdot Z$$

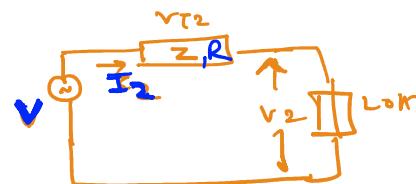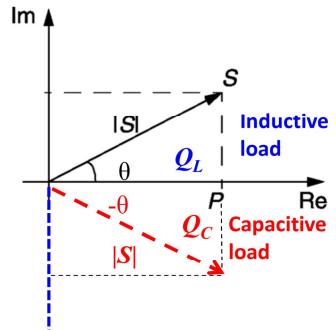


$$I_2^2 \cdot R \rightarrow T.L. Losses$$

$$V_2 = V - V_{T_2}$$

16

Power Factor Correction (PFC)

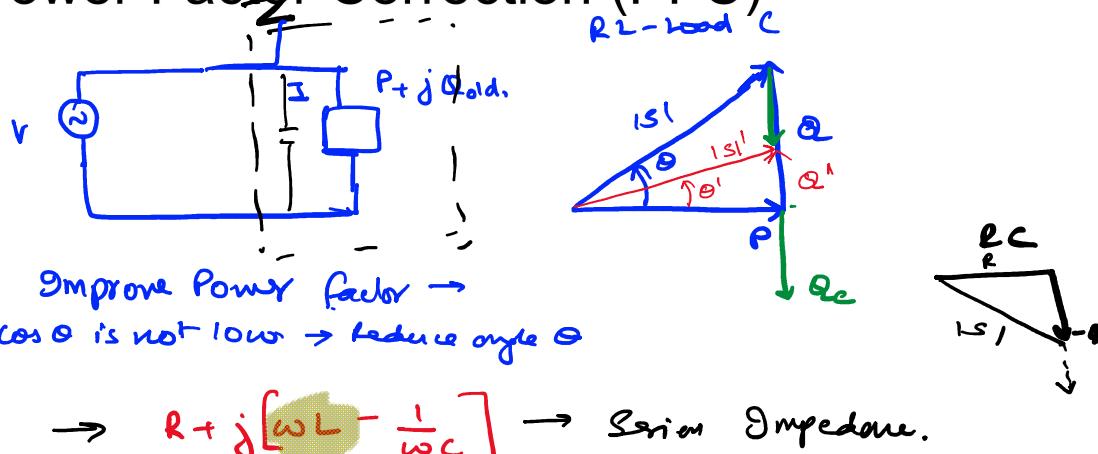


Aim \rightarrow Reduce θ so that $\cos\theta$ is larger \rightarrow reduce Q



$R_L \rightarrow$ We add a capacitor to improve p.f.

$R_C \rightarrow$ We add an inductor to improve p.f.

17

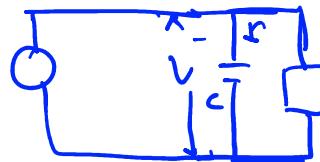


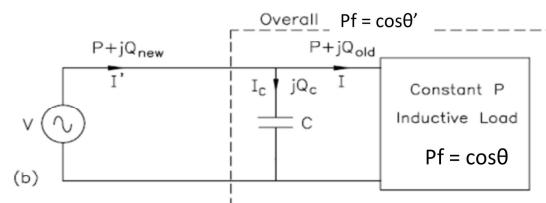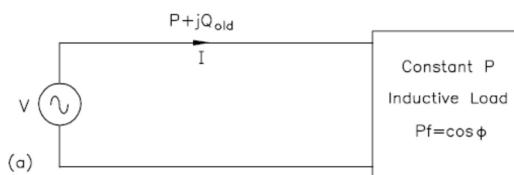PFC: Fixed Capacitive Load \rightarrow New Power Factor



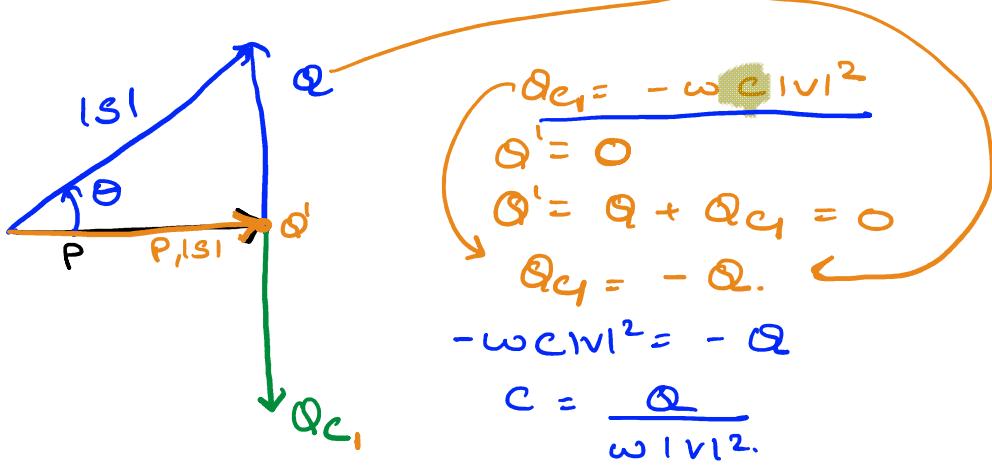a) low power factor \rightarrow unity power factor
lagging. $\rightarrow \theta' = 0^\circ$





18


b) low power factor lagging \rightarrow better power factor lagging.

$$0.4 \text{ lag} \xrightarrow{\cos\theta} 0.9 \text{ lag.} \xrightarrow{\cos\theta} \underline{Q' = Q + QC_2}$$

$$\cdot P = s \cos\theta$$


$$s = \frac{P}{\cos\theta}$$

$$Q = s \sin\theta = P \tan\theta$$


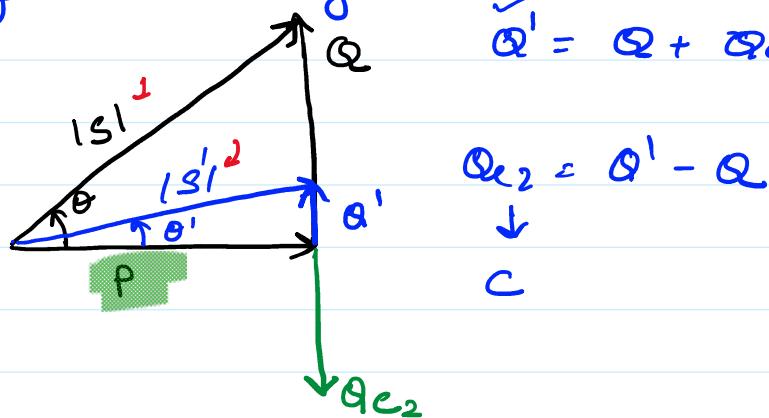


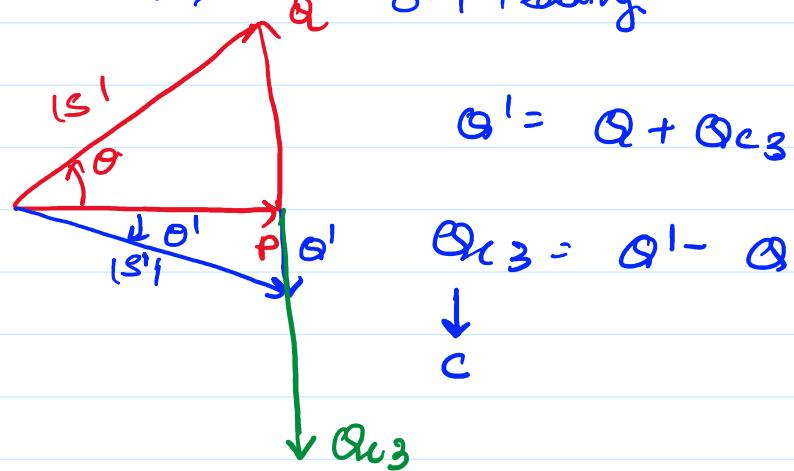c) low power factor lagging \rightarrow better power factor leading.


$$0.4 \text{ lag} \xrightarrow{\cos\theta} 0.9 \text{ leading}$$



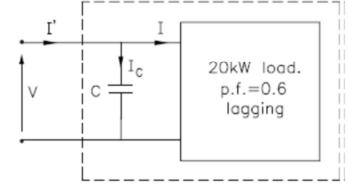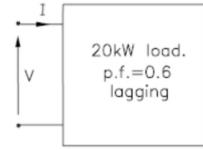
Example: A load connected across a 230V, 50HZ line draws 20kW at 0.6pf lagging. Determine the current drawn by the load. If a capacitor of 800 μ F is connected in parallel with the load, what will be the current drawn from the source? Also determine the overall power factor of the system as seen by the source



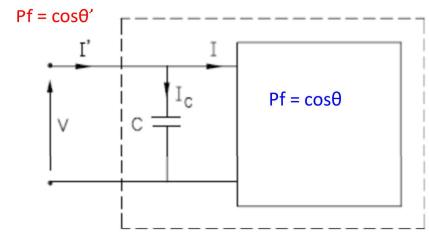■ PFC: Required Power Factor \rightarrow Capacitive Load



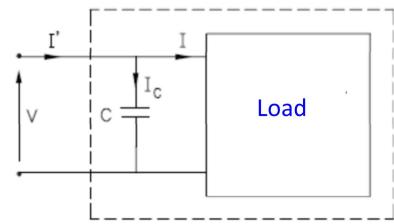Example :A load connected across a 200 V, 50Hz line draws 10 kW at 0.5 power factor lagging. Determine the current drawn by the load. A capacitor C is now connected in parallel with the load to improve the power factor. What must be the value of C to make the overall power factor 0.9 lagging




■ Thank You

© Copyright National University of Singapore. All Rights Reserved.

22

$R C \rightarrow R - \tau \rightarrow$

$$S = 1s/L - 45^\circ$$

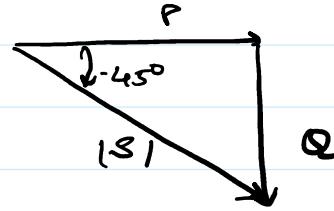

$Z \rightarrow 100 \Omega$.

$V \rightarrow \text{Same}$

$R \rightarrow 100 \Omega$.

R_L .

$$R' = \sqrt{10^2 - \omega^2 L^2}$$

$$\overline{R' < R_L}$$

$$|I| = \frac{|V|}{|Z|} = \text{same}$$

$\xrightarrow{k \leftarrow k_1}$

$$\begin{aligned} P' &= |I|^2 R' \\ P &= |I|^2 R \end{aligned} \quad \left\{ \begin{array}{l} P' < P \end{array} \right.$$

$$P \rightarrow |V| |I| \cos \theta$$

$$S \rightarrow |V| |I|$$



Projection of $|V| |I|$ on x -axis is P



$$|V| |I| \cos \theta$$



$|V| |I| \cos \theta \rightarrow$ projection of $|V| |I|$ on x -axis

$$|I| \cos \theta = I \cos \theta$$

$$\begin{aligned} Tr 1 &\rightarrow \\ 1000W & \\ P.F. \rightarrow 0.5 \text{ lag.} & \end{aligned}$$
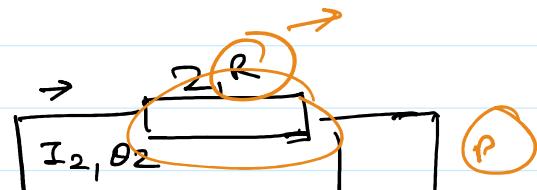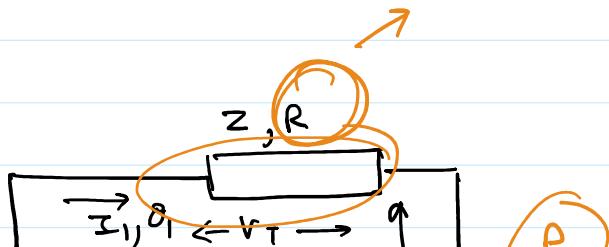
$$\begin{aligned} Tr 2 &\rightarrow \\ 1000W & \\ P.F. \rightarrow 0.9 \text{ lag.} & \end{aligned}$$




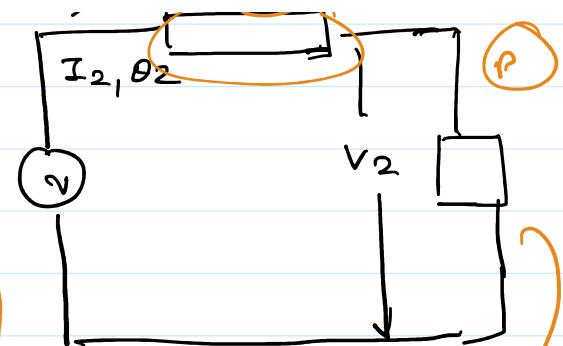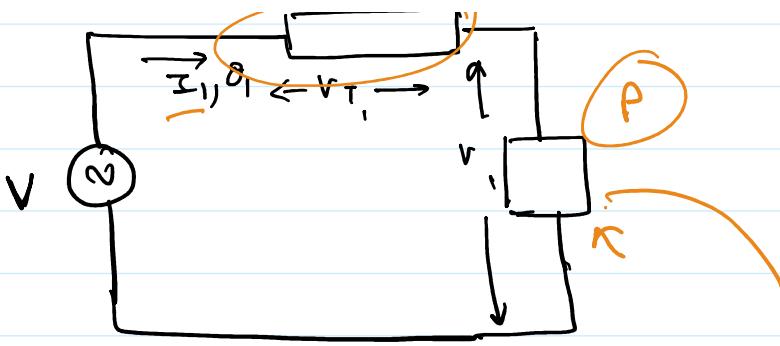

$$\begin{aligned} \theta_2 &> \theta_1 \\ \Rightarrow \cos \theta_2 &< \cos \theta_1 \\ \rightarrow |I_2| &> |I_1| \end{aligned}$$

$$|I_1|^2 \quad |I_2|^2$$

$$P = |V| |I_1| \cos \theta_1 = P = |V| |I_2| \cos \theta_2$$

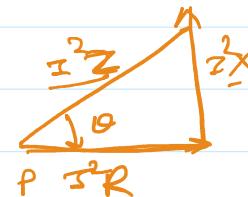

$$(I_1) \cos \theta_1 = (I_2) \cos \theta_2$$

$$\begin{aligned} \rightarrow V_{T1} &\propto I_1^\star \\ &= P_{T1} + j Q_{T2} \end{aligned}$$

$$\begin{aligned} V_{T2} &\propto I_2^\star \\ &= P_{T2} + j Q_{T2}. \end{aligned}$$

$$V_{T1} \approx V_{T2}$$

$$P_{T1} = V_{T1} I_1 \cos \theta_T$$

$$P_{T2} = V_{T2} I_2 \cos \theta_T$$