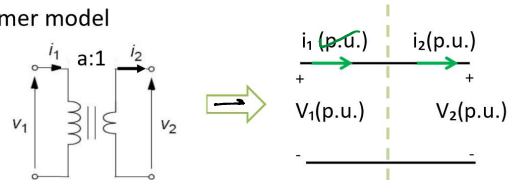





P.U. Equivalent Circuit of a Transformer

- Ideal transformer model





- Practical transformer model

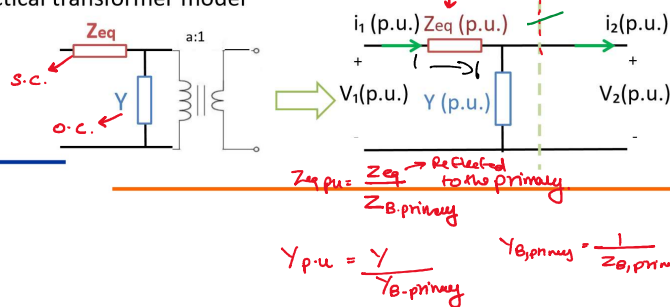

Change of Base Value

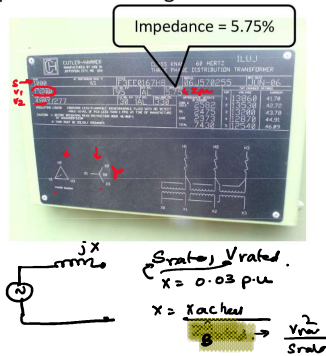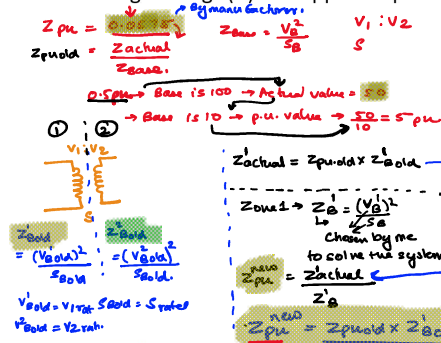- Manufacturers usually specify equipment impedances in per unit values together with voltage ratings (V) and apparent power rating (VA).




$Z_B \rightarrow 100 \Omega$
 $jX \rightarrow j10 \rightarrow 10 \angle 90^\circ$
 $X_{pu} = \frac{10 \angle 90^\circ}{100} = 0.1 \angle 90^\circ$ (RIGHT) ✓
 $X_{pu} = \frac{10 \angle 90^\circ}{100 \angle 90^\circ} = 0.1 \angle 0^\circ$ (WRONG) ✗
 WRONG BASE ↓
 $Z_B \rightarrow 100 \angle 90^\circ \Omega$
 $jX \rightarrow j10 \rightarrow 10 \angle 90^\circ$

Advantages of Per Unit Analysis

- ✓ Simplify calculation by eliminating transformers.
 - ⇒ p.u. is more uniform compare to actual impedance value of different sizes of equipment.
- ✓ Helps to spot errors in the data
 - Operator at control center can spot over/under voltage/current rating easily.



12

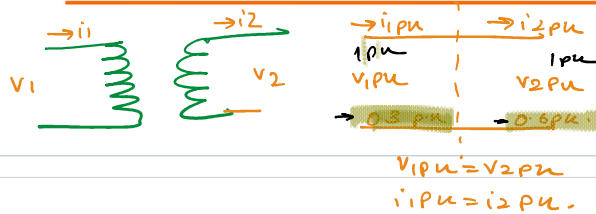

Steps of 1 Φ Per Unit Analysis

1. Choose $S_B^{1\Phi}$ for the system.
2. Select V_B for different zones (usually follows transformer voltage ratings).
 → Choose or given V_B for one of the zones
 → calculate V_B for other zones using transformer ratio.
3. Calculate Z_B for different zones.
 → $Z_B = \frac{V_B^2}{S_B}$
4. Express all quantities in p.u.
5. Draw impedance diagram and solve for p.u. quantities.
6. Convert back to actual quantities if needed.

4.1 → Find new p.u. impedance values if manufacturer has given impedance in p.u. instead of ohms.

13

Three-Phase Transformers



Three-phase transformers
at substations



Source: <http://www.meidensg.com.sg>

Pole-mounted
three single-phase
transformers.



14


3 Φ Transformer Connection

designation	winding connection	single-phase equivalent
Yy		
Yd		
Dy		
Dd		


- The voltage rating of a three phase transformer is the ratio between **line-to-line** voltage at the primary side and **line-to-line** voltage at the secondary side.
- The single-phase equivalent shows line-to-neutral voltage.
- For Y-Y and Δ - Δ transformers, voltage and current in both primary and secondary are in phase. The ratio of the voltage and current follows the turn ratio of the transformer.
- The same does not apply to Y- Δ and Δ -Y connections.


15

\Rightarrow 3 Φ Transformer connections,

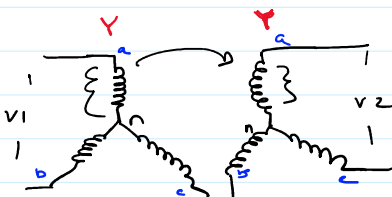


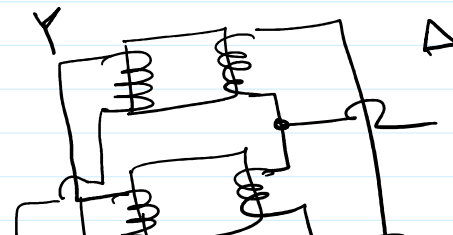
Voltage rating of a 3 Φ transformer.
 \rightarrow Ratio of the line voltage of primary
to the line voltage of secondary.
 \rightarrow Voltage & current in both primary & secondary.



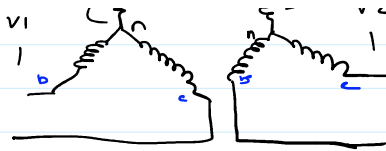

to the line voltage of secondary.

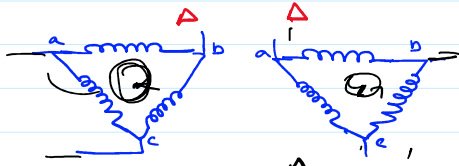
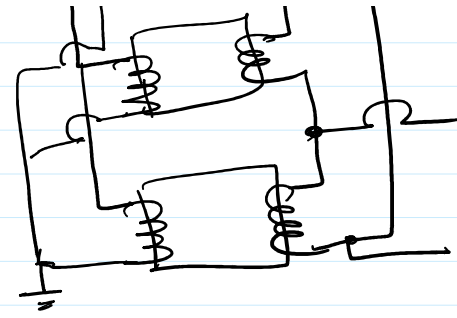
→ Voltage & current in both primary and secondary are in phase with each other.
→ Y-Y, Δ-Δ



→ Y-Δ or Δ-Y configuration

→ Phase shift of $\pm 30^\circ$ in both voltage & current of secondary with respect to primary,

→ Y-Δ → Step down transformer

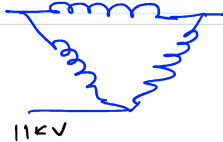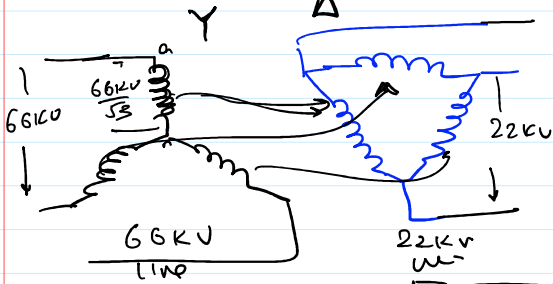

→ Δ-Y → Step up transformer




Y-Δ 3Φ Transformer: Per Phase Model

For a positive sequence voltage source,

$$V_{A1-n} = \left[\frac{N_1}{N_2} \right] \sqrt{3} V_{A2-n} \angle 30^\circ$$



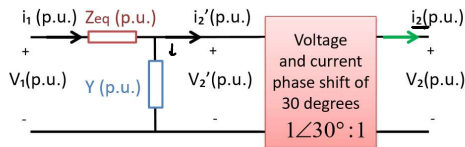
$$\angle V_{A1-n} : \angle V_{A2-n} = 1 \angle 30^\circ : 1$$




$$i_2 = i_2' \angle -30^\circ$$

$$V_2 = V_2' \angle -30^\circ$$

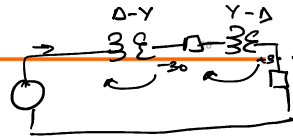Δ-Y → $i_2 \rightarrow i_2' \angle 30^\circ$
 $v_2 \rightarrow v_2' \angle 30^\circ$



3Φ Transformer Per Unit Model

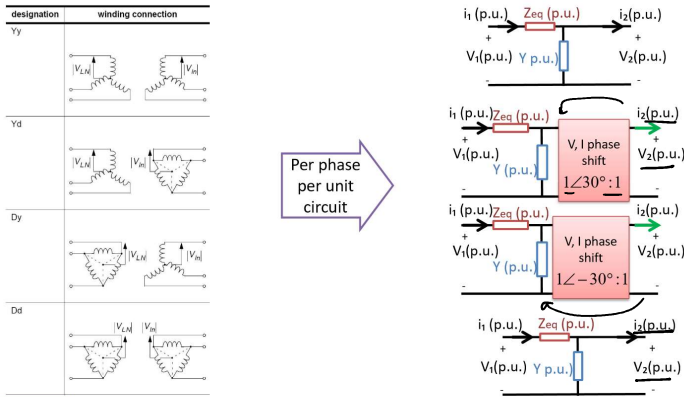

17

3Φ system

→ Voltage is line-to-line voltage.

→ Current is line current.

→ Apparent power → 3Φ power

$$|S_{3\phi}| = \sqrt{3} |V_{\text{line-line}}| |I_{\text{line}}|$$

3Φ Base Values

- Complex Power Base → single $S_{3\phi}$ for the whole system
- Voltage Base → Each zone different base value.
→ $V_{\text{line-line}}^B$
- Current Base
 $V_{\text{line-line}}^B / \sqrt{3} = V_{\text{ph}}^B$ → Different for each zone
 $I_{\text{line}}^B = \frac{S_B}{\sqrt{3} V_{\text{line-line}}^B}$
- Impedance Base → Different for each zone

$$Z_B = \frac{V_{\text{line-line}}^2}{S_{3\phi}^B}$$

18

Steps of Calculation: 3 Φ Case

1. Choose $S_B^{3\Phi}$ for the system.
2. Select $V_B^{\text{line-to-neutral}}$ or $V_B^{\text{line-to-line}}$ for different zones.
3. Calculate Z_B for different zones.
4. Express all quantities in p.u.
5. Draw impedance diagram and solve for p.u. quantities.
6. Convert back to actual quantities if needed.

Note that the **per unit circuit** is the circuit in **per-phase analysis** with normalization of the voltage magnitude at different locations. This means that **the phase of voltage** in per unit analysis **refers to the line-to-neutral voltage**.