
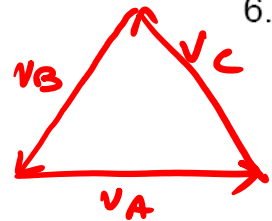


EE2029: Introduction to Electrical Energy System


3-Phase Power

Lecturer : Dr. Sangit Sasidhar
Department of Electrical and Computer Engineering

Three-Phase Voltage Sources

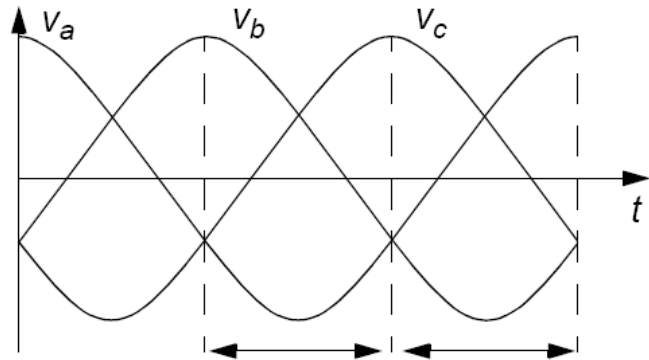

$$V_A + V_B + V_C = 0$$

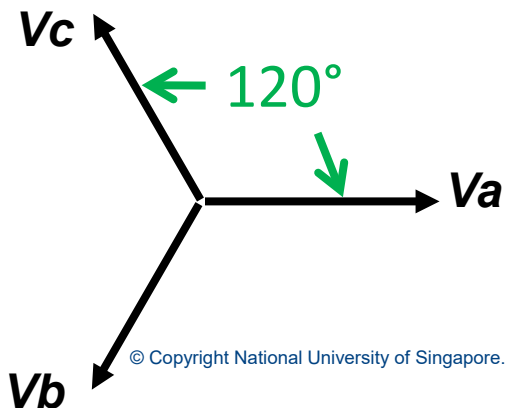


$$v_a = \sqrt{2}|V|\cos(\omega t)$$


$$v_b = \sqrt{2}|V|\cos\left(\omega t - \frac{2\pi}{3}\right)$$

$$v_c = \sqrt{2}|V|\cos\left(\omega t - \frac{4\pi}{3}\right)$$






• Positive Sequence

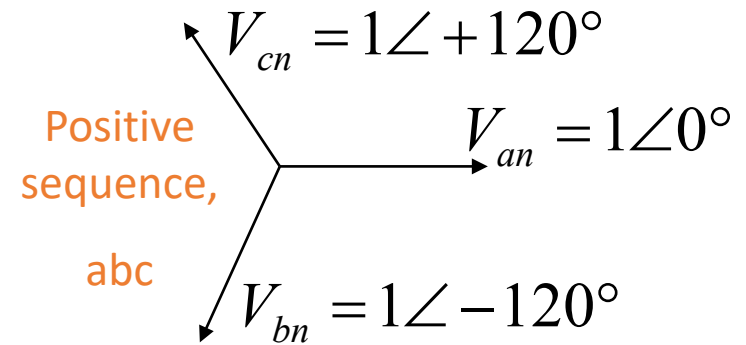

• Negative Sequence

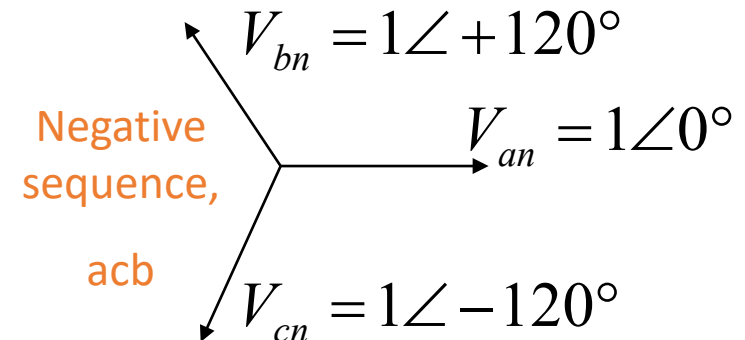

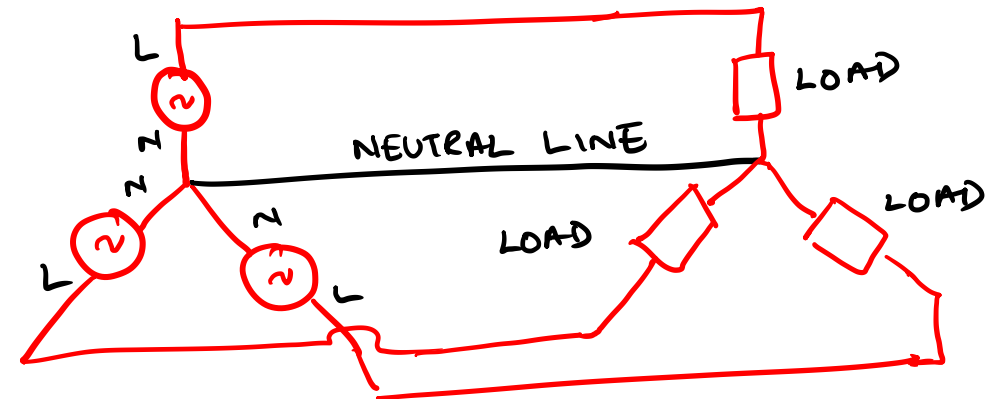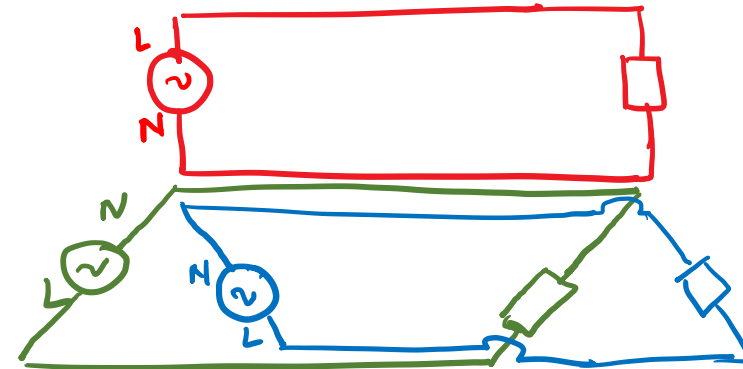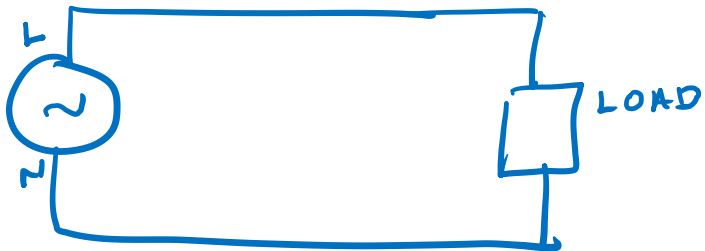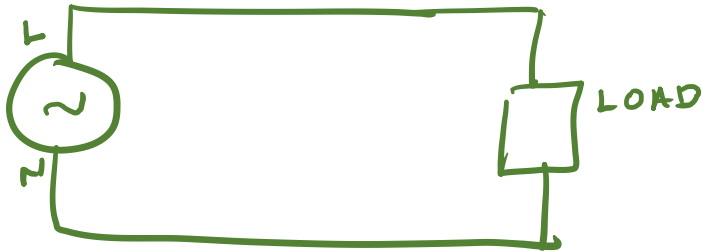
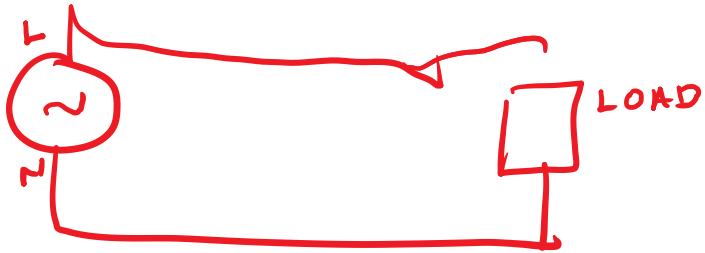
Three Single Phase vs Three Phase Circuits



REDUCED CONDUCTORS FROM
6 TO 4 \Rightarrow 33.33% SAVINGS

Balanced Three-Phase Circuit

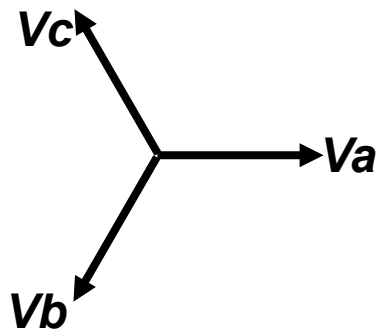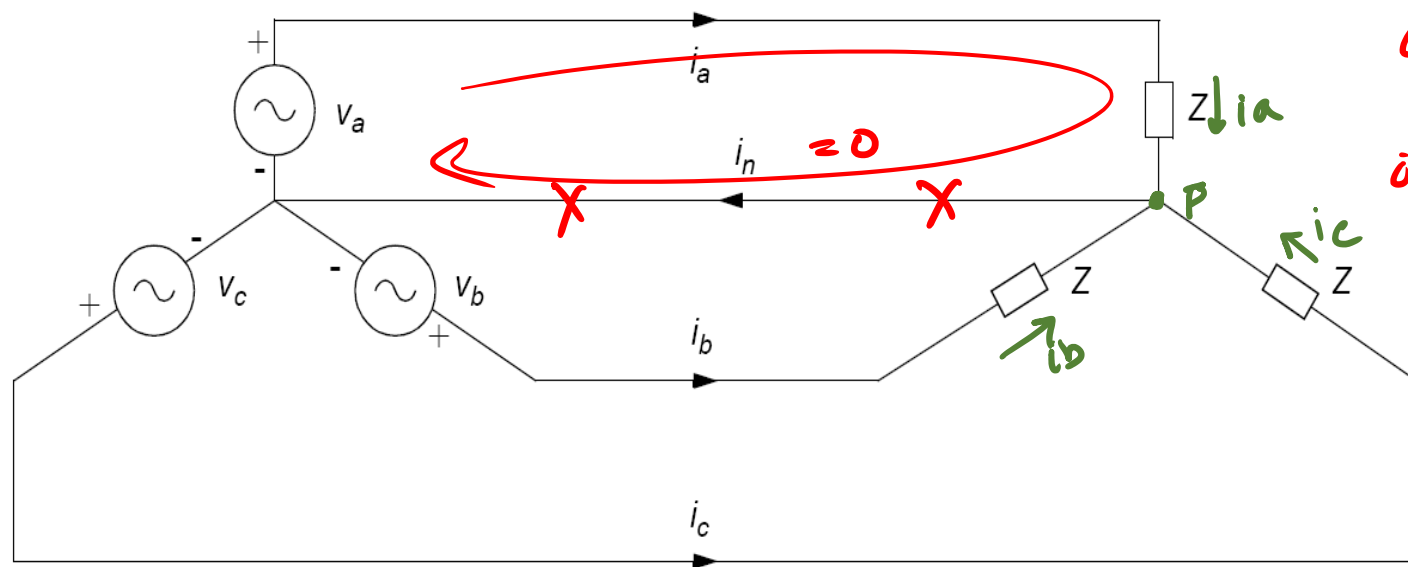- Three-phase circuit is said to be balanced when the impedances in the 3 phases are identical



$$\begin{aligned} V_a &= 1 \angle 0^\circ \\ V_b &= 1 \angle -120^\circ \\ V_c &= 1 \angle +120^\circ \end{aligned}$$

$$i_a = \frac{V_a}{Z}$$

$$i_b = \frac{V_b}{Z}$$

$$i_c = \frac{V_c}{Z}$$


$$\begin{aligned} \text{KCL @ node P} \\ i_a + i_b + i_c = i_n \end{aligned}$$

$$\begin{aligned} i_a + i_b + i_c \\ = \frac{V_a}{Z} + \frac{V_b}{Z} + \frac{V_c}{Z} = \frac{1}{Z} (V_a + V_b + V_c) \end{aligned}$$


$$= \frac{0}{Z} = 0 = i_n \quad \Bigg| \quad \Rightarrow i_n = 0$$

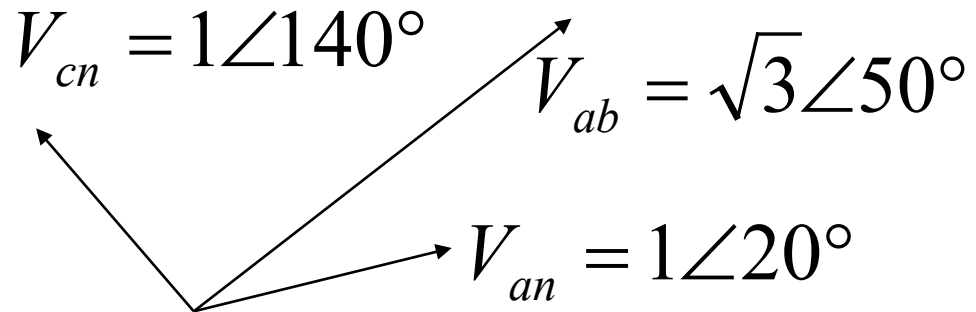Example:



- What is the phase sequence?
- Are these balanced three-phase voltage sources?



How do we Measure Voltage/Current

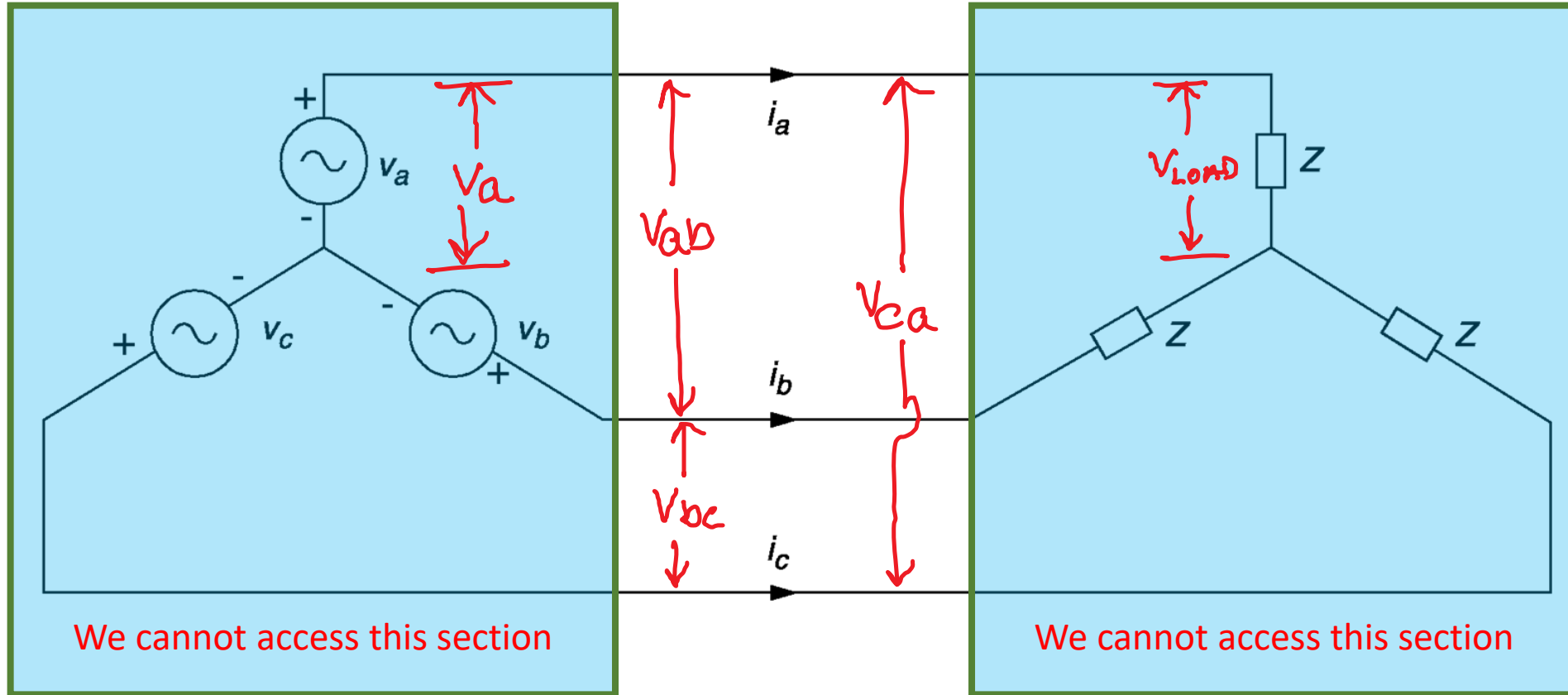

Line-To-Line Voltage (Line Voltage)

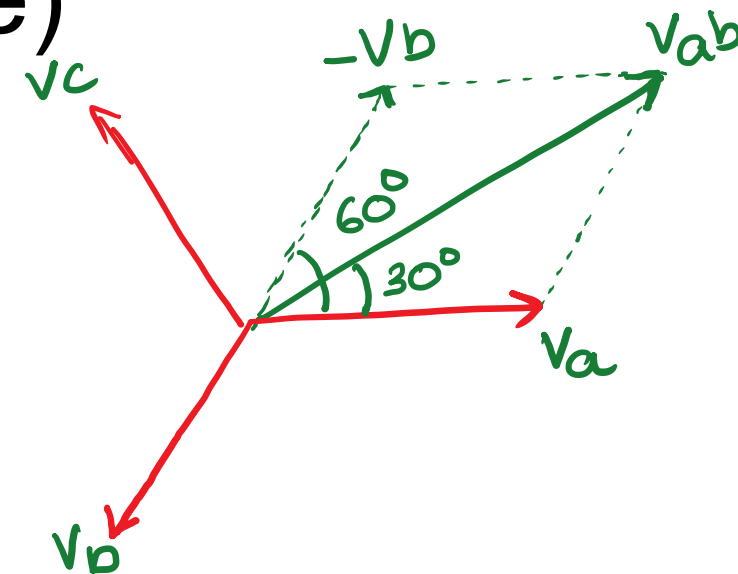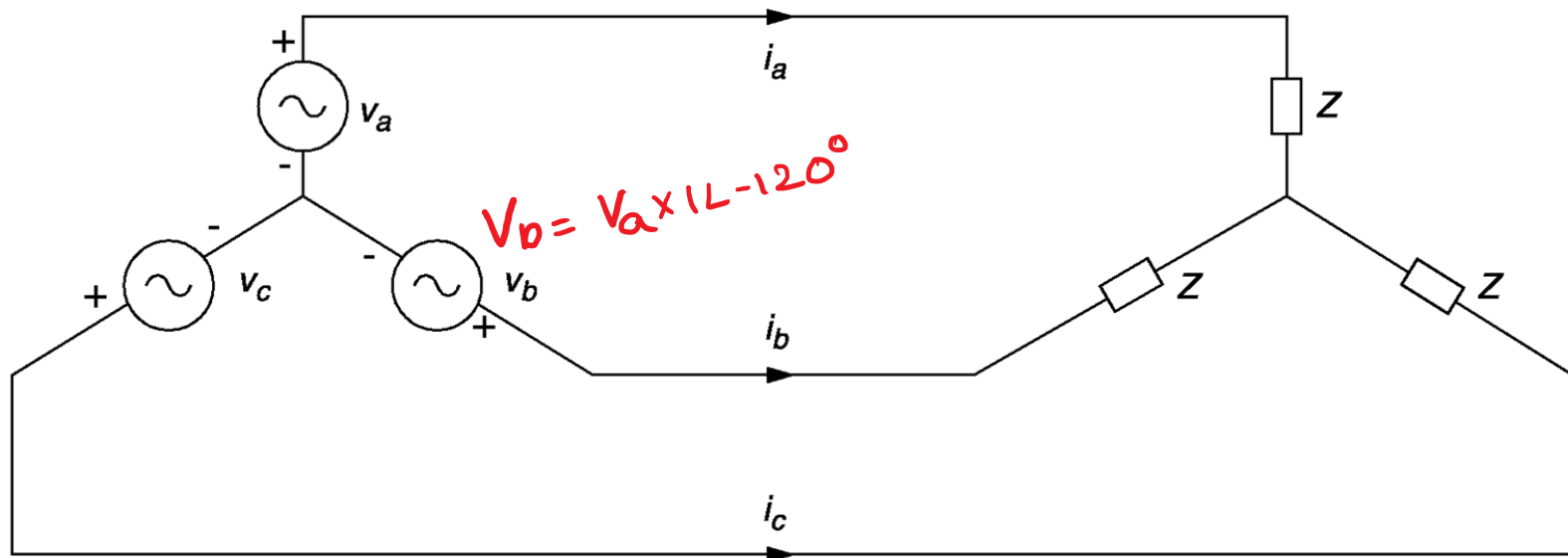

$$\begin{aligned}
 V_{ab} &= V_a - V_b = V_a + (-V_b) \\
 &= V_a + V_a \angle 60^\circ \\
 &= V_a \angle 0^\circ + V_a \angle 60^\circ \\
 &= \sqrt{3} V_a \angle 30^\circ
 \end{aligned}$$

$$\begin{aligned}
 V_{bc} &= V_b + (-V_c) \\
 &= \sqrt{3} V_b \angle 30^\circ \\
 V_{ca} &= V_c + (-V_a) \\
 &= \sqrt{3} V_c \angle 30^\circ
 \end{aligned}$$

Line-To-Neutral Voltage (Phase Voltage)

$$V_{ab} = \sqrt{3} V_a \angle 30^\circ$$



$$V_{bc} = \sqrt{3} V_b \angle 30^\circ$$

$$V_{ca} = \sqrt{3} V_c \angle 30^\circ$$

$$|V_a| = \frac{|V_{ab}|}{\sqrt{3}}$$

$$|V_b| = \frac{|V_{bc}|}{\sqrt{3}}$$


$$|V_c| = \frac{|V_{ca}|}{\sqrt{3}}$$

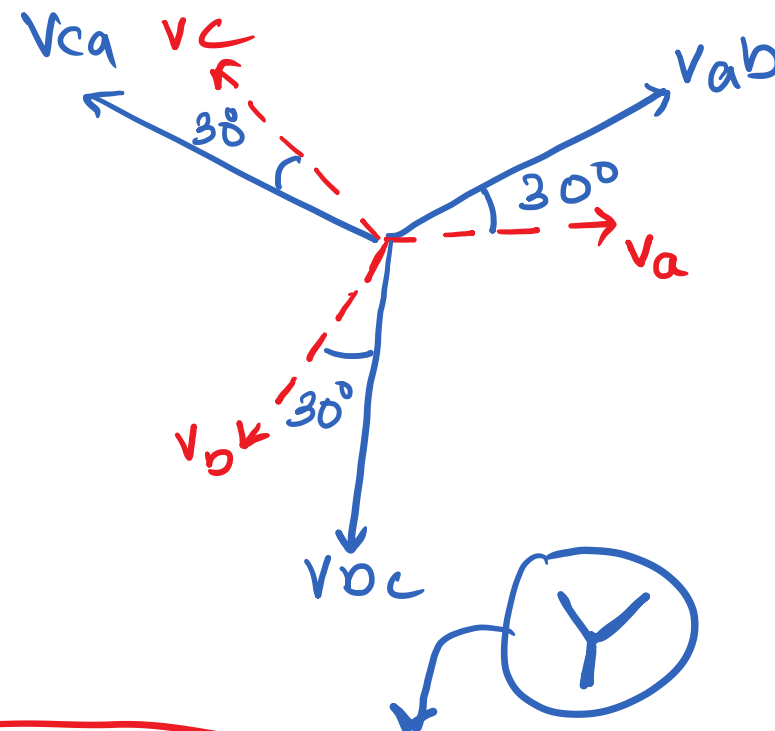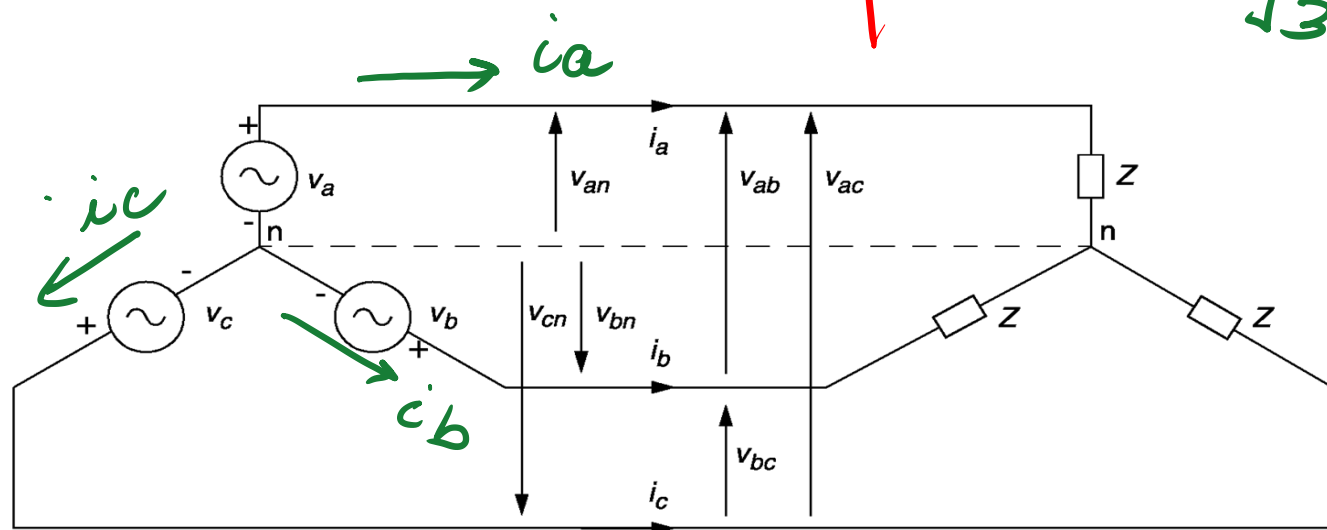


$$V_{\text{phase}} = \frac{V_{\text{line}}}{\sqrt{3}}$$

3-Phase Circuit Connection

Wye Connection

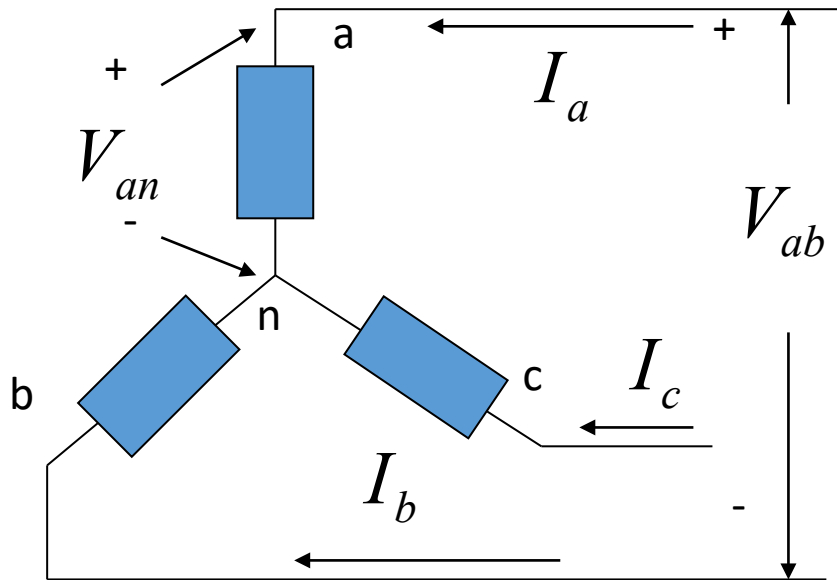

Delta Connection

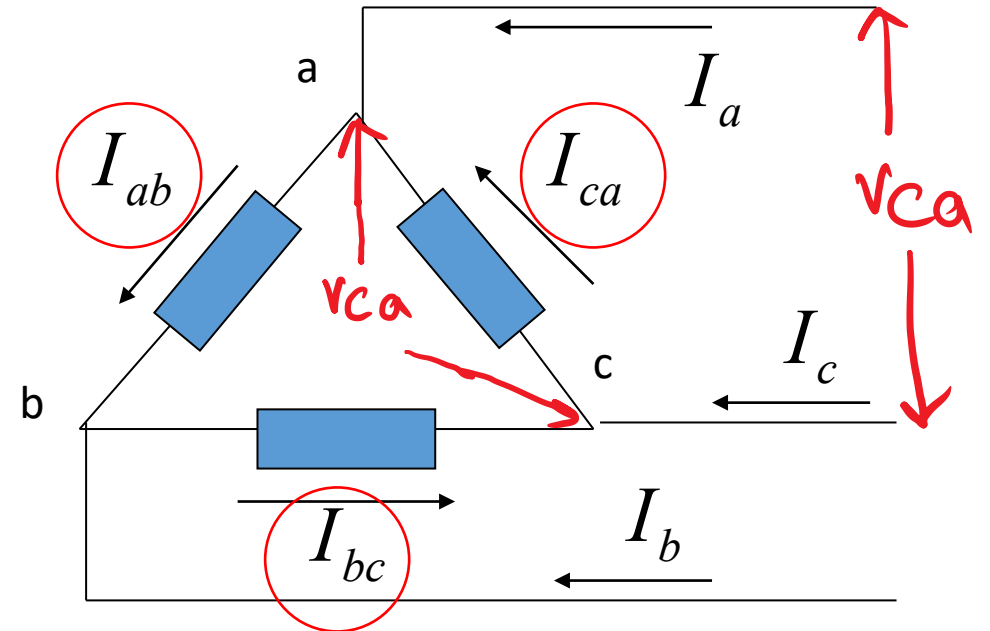

What are these currents?

These two types of connections apply to both three-phase voltage sources and three-phase loads

Delta-Connected Load

$$V_{\text{LINE}} = V_{\text{PHASE}}$$

KCL @ JUNCTION A

$$I_{ab} = I_{ca} + I_a$$



$$\Rightarrow I_a = I_{ab} - I_{ca}$$

$$\begin{aligned} I_a &= I_{ab} + (-I_{ca}) \\ &= \sqrt{3} I_{ab} \angle -30^\circ \end{aligned}$$

$$I_a = \sqrt{3} I_{ab} \angle -30^\circ$$

$$I_b = \sqrt{3} I_{bc} \angle -30^\circ$$
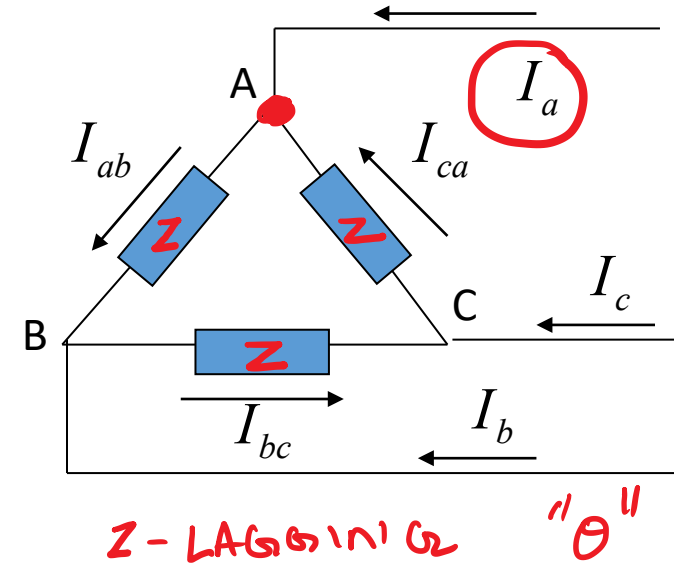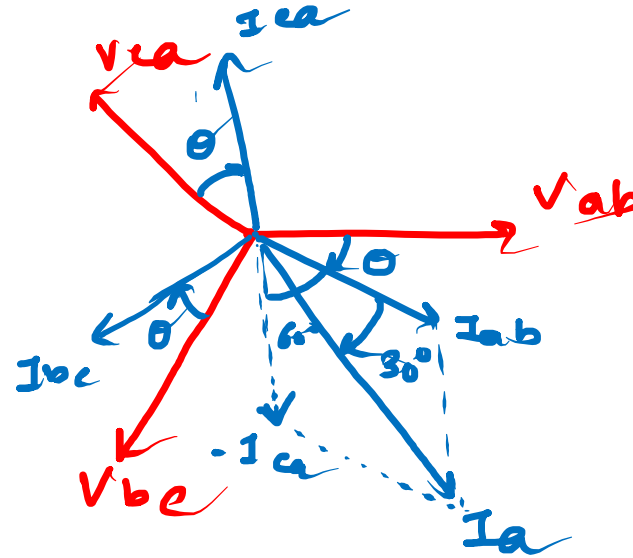
$$I_c = \sqrt{3} I_{ca} \angle -30^\circ$$



\Rightarrow FOR Δ (DELTA)

$$|I_{\text{LINE}}| = \sqrt{3} |I_{\text{PHASE}}|$$

$$\text{OR } I_{\text{PHASE}} = \frac{I_{\text{LINE}}}{\sqrt{3}}$$

Example: For a balanced Y-connected three phase voltage source and Y-connected load system with a line voltage of 440 V and three equal resistive loads of $100\ \Omega$ per phase, assume positive sequence, what will be the magnitudes of
(a) the line-to-neutral voltage, (b) the phase current, (c) the line current?

Balanced Three-Phase Power


$$S_{1\phi} = V I^*$$

- From three phase power,

$$S_{3\phi} = V_{an} I_a^* + V_{bn} I_b^* + V_{cn} I_c^*$$

- When the system is balanced, (assume positive sequence) we can write,
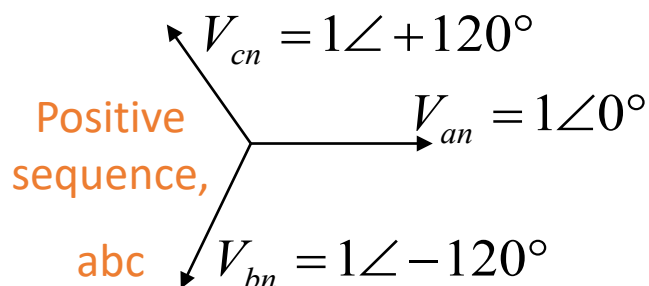
$$S_{3\phi} = V_{an} I_a^* + V_{an} \angle -120^\circ (I_a \angle -120^\circ)^* + V_{an} \angle 120^\circ (I_a \angle 120^\circ)^*$$





$$S_{3\phi} = 3V_{an} I_a^* = 3(P + jQ)$$

$$\Rightarrow P_{3\phi} = 3V_{an} I_a \cos \theta$$

$$Q_{3\phi} = 3V_{an} I_a \sin \theta$$

Delta/Wye Connected 3-Phase Load

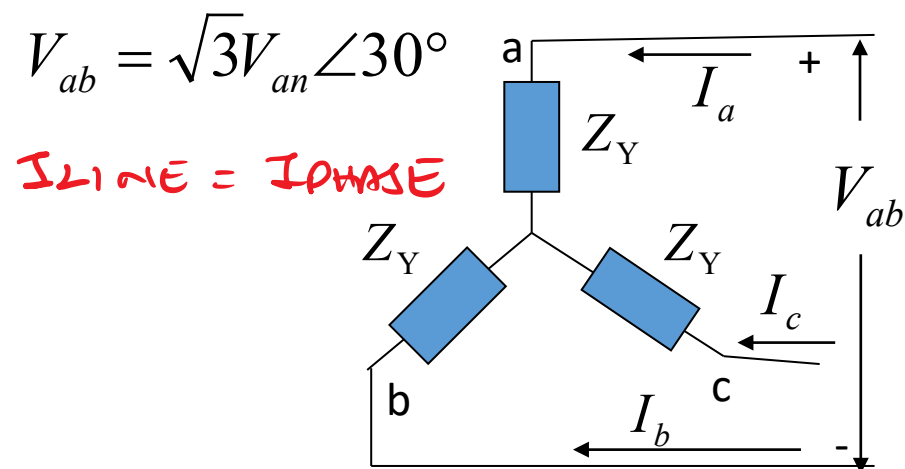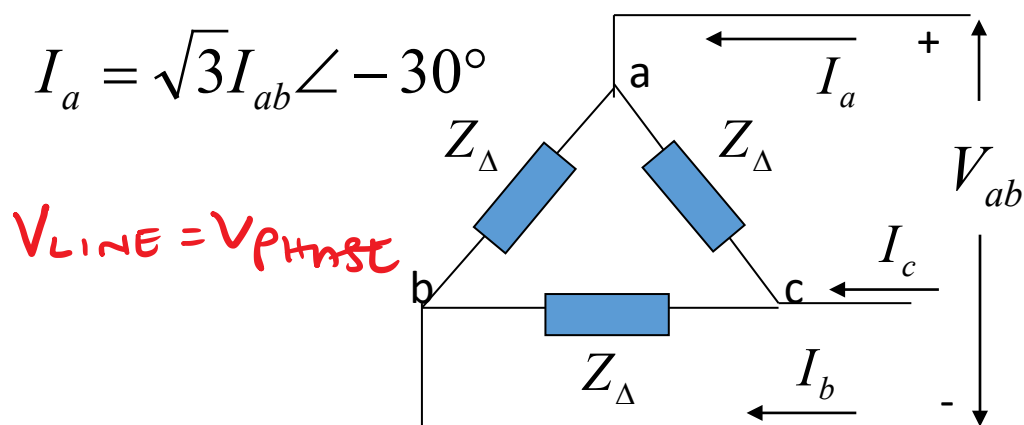

$$\begin{aligned}
 |S_{3\phi}| &= 3|V_{ab}| |I_{ab}| \\
 &= 3|V_{ab}| \frac{|I_a|}{\sqrt{3}} \\
 &= \sqrt{3}|V_{LINE}| |I_{LINE}|
 \end{aligned}$$

$$\begin{aligned}
 S_{3\phi} &= 3|V_{an}| |I_{an}| \\
 &= 3 \frac{|V_{ab}|}{\sqrt{3}} |I_{an}| \\
 &= \sqrt{3}|V_{LINE}| |I_{LINE}|
 \end{aligned}$$





$$|S_{3\phi}| = \sqrt{3} |V_{Line-To-Line}| |I_{Line}|$$

BOTH Δ & γ

Delta-Wye Load Transformation

$$I_{ph} = \frac{I_{LINE}}{\sqrt{3}}$$

$$V_{ph} = V_{LINE}$$

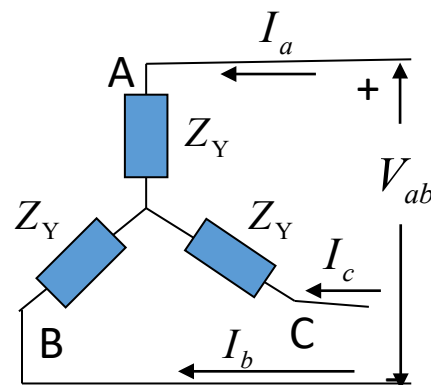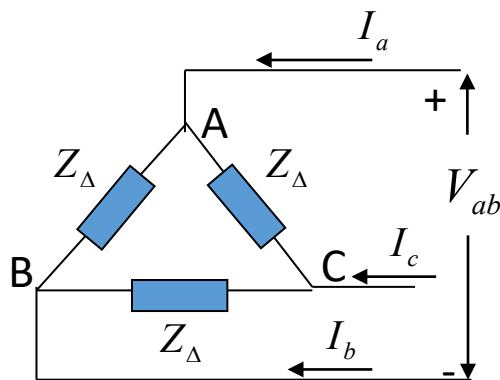

$$V_{ph} = \frac{V_{LINE}}{\sqrt{3}}$$

$$I_{ph} = I_{LINE}$$

$$Z_{\Delta} = \frac{V_{ph}}{I_{ph}} = \frac{V_{AB}}{I_{AB}}$$

$$Z_{\Delta} = \frac{V_{AB}}{I_A / \sqrt{3}} = \frac{\sqrt{3} V_{AB}}{I_A}$$

$$\Rightarrow \frac{V_{AB}}{I_A} = \frac{Z_{\Delta}}{\sqrt{3}} \quad - (1)$$

$$Z_Y = \frac{V_{ph}}{I_{ph}} = \frac{V_{AN}}{I_{AN}}$$

$$Z_Y = \frac{V_{AB} / \sqrt{3}}{I_A} = \frac{V_{AB}}{\sqrt{3} I_A}$$

$$\Rightarrow \frac{V_{AB}}{I_A} = \sqrt{3} Z_Y \quad - (2)$$

① & ②




$$\Rightarrow \frac{Z_{\Delta}}{\sqrt{3}} = \sqrt{3} Z_Y$$

$$\Rightarrow \boxed{Z_{\Delta} = 3 Z_Y}$$

Per Phase Analysis: Assumption

It must be balanced
three-phase circuit


$$I_n = I_a + I_b + I_c = 0$$

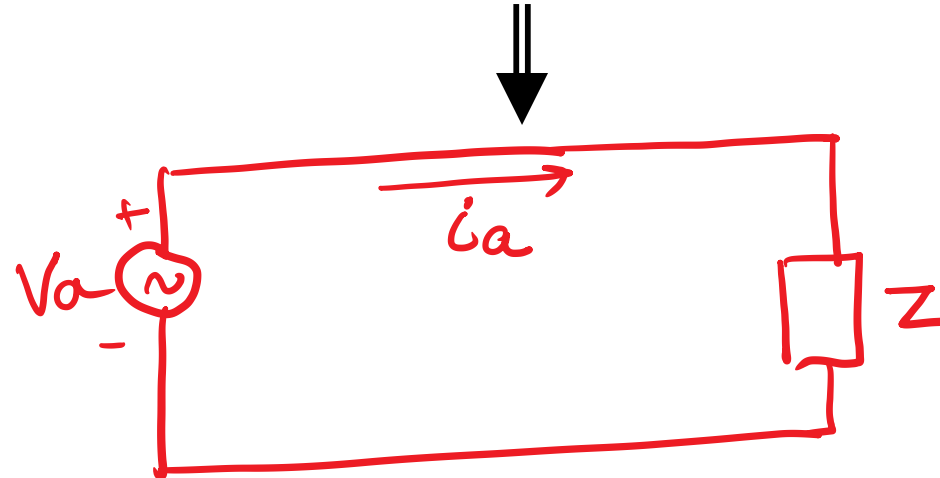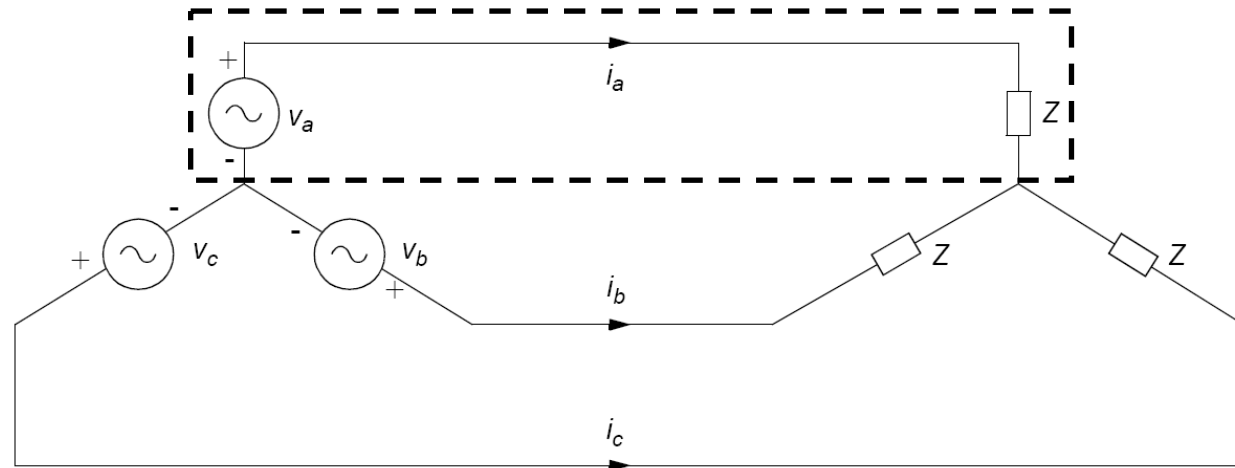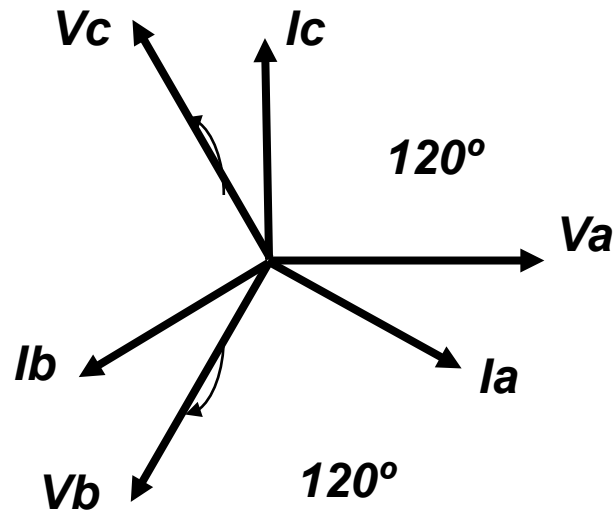

Steps of Per Phase Analysis


- Make sure that the three-phase system is **balanced**.
 - The three-phase sources need to have the same magnitude with 120 degree phase difference.
 - The three-phase impedances must be of the same value (both phase and magnitude).
- **Convert** all **Delta**-connected sources/loads to **Wye**-connected sources/loads.
- Per phase analysis reduce three-phase circuit to **single-phase** circuit. We can apply the same concept used in single-phase.

Single-Line Diagram

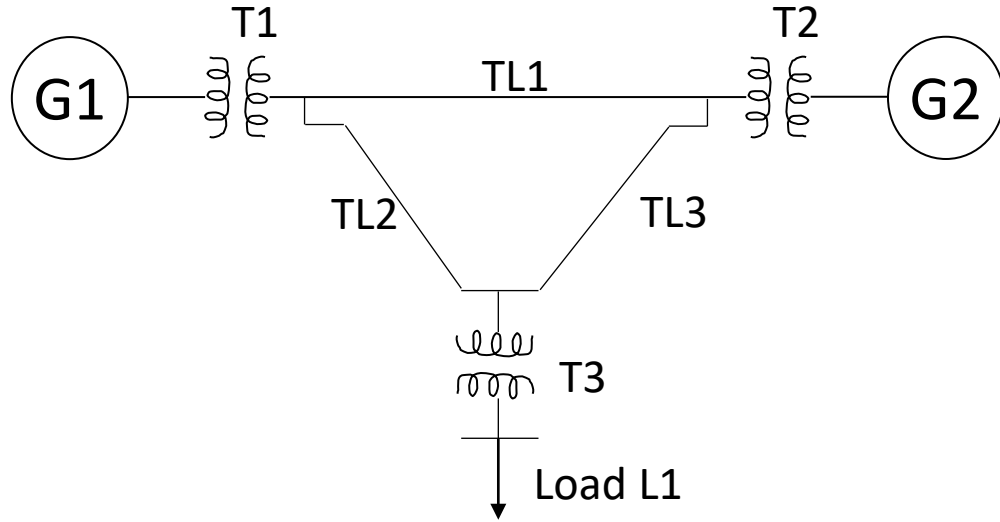

- Show the interconnections of a transmission system
 - Generator
 - Load
 - Transmission line
 - Transformer
- This is a representation of a 3 Φ circuit. Each line represents three conductors in three-phase system.

Example: Given a one-line diagram, If the voltage source is $|V_{line}| = \sqrt{3}$ V. Find, the current magnitude supplied by source, $|I_S|$, and, the current magnitude through a capacitor, $|I_C|$.

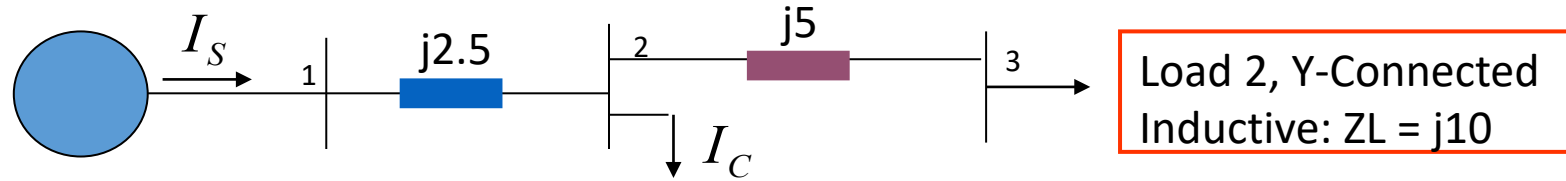


Source, Δ -Connected
Positive sequence.

Load 1, Δ -Connected
Capacitor: $Z_C = -j15$

Step 1: Make sure that the three-phase system is balanced.

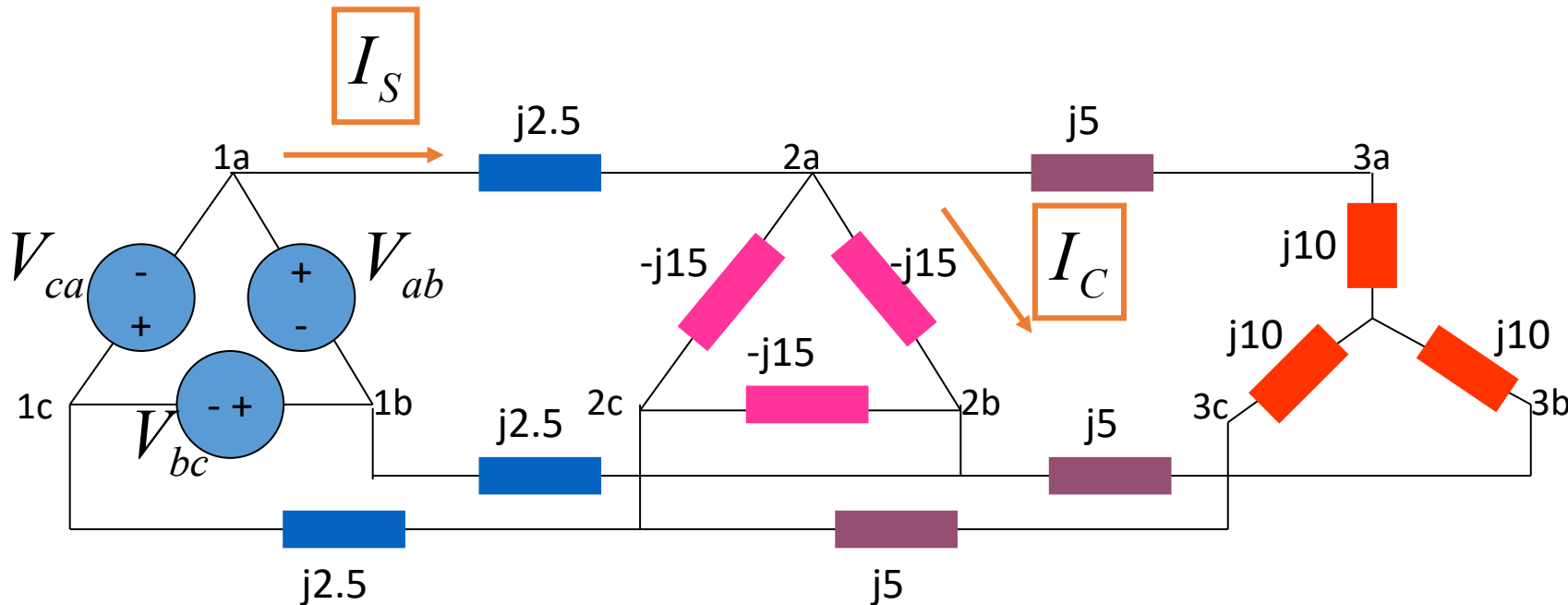
- The three-phase sources need to have the same magnitude with 120 degree phase difference.
- The three-phase impedances must be of the same value (both phase and magnitude).




Step 2: Convert from $\Delta \rightarrow Y$

- Converting the Z_{Δ} to Z_Y : Load 1 $Z_{\Delta} = -j15\Omega \rightarrow Z_Y = \frac{Z_{\Delta}}{3} = \frac{-j15}{3} = -j5\Omega$
- Converting the Voltage Source from $\Delta \rightarrow Y$

Step 3 : Draw the 1-phase Diagram

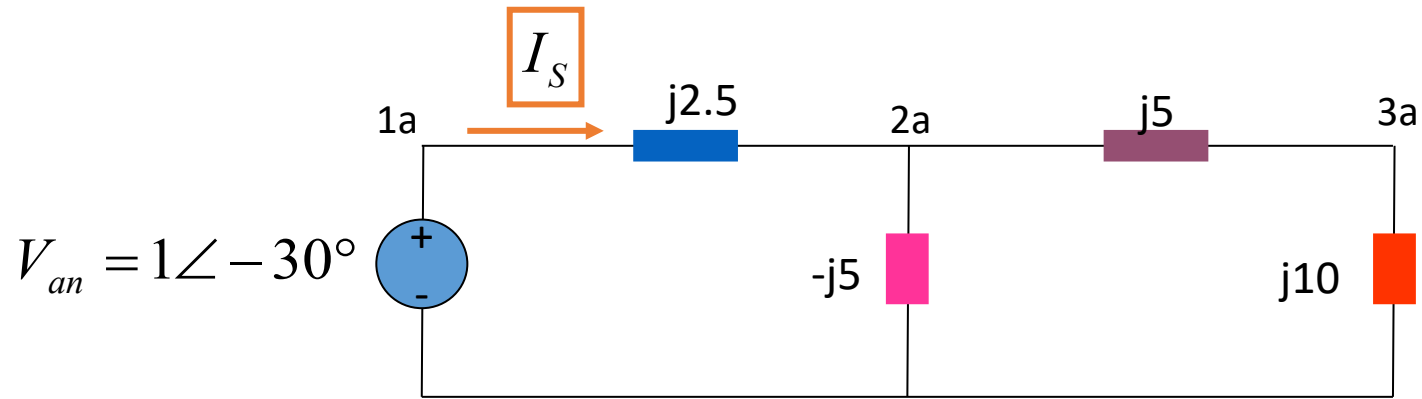

Step 4: Find the capacitor Current I_C

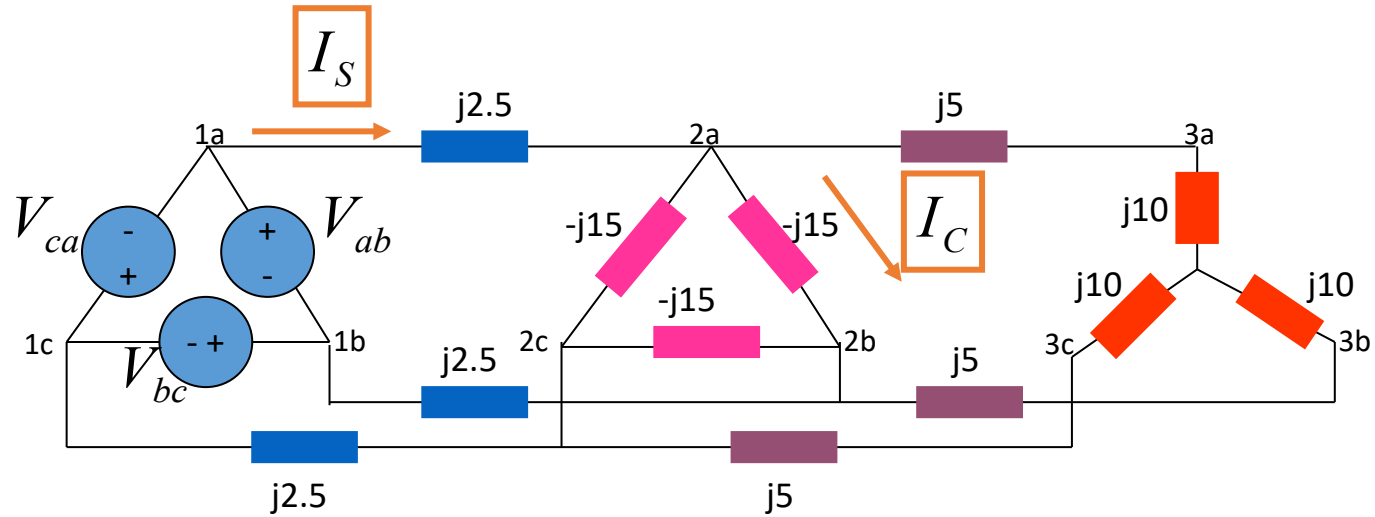



Questions!!!