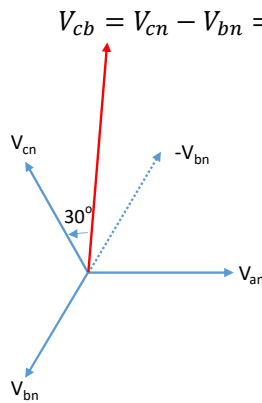


## EE2029 Introduction to Electrical Energy Systems (Solution for Tutorial 3 on Three-Phase Circuit Analysis)

### Solution Q.1

Drawing the phasor diagram for abc phase sequence and showing  $V_{cb}$ .



Given  $V_{cb} = 480 \angle 65^\circ \text{ V}$ , we can get  $V_{cn} = \frac{V_{cb}}{\sqrt{3}} \angle 30^\circ = \frac{480 \angle 65^\circ}{\sqrt{3}} \angle 30^\circ = 277.13 \angle 95^\circ \text{ V}$ .

With load impedance of  $Z_Y = 60 \angle -30^\circ \Omega$ ,

We can get C phase current  $I_c = I_{cn} = \frac{V_{cn}}{Z_Y} = \frac{277.13 \angle 95^\circ}{60 \angle -30^\circ} = 4.62 \angle 125^\circ \text{ A}$

Then we can get the other line currents by adding the phase difference:

$$I_a = I_c \angle -120^\circ = 4.62 \angle 5^\circ \text{ A}; \quad I_b = I_a \angle -120^\circ = 4.62 \angle -115^\circ \text{ A};$$

### Solution Q.2

Line-to-neutral voltage  $V_{LN} = \frac{V_{LL}}{\sqrt{3}} = \frac{500}{\sqrt{3}} = 288.675 \text{ V}$

We can take phase a voltage phasor  $V_{an} = 288.675 \angle 0^\circ \text{ V}$

The loads are given as Wye-connected

a)  $Z_Y = 30 + j0 \Omega$

Phase a current  $I_{an} = \frac{V_{an}}{Z_Y} = \frac{288.675 \angle 0^\circ}{30 + j0} = 9.623 \angle 0^\circ \text{ A}$

$$S_{3\phi} = 3V_{an}I_{an}^* = 3 \times 288.675 \angle 0^\circ \times 9.623 \angle 0^\circ = 8333.76 \angle 0^\circ \text{ VA} = 8333.76 + j0 \text{ VA}$$

Average power  $P_{3\phi} = 8333.76 \text{ W}$

b)  $Z_Y = 30 + j72 \Omega$

Phase a current  $I_{an} = \frac{V_{an}}{Z_Y} = \frac{288.675 \angle 0^\circ}{30 + j72} = 3.701 \angle -67.38^\circ \text{ A}$

$$S_{3\phi} = 3V_{an}I_{an}^* = 3 \times 288.675 \angle 0^\circ \times 3.701 \angle 67.38^\circ = 3205.158 \angle 67.38^\circ = 1232.76 + j2958.6 \text{ VA}$$

Average power  $P_{3\phi} = 1232.76 \text{ W}$

c)  $Z_Y = 30 - j12.5 \Omega$

Phase a current  $I_{an} = \frac{V_{an}}{Z_Y} = \frac{288.675 \angle 0^\circ}{30 - j12.5} = 8.882 \angle 22.62^\circ \text{ A}$

$$S_{3\phi} = 3V_{an}I_{an}^* = 3 \times 288.675 \angle 0^\circ \times 8.882 \angle 22.62^\circ = 7692.034 \angle 22.62^\circ \text{ VA}$$

$$= 7100.33 + j2958.49 \text{ VA}$$

Average power  $P_{3\phi} = 7100.33 \text{ W}$

### Solution Q.3

Line current,  $I_{line} = \frac{100}{|10 - j9|} = 7.43 \text{ A}$

Line-to-neutral voltage at the source,

$$|V_{Line-neutral}| = |I_{line}| \times |Z_{total}| = 7.43 |(2 + j3) + (10 - j9)| = 99.7 \text{ V.}$$

Line voltage at the source,

$$V_{Line-Line} = \sqrt{3} \times |V_{Line-neutral}| = \sqrt{3} \times 99.7 = 173 \text{ V.}$$

### Solution Q.4

We first need to combine the two loads,  $\Delta$  is transformed to Y,

$$Z_Y = \frac{Z_\Delta}{3} = \frac{21 \angle 30^\circ}{3} = 7 \angle 30^\circ \Omega.$$

Now we have two balanced Y connected loads of  $9 \angle -60^\circ \Omega$  and  $7 \angle 30^\circ \Omega$  in parallel.

The total load impedance per phase,  $Z_{Y,total} = \frac{(7 \angle 30^\circ) \times (9 \angle -60^\circ)}{(7 \angle 30^\circ + 9 \angle -60^\circ)} = 5.53 \angle -7.87^\circ \Omega$


The rms line current is found from,

$$I_{line} = \frac{V_{line-to-neutral}}{|Z_Y|} = \frac{V_{line-to-line}}{\sqrt{3}|Z_Y|} = \frac{208}{\sqrt{3} \times 5.53} = 21.7 \text{ A}$$

The total power absorbed by the two loads is ,

$$|P_{3\phi}| = \sqrt{3} |V_{line-to-line}| |I_{line}| \times \text{p.f.} = \sqrt{3} \times 208 \times 21.7 \times \cos(7.87) = 7744.15 \text{ W}$$

### Solution Q.5

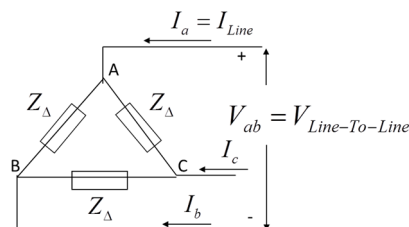

For a balanced three-phase load,  $|P_{3\phi}| = \sqrt{3} |V_{line-to-line}| |I_{line}| \times \text{p.f.}$  By substituting

$|V_{line-to-line}| = 208 \text{ V}$ ,  $P_{3\phi} = 2000 \text{ W}$ ,  $\text{p.f.} = 0.8$  in the above equation, we have  $|I_{line}| = 6.94 \text{ A}$ .

The phase current that pass through an impedance  $z$  can be found from

$$|I_{phase}| = \frac{|I_{line}|}{\sqrt{3}} = 4.01 \text{ A.}$$

Let  $V_{line-to-line} = 208\angle 0^\circ$ , the angle of the phase current can be found from power factor leading.

$$\angle I_{phase} = +\cos^{-1} 0.8 = 36.87^\circ$$

Note that the phase angle is positive because the power factor is leading.

We can find the impedance of  $\Delta$ -connected load as follows.

$$Z_{\Delta} = \frac{V_{ab}}{I_{ab}} = \frac{V_{line-to-line}}{I_{phase}} = \frac{208\angle 0^\circ}{4.01\angle 36.87^\circ} = 51.9\angle -36.87^\circ = 41.44 - j31.08 \Omega$$

### Solution Q.6

#### a) Power triangle for the induction motor.


From  $P_{3\Phi} = |S_{3\Phi}| \times p.f.$ , given that the real power,  $P_{3\Phi} = 400 \text{ kW}$ , we can find,

$$|S_{3\Phi}| = \frac{P_{3\Phi}}{p.f.} = \frac{400}{0.8} = 500 \text{ kVA.}$$

Then, the reactive power can be found from,

$$Q_{3\Phi} = |S_{3\Phi}| \times \sin(\cos^{-1}(p.f.)) = 500 \times \sin(\cos^{-1} 0.8) = 300 \text{ kVAR.}$$

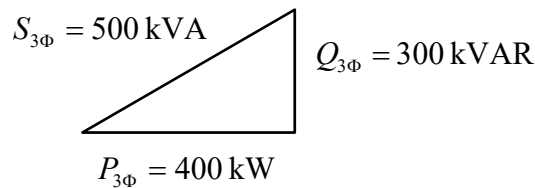Since the power factor is *lagging*, this reactive power is *absorbed* by the induction motor. The power triangle is given below.



#### Power triangle for the synchronous motor.


$$S_{3\Phi} = 150 \text{ kVA}$$

$$P_{3\Phi} = |S_{3\Phi}| \times p.f. = 150 \times 0.9 = 135 \text{ kW.}$$

Since the power factor is *leading*, this reactive power is *injected* by the synchronous motor.

$$Q_{3\Phi} = |S_{3\Phi}| \times \sin(\cos^{-1}(p.f.)) = 150 \times \sin(-\cos^{-1} 0.9) = -65.4 \text{ kVAR.}$$

$$P_{3\Phi} = 135 \text{ kW}$$

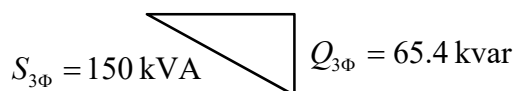

#### Power triangle for the combined-motor load.


$$P_{3\Phi} = 400 + 135 = 535 \text{ kW.}$$

$$Q_{3\Phi} = 300 - 65.4 = 234.6 \text{ kVAR}$$

Since the reactive power is positive, this reactive power is *absorbed* by the combined-motor load.

The magnitude of apparent power is found below.

$$S_{3\Phi} = \sqrt{|P_{3\Phi}|^2 + |Q_{3\Phi}|^2} = 584.2 \text{ kVA.}$$

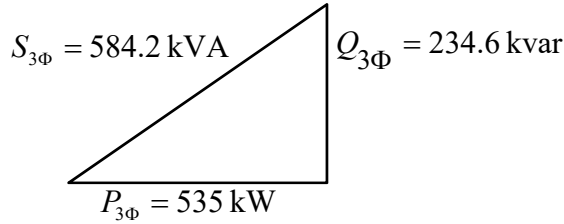

- b) Power factor of the combined-motor load,

$$p.f. = \frac{P_{3\Phi}}{|S_{3\Phi}|} = 0.916$$

Since the load absorbs reactive power, the power factor is 0.916 lagging.

- c) From  $|S_{3\Phi}| = \sqrt{3}|V_{line-to-line}||I_{line}|$ , we can find the line current below.

$$|I_{line}| = \frac{|S_{3\Phi}|}{\sqrt{3}|V_{line-to-line}|} = \frac{584.2 \times 10^3}{\sqrt{3} \times 4160} = 81.1 \text{ A}$$

- d) To make the source power factor unity, the reactive power supplied by the capacitor bank,  $Q_{c,3\Phi} = -234.6 \text{ kVAR}$ .

For a delta connected capacitor bank, the voltage applied to the capacitor at each phase is the line-to-line voltage.

$$Q_{c,1\Phi} = \frac{Q_{c,3\Phi}}{3} = -78.2 \text{ kVAR}$$

The capacitive reactance at each phase,  $X_{c,1\Phi}$ , can be found from  $Q_{c,1\Phi} = \frac{|V_{line-to-line}|^2}{X_{c,1\Phi}}$ .

We have,

$$X_{c,1\Phi} = \frac{|V_{line-to-line}|^2}{Q_{c,1\Phi}} = \frac{4160^2}{-78.2 \times 10^3} = -221.3 \Omega.$$

The capacitive reactance is then  $-j221.3 \Omega$ .

- e) With the capacitor bank installed, power factor=1.

Active power delivered by the source,  $P_{3\Phi} = \sqrt{3}|V_{line-to-line}||I_{line}| \times p.f. = 535 \text{ kW}$ .

With the capacitor bank installed, power factor=1. The line current magnitude is found below.

$$|I_{line}| = \frac{|P_{3\Phi}|}{\sqrt{3}|V_{line-to-line}| \times p.f.} = \frac{535 \times 10^3}{\sqrt{3} \times 4160 \times 1} = 74.3 \text{ A}$$

Note that once the power factor is adjusted to 1, the line current magnitude is reduced from 81.1 A to 74.3 A. This helps to reduce the power losses in the transmission lines.