

NATIONAL UNIVERSITY OF SINGAPORE

Department of Electrical Engineering

EE2029 ELECTRICAL ENERGY SYSTEMS

(Tutorial: Per Unit Analysis)

1. A single-phase transformer is rated 110/440V, 2.5 kVA. Leakage reactance measured from the low voltage side is 0.06Ω . What is the base impedance in Ohm at the low-voltage side of the transformer? Determine leakage reactance in per unit.

(Answer: 4.84Ω , 0.0124 per unit)

2. The reactance of a single-phase generator designated X'' is given as 0.25 per unit based on the generator's name plate rating of 18 kV, 500 MVA. What is the reactance value in ohm? If the new base for calculations is 20 kV, 100 MVA, find X'' on the new base.

(Answer: 0.162Ω , 0.0405 per unit)

3. Three parts of a single-phase electric system are designated A, B and C and are connected to each other through transformers, as shown in Fig. 2. The transformers are rated as follows. Note that the transformer reactances are given in percent; for example, 10% = 0.1 p.u.

A-B 10,000 kVA, 13.8/138 kV, leakage reactance 10%

B-C 10,000 kVA, 138/69 kV, leakage reactance 8%

If the base in circuit B is chosen as 10,000 kVA, 138 kV, find the per unit reactance of both transformers and per unit impedance of the 300Ω resistive load in circuit C referred to circuits C, B and A. Draw the impedance diagram neglecting magnetizing current, transformer resistance and line impedance.

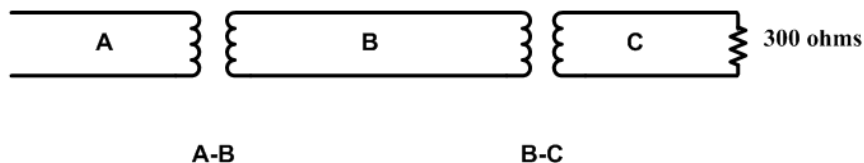


Fig. 2

(Answer: j0.1 per unit, j0.08 per unit, 0.63 per unit)

4. Consider a system with the single line diagram shown in Fig. 3. The three phase transformer name plate ratings are listed. The transformer reactances are given in percent; 10% = 0.1 p.u. The transmission line impedance Z_L is $10 + j100$ ohms and load impedance Z_{load} is 440 ohms. The generator has a terminal voltage (magnitude) of 13.2 kV (line-line). Find the power delivered to the load, the power supplied by the generator and the efficiency.

Figure 1: Single-line diagram of the power system. The diagram shows a 13.2 kV source connected to a 5MVA transformer (K-L) with 10% reactance. The secondary of this transformer is connected to a 10MVA transformer (M-N) with 8% reactance. The load is $Z_L = 10 + j100$. The voltage levels are 13.2 Δ - 132 Y kV for the first transformer and 138 Y - 69 Δ kV for the second transformer. The current I_2 is shown flowing from the 5MVA transformer towards the 10MVA transformer.

(Answer: 8.78 MW, 8.83 MW, 99.4%)