

EE2029: Introduction to Electrical Energy Systems

Renewable Energy Integration

Lecturer : Dr. Sangit Sasidhar (elesang)
Department of Electrical and Computer Engineering







Learning Outcomes

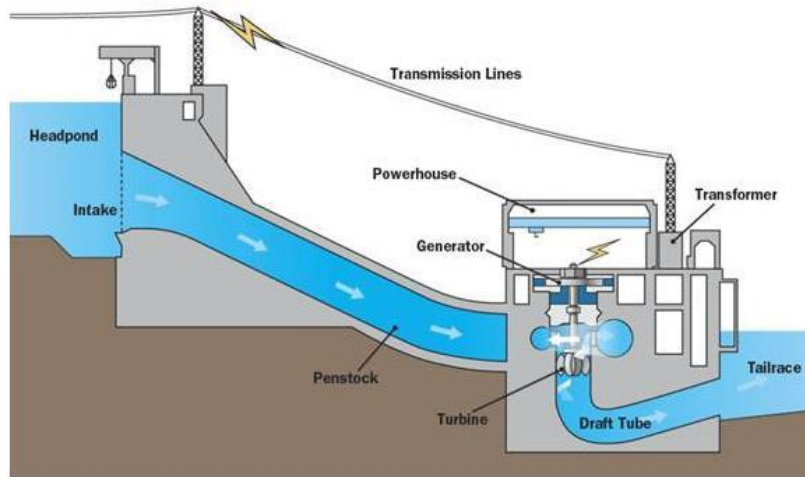- Explain the motivations for Renewable energy
- Describe Solar and Wind energy systems





Renewable energy

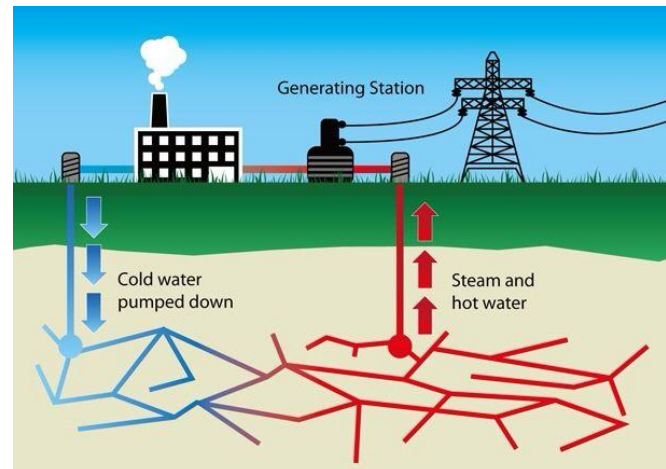

Motivations for Renewable Energy

Fossil Fuels



Energy
Efficiency




Off Grid
Systems




How to make places more energy efficient?




Solar Energy

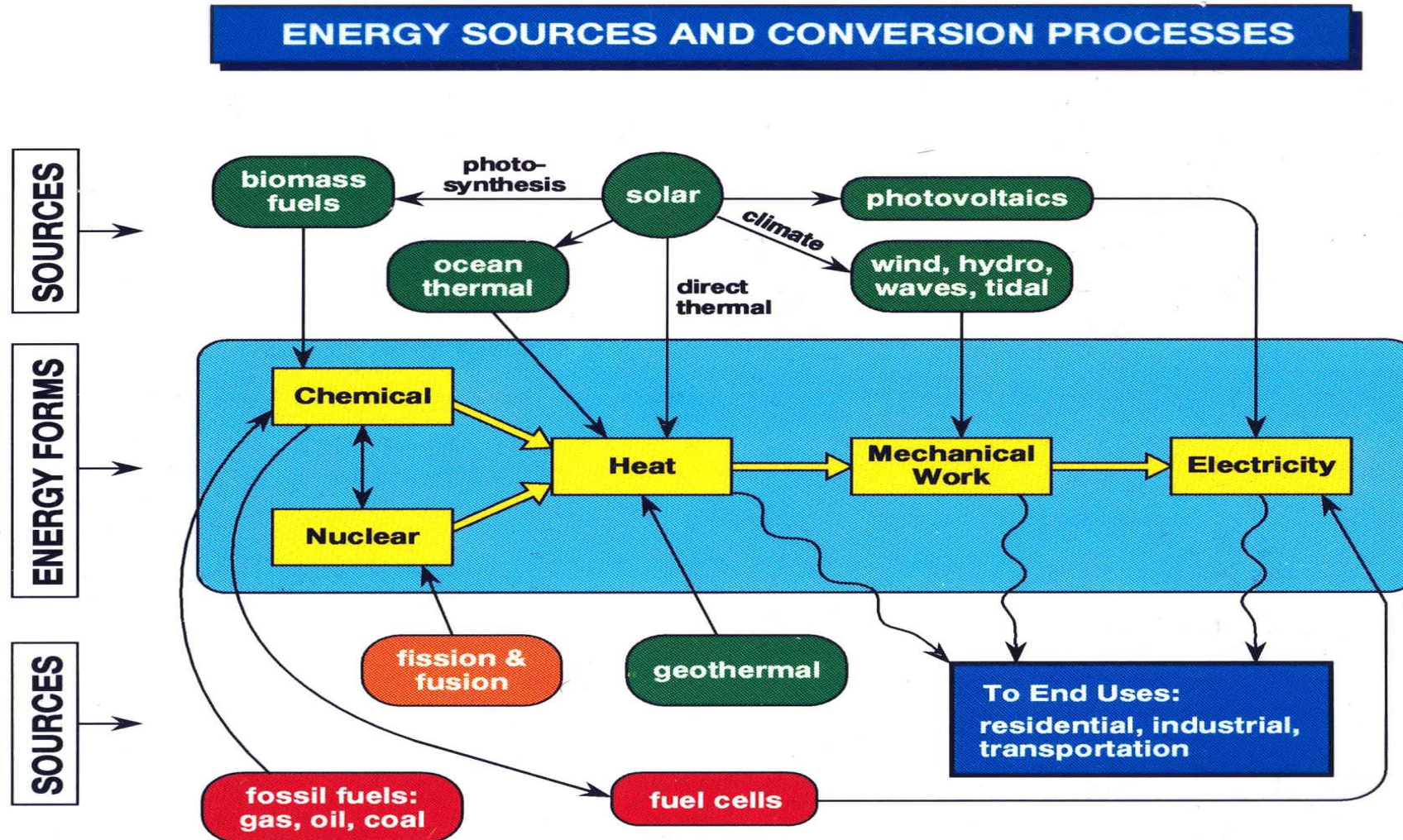

Solar Irradiation of the World

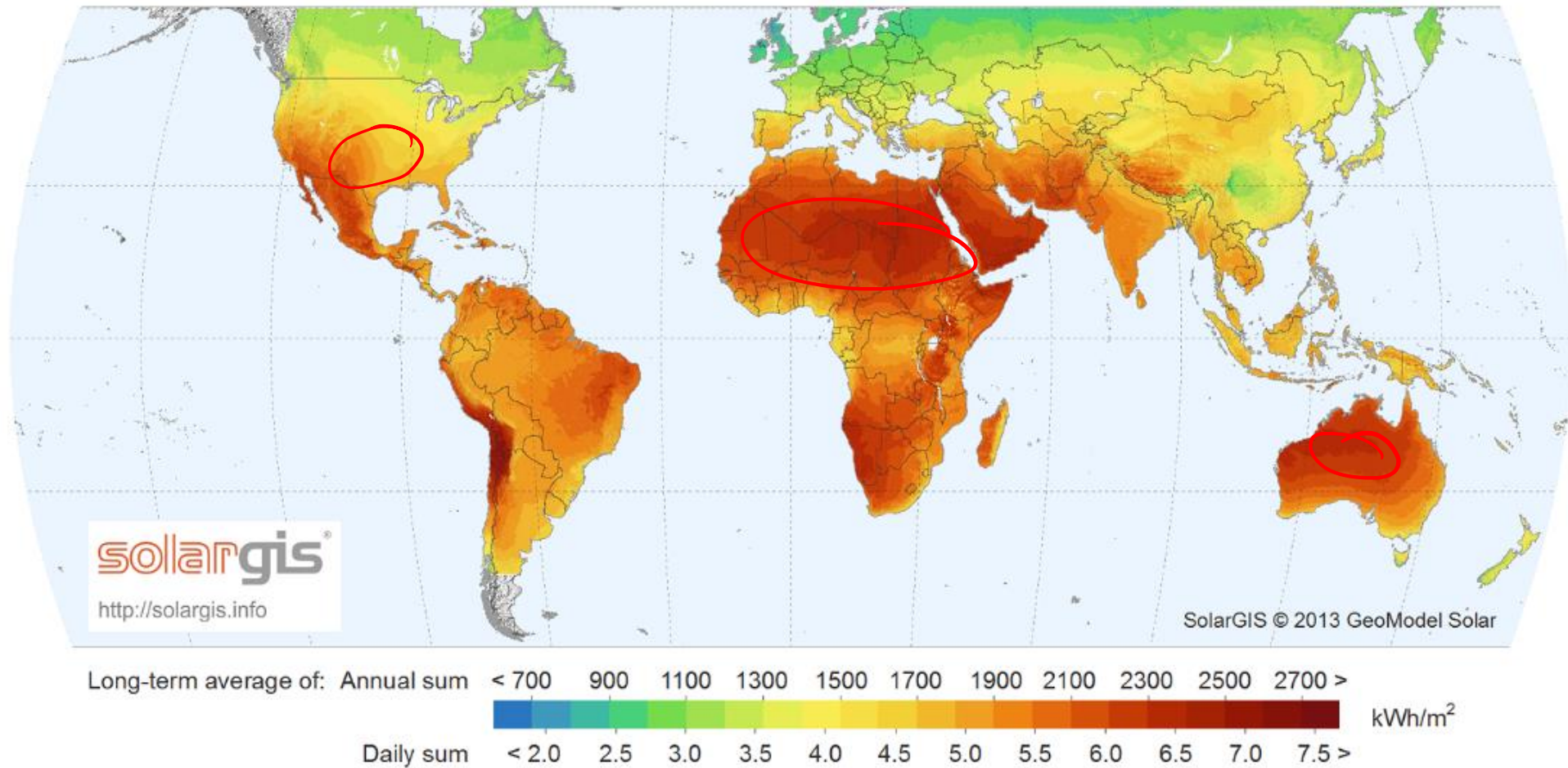

Generating Electricity from the Sun

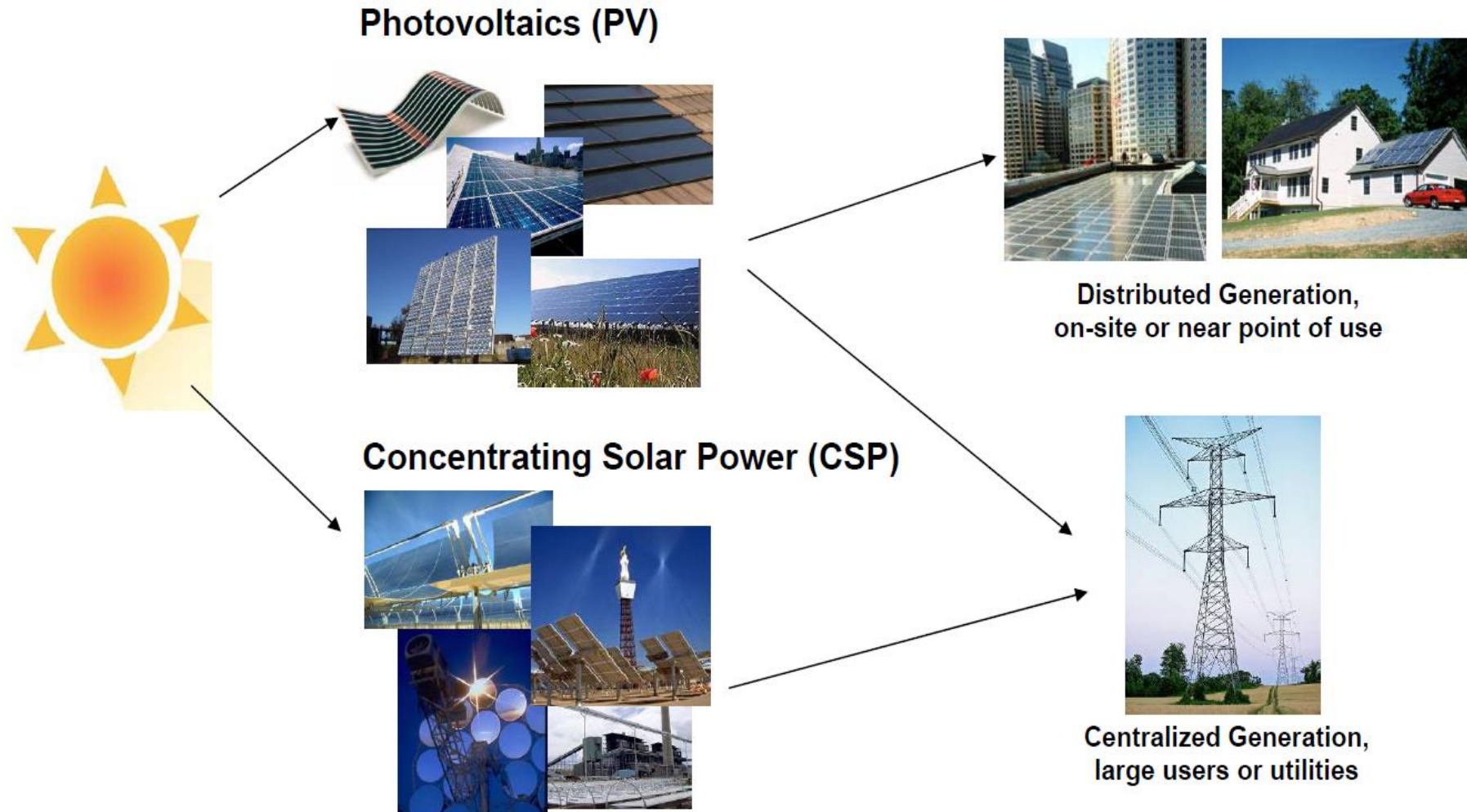

Solar Thermal Technologies

Kramer Junction, CA
5 x 33MW
1985
 $\eta = 15\%$



Parabolic Trough

Solar Two
Barstow, CA
10 MW
1995-1999
 $\eta = 15\%$



Solar Tower

Bakersfield, CA
5MW
2008
 $\eta = 20\%$



Fresnel Reflector

- Solar thermal systems capture and concentrate high-intensity sunlight focused onto working fluids

SNL Solar Stirling
25 kW
2005
 $\eta = 30\%$




Solar Dish



Solar PV Cell

- Photons in sunlight hit the solar panel and are absorbed by semiconducting materials, such as silicon
- Electrons (negatively charged) are knocked loose from their atoms, allowing them to flow through the material to produce electricity. Due to the **special composition** of solar cells, the electrons are only allowed to move in a single direction
- An array of solar cells converts solar energy into a usable amount of direct current (DC) electricity

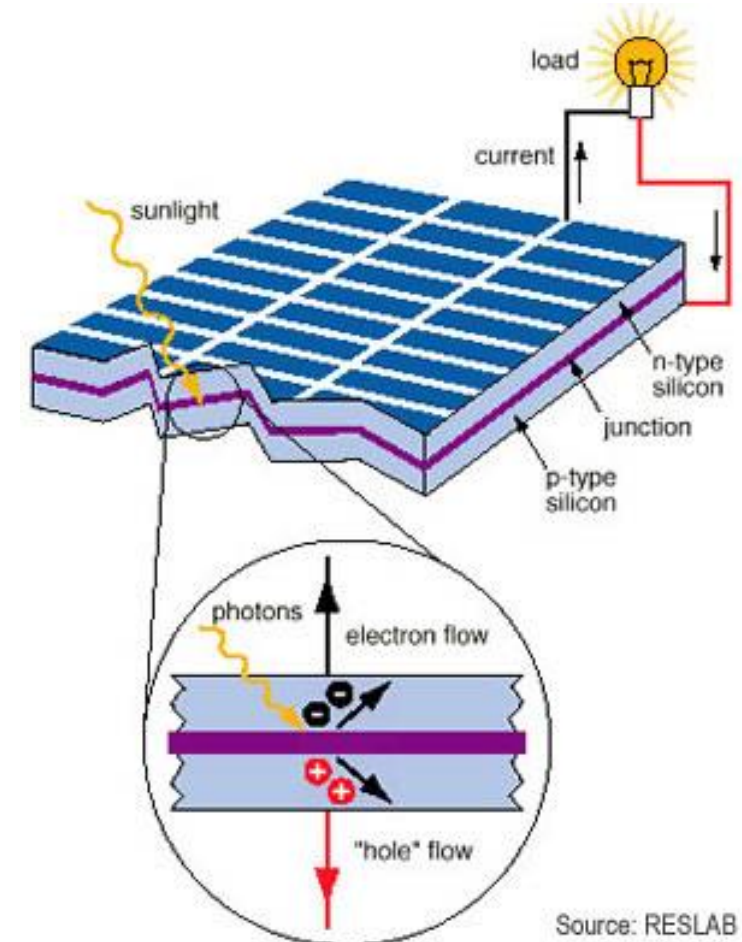


Source: RESLAB



Wind Energy

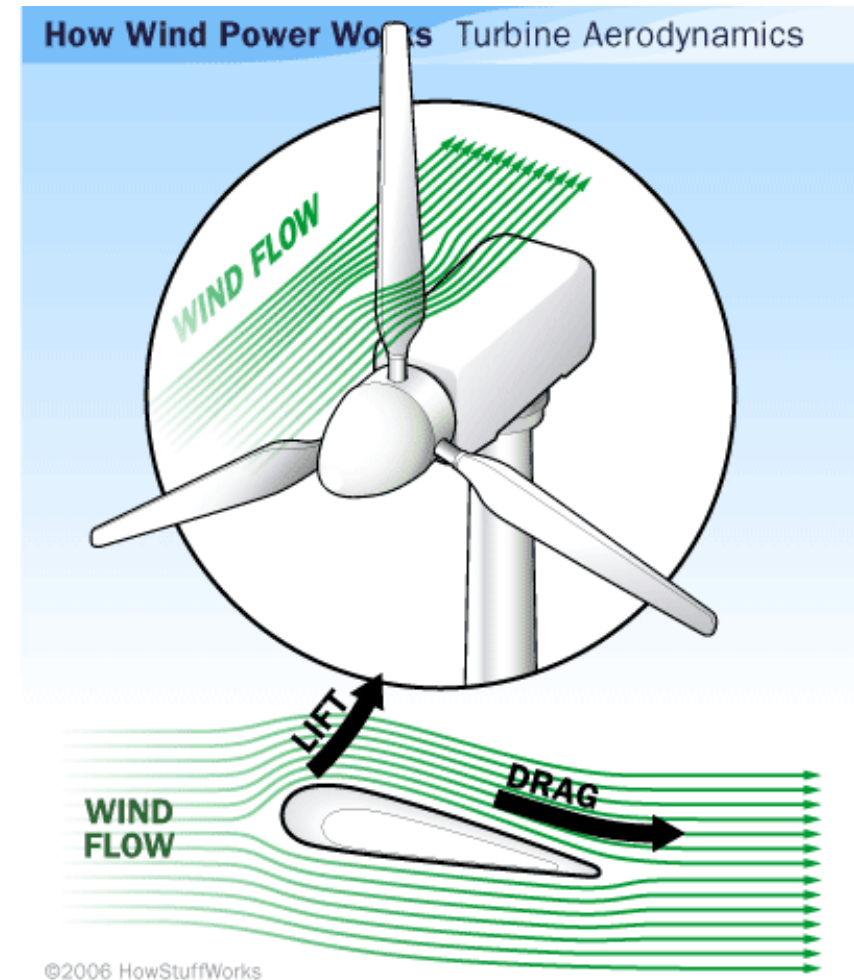- A wind turbine extracts energy from moving air by slowing the wind down, and transferring this energy into a spinning shaft, which usually turns a generator to produce electricity.
- The power in the wind that's available for harvest depends on both the wind speed and the area that's swept by the turbine blades.



Types of Wind Turbines

- Two main types of turbines: Horizontal axis and Vertical axis.
- HAWT: It is possible to catch more wind and so the power output can be higher than that of vertical axis, but the tower is higher and more blade design parameters have to be defined.
- VAWT: No yaw system is required and it is easier to design. Maintenance is easier in vertical axis turbine whereas horizontal axis turbine offers better performance.




Horizontal axis wind
Turbine (HAWT)



Vertical axis wind
Turbine (VAWT)



Power In The Wind

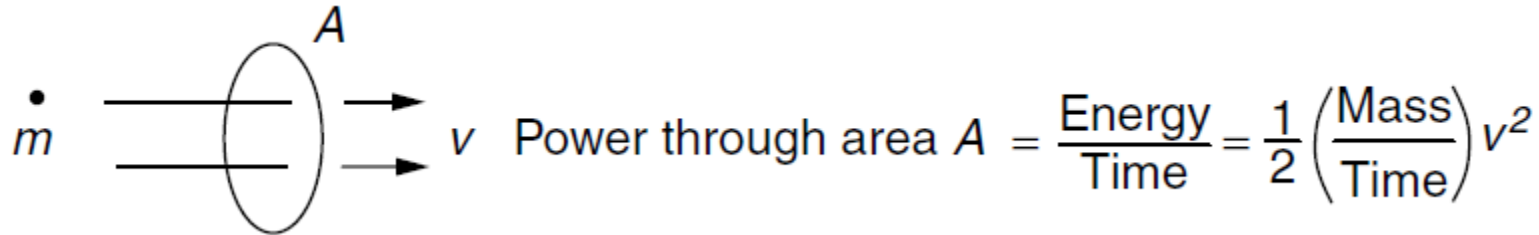

- The mass flow rate $\dot{m} = \left(\frac{\text{Mass}}{\text{Time}} \right)$, through area A , is the product of air density ρ , speed v , and cross-sectional area A :

$$P_w = \frac{1}{2} \rho A v^3$$

P_w is the power in the wind (watts)
 ρ is the air density (kg/m^3)
 A is the cross-sectional area
 v = windspeed normal to A (m/s)


- Specific Power in the Wind is P_w per unit area or $\frac{P_w}{A} = \frac{1}{2} \rho v^3$




Renewable Energy and the Grid





Wind Energy

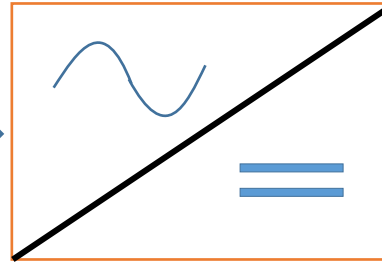



AC – DC Rectifier

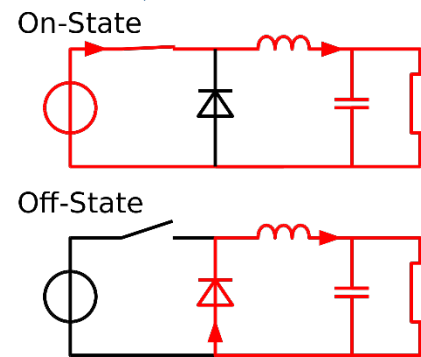

DC - DC Converter

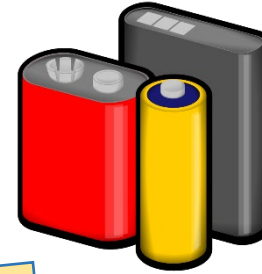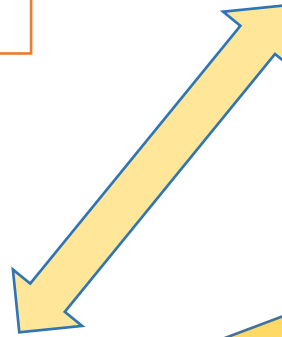



Energy Storage Systems

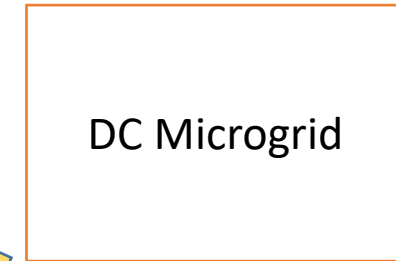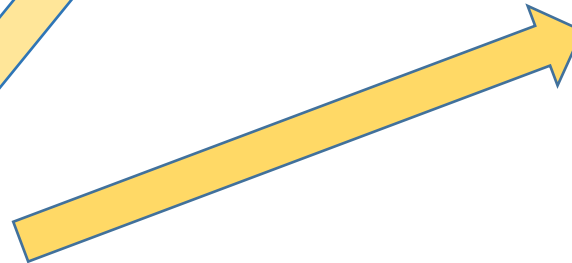

DC Microgrid



Solar Energy

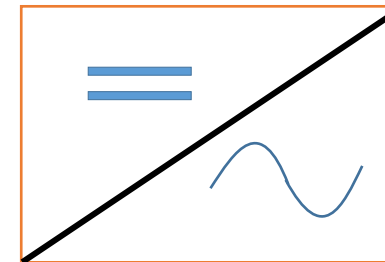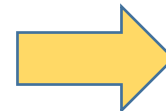


DC – AC Invertor




AC Power Grid

Renewable Energy and the Grid

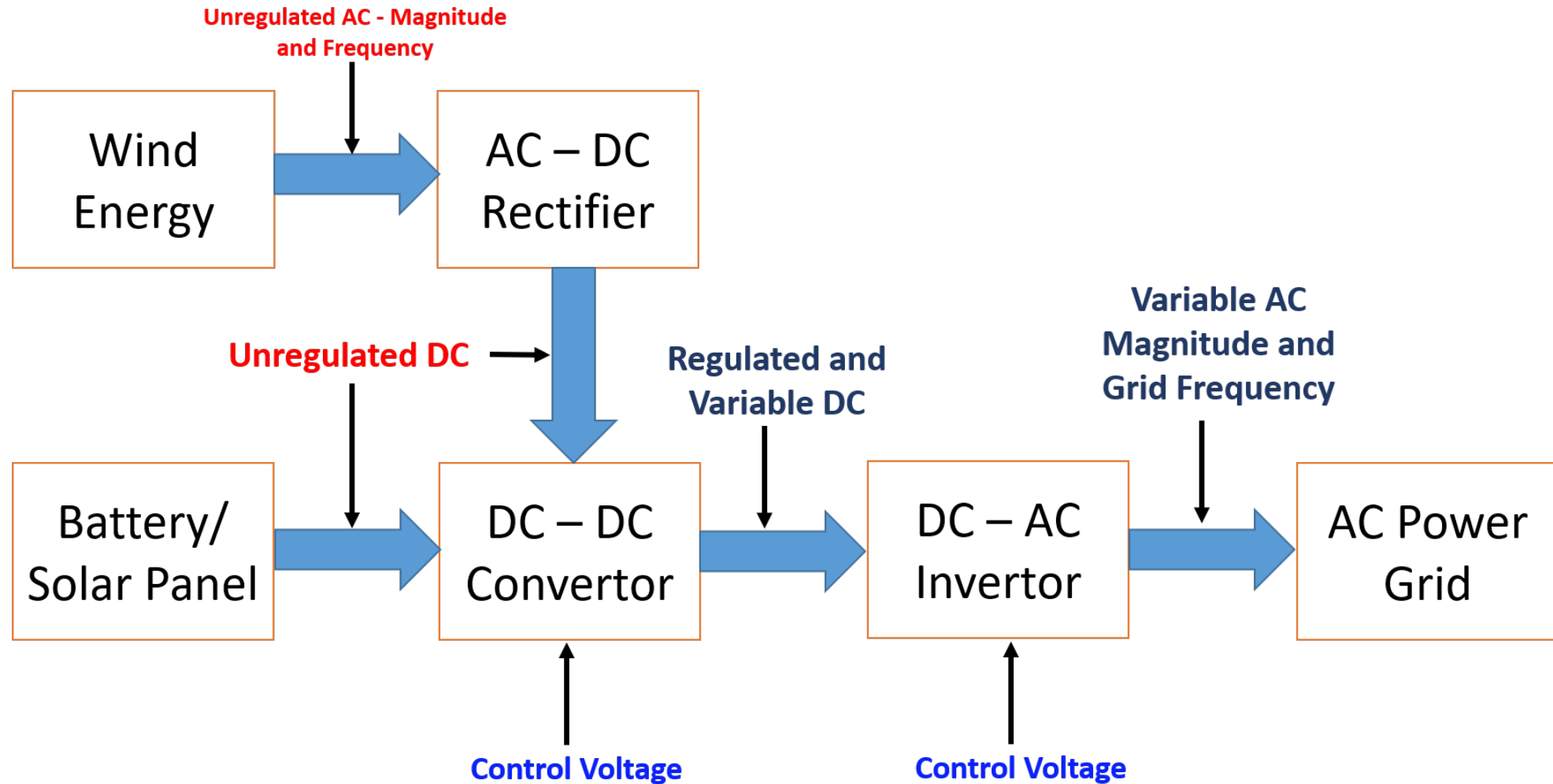


Power Semiconductor Switches

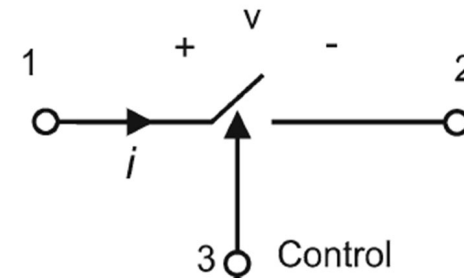
- Power semiconductor devices can be used as electronic switches capable of handling high voltage and current operations at high frequency
- An ideal power electronic switch can be represented as a three terminals device
- The ideal switch has
 - zero-voltage drop,
 - zero-leakage current, and
 - instantaneous transitions
- Diode is an uncontrolled switch
- Transistors are controlled switches




• Diode

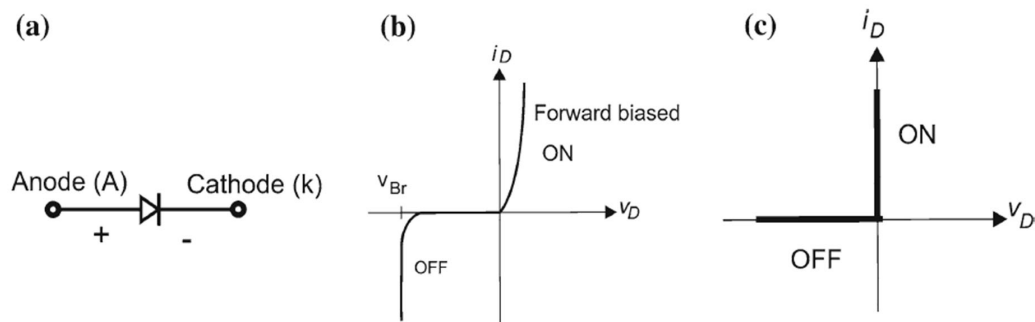

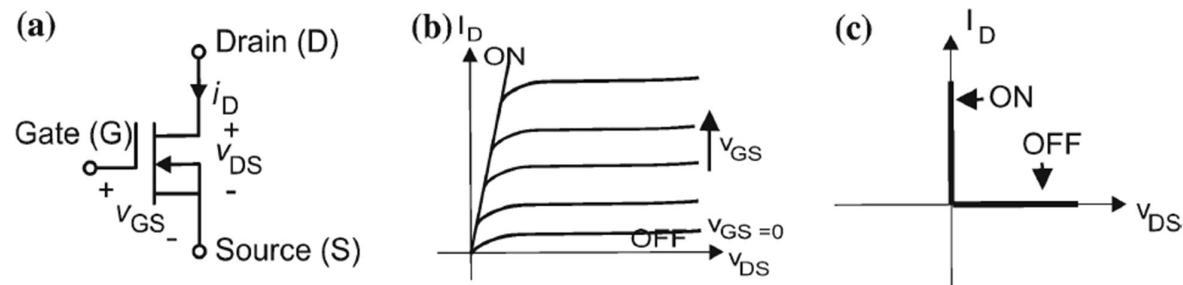
• Metal Oxide Semiconductor Field Effect Transistor (MOSFET)



• Bipolar Junction Transistor (BJT)

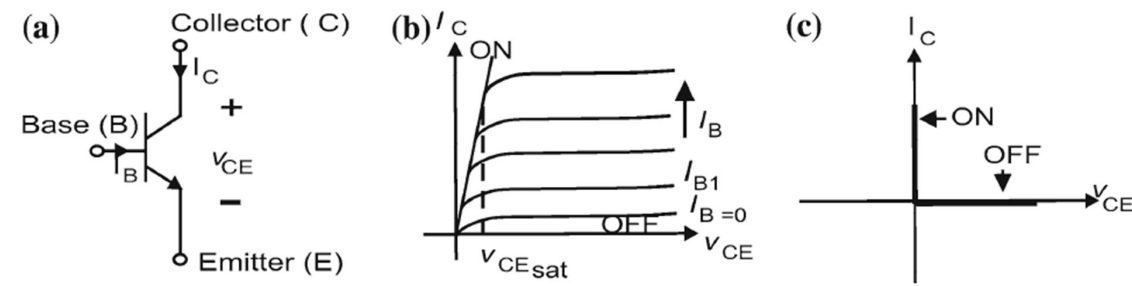

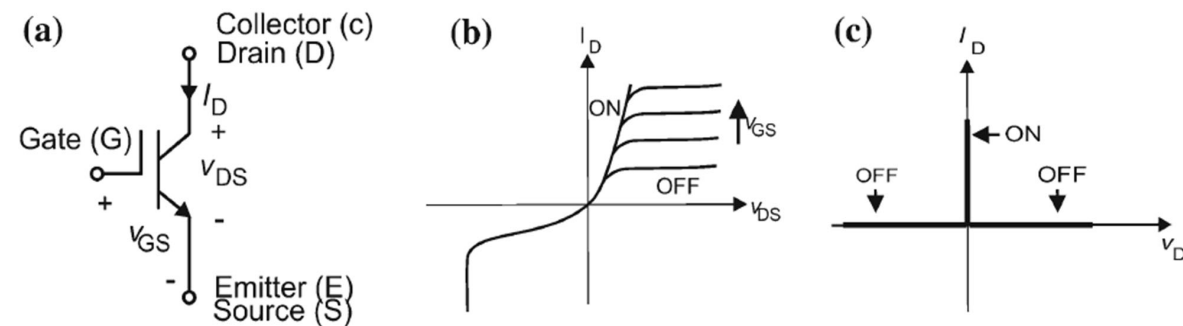
• Insulated Gate Bipolar Transistor (IGBT)




a) Symbol; b) i-v characteristics; c) idealized characteristics



AC-DC Rectifier

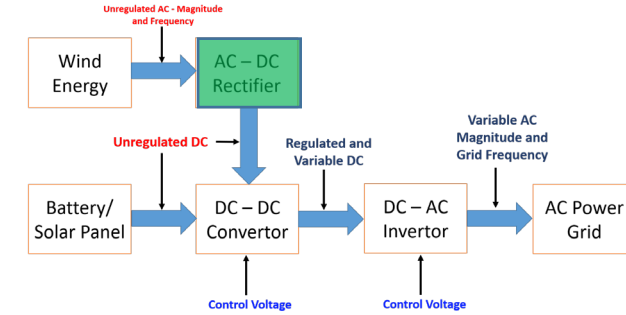


• Rectifier without capacitor

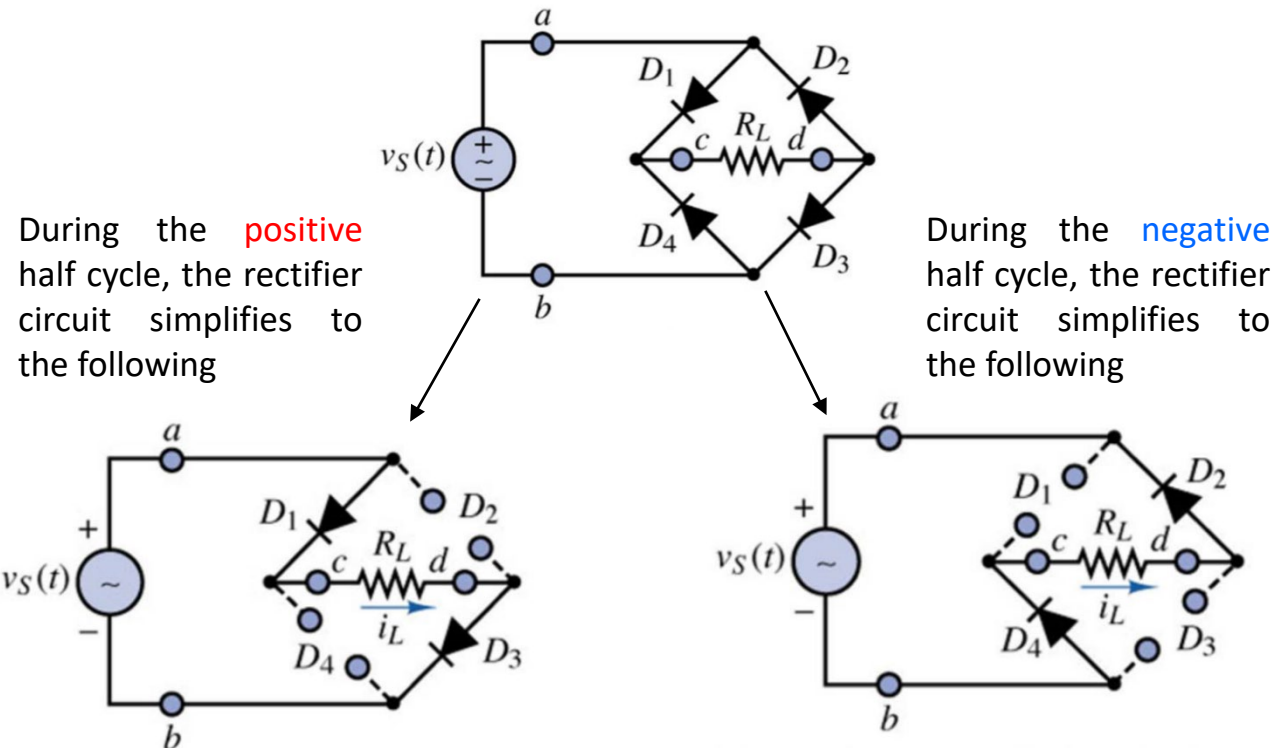

$$V_{avg} = \frac{1}{\pi} \int_0^{\pi} V \sin \omega t d\omega t = \frac{2V}{\pi}$$

• Rectifier with filter capacitor

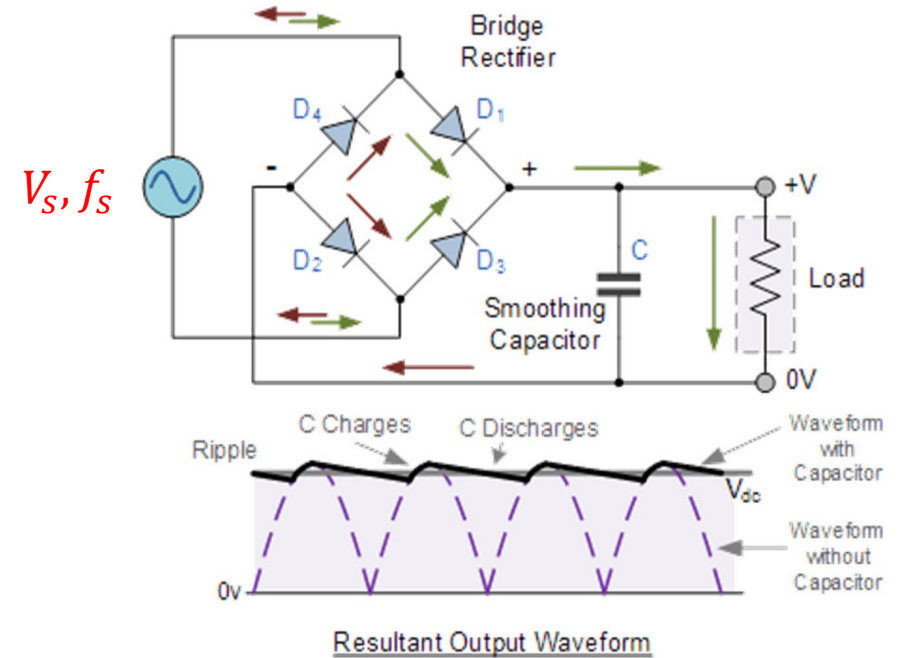

$$\Delta V_{ripple} = \frac{V_{load}}{R_{load}} \cdot \frac{1}{f_s} \cdot \frac{1}{C}$$





Example: The AC-DC rectifier circuit needs to deliver a current of 0.2 A to a load with an average voltage of 15 V. The AC source has a frequency of 50 Hz. The peak-to-peak voltage ripple is to be less than 0.5 V. Assume the diodes are ideal with no voltage drop. Find the minimum value of the filter capacitor needed.






DC-DC Convertors

- Buck Convertor

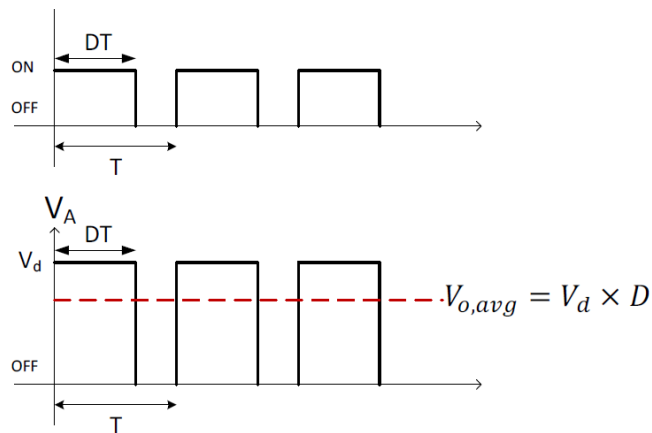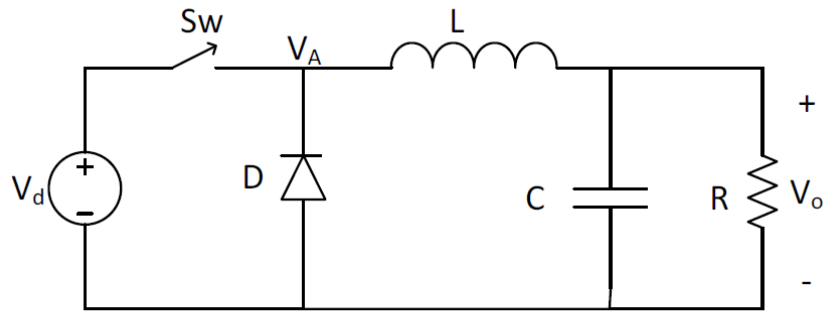


- Boost Convertors

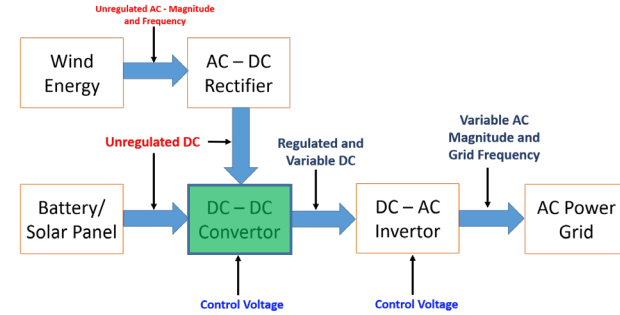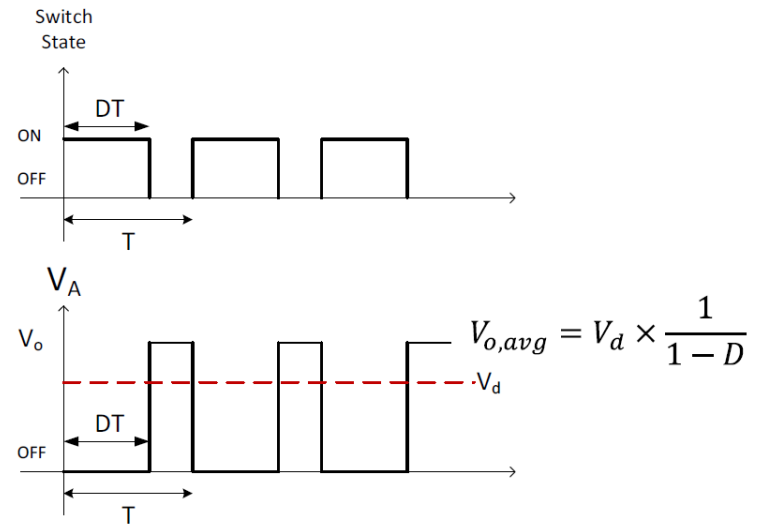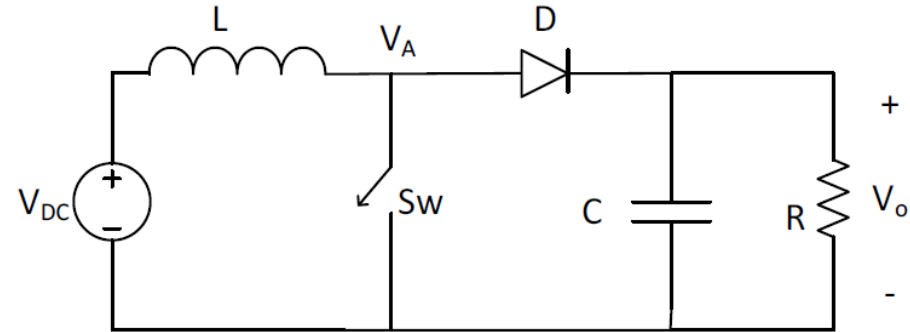


DC-DC Convertor

- DC Voltage from Battery/ Solar Panel

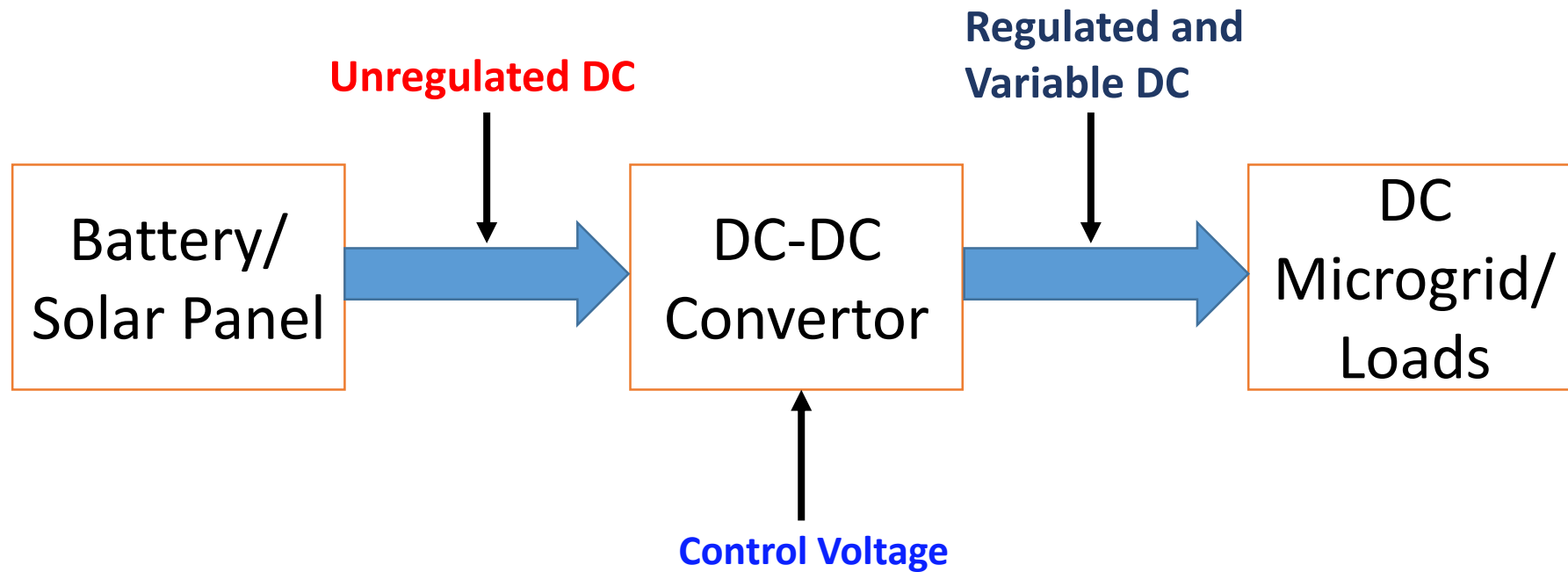

DC-DC Buck Converter

- **Duty Cycle**

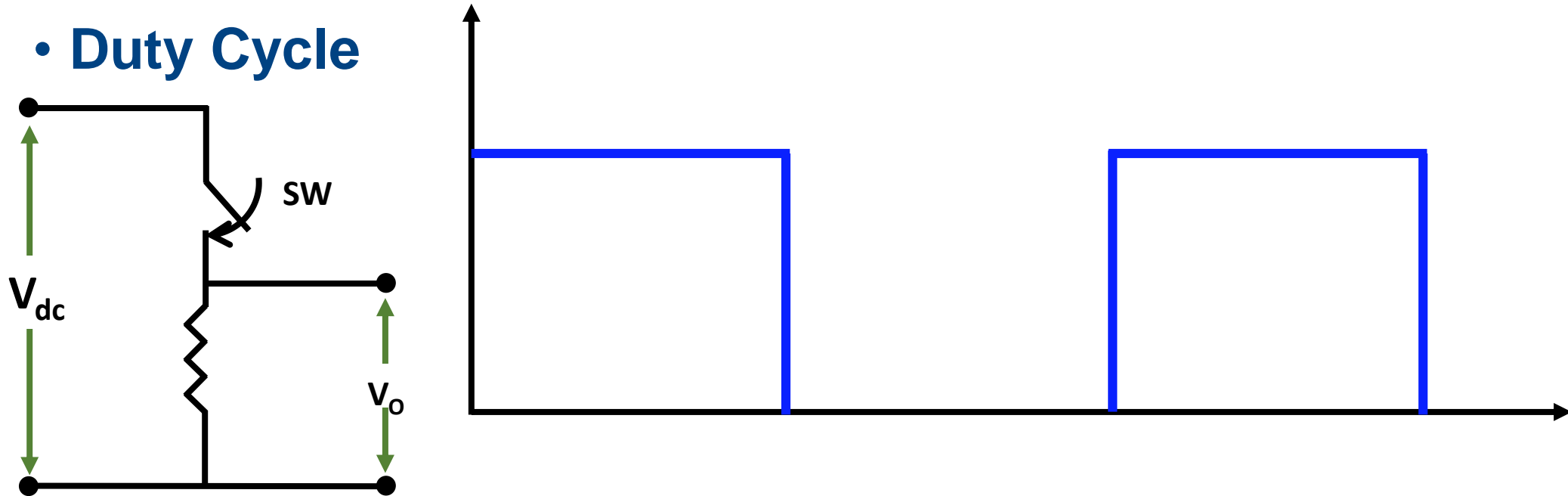

- **Output Voltage**







DC-DC Buck Converter Design




DC Buck Converter Design

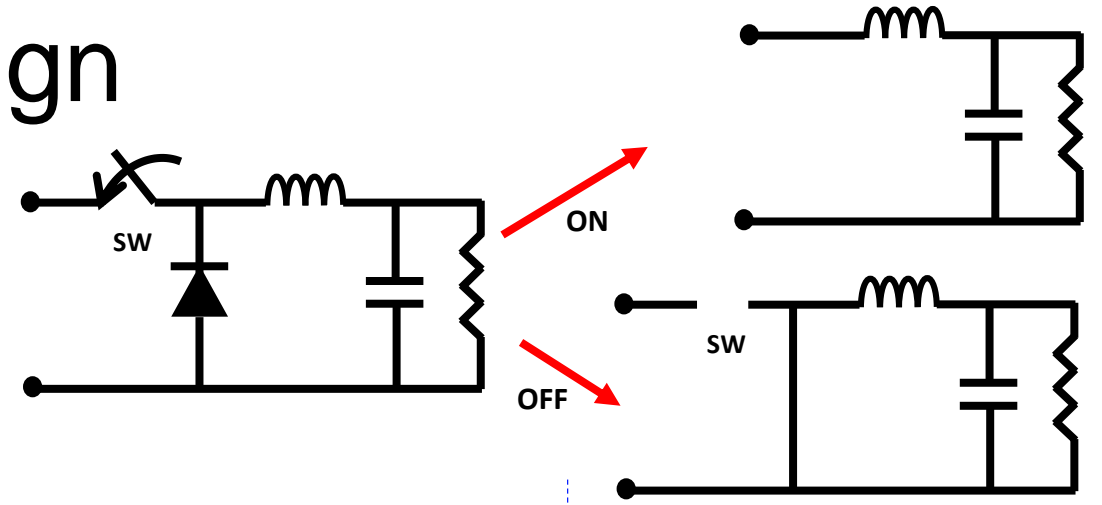


DC Buck Converter Design

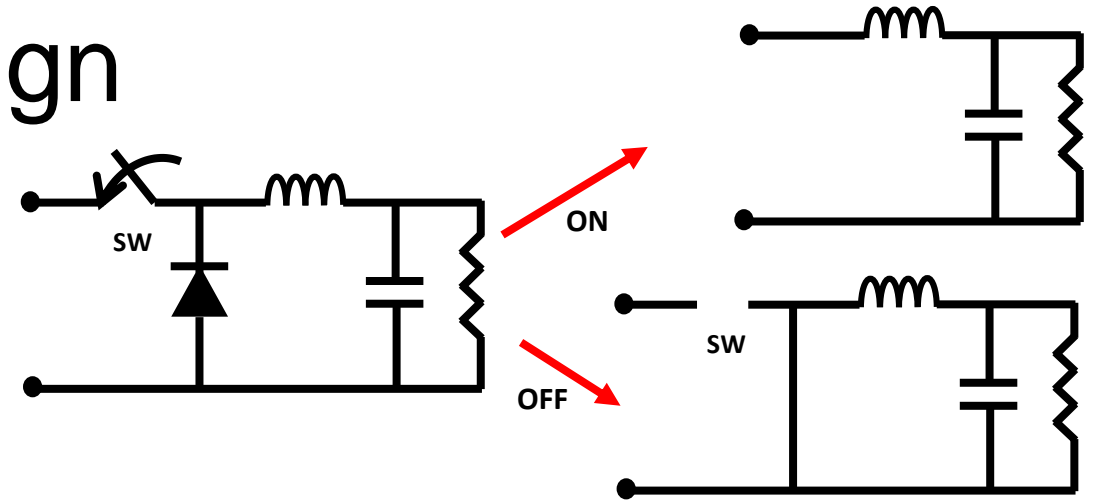

DC Buck Converter Design

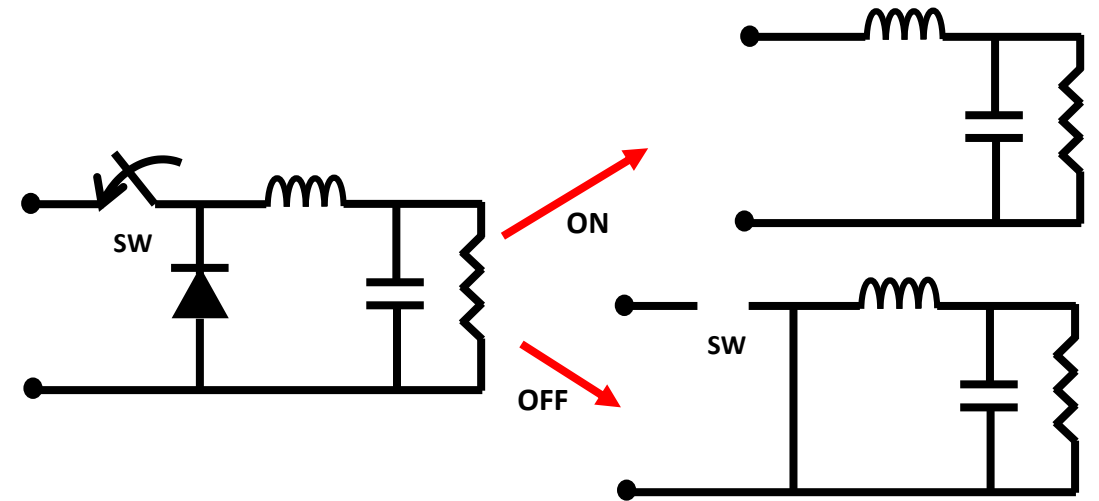

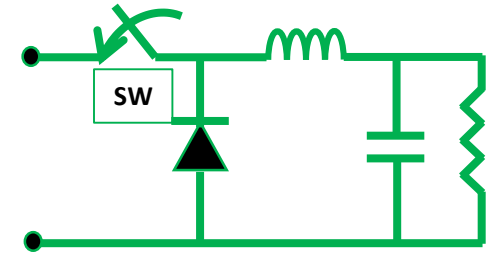Example: A DC DC buck Converter as shown below is switching at a frequency of $f_s = 1 \text{ kHz}$ with a duty cycle of 50 %, $L = 10 \text{ mH}$, $R = 5 \Omega$, $C = 100 \mu\text{F}$, $V_d = 100 \text{ V}$.





DC-AC Invertor

- Voltage Source Invertors
 - Pulse-width modulated inverter (e.g. Sine –PWM)
 - The inverter itself controls the frequency as well as magnitude of the ac output voltage by doing pulse-width modulation
 - Square Wave Invertors
 - Invertor needs to control only the frequency
 - The input DC voltage is controlled by external means (e.g. DC-DC Convertors)
 - The output of such a converter is more like a square-wave and therefore the name given as square-wave inverter
 - **Half-Bridge Invertor**
 - Full-Bridge Invertor




DC- AC Invertor


- Single Phase Square Wave Invertor

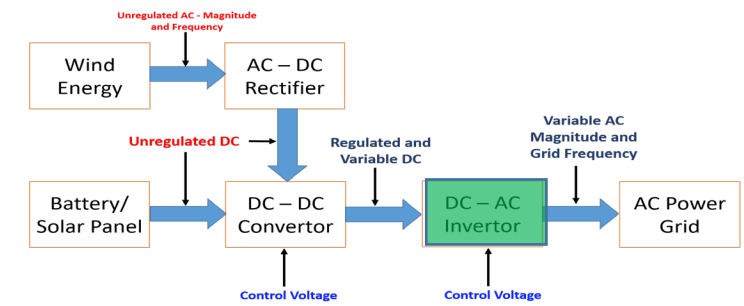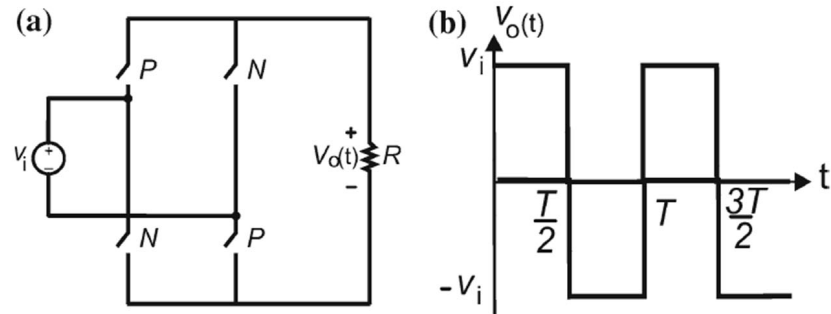

- Single Phase Sine PWM Invertor

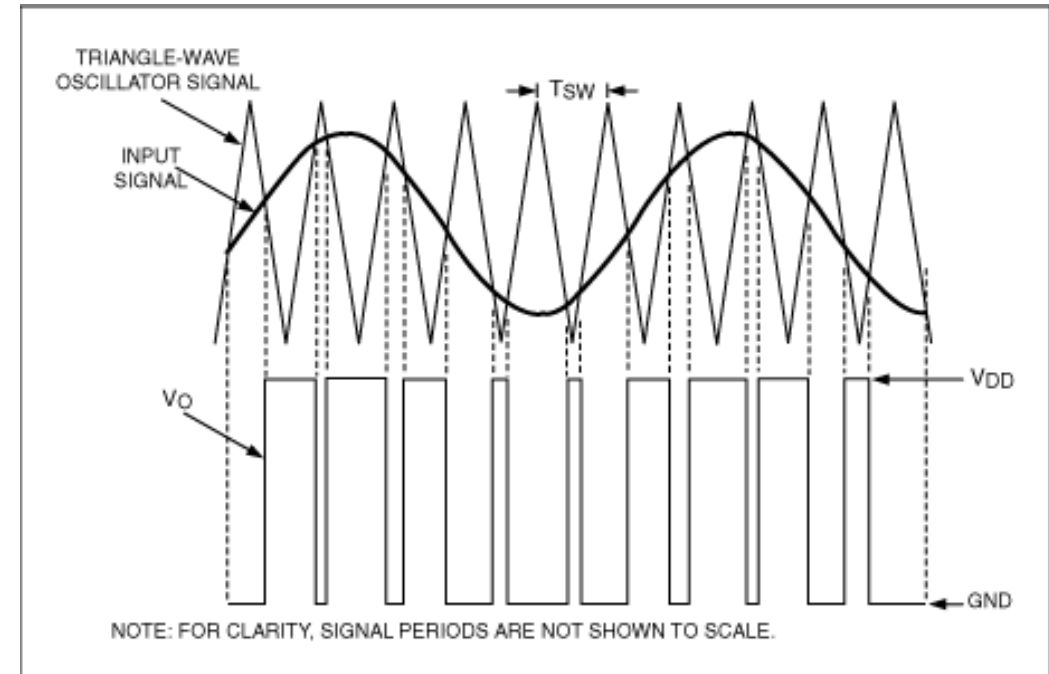



Half Bridge Square Invertor

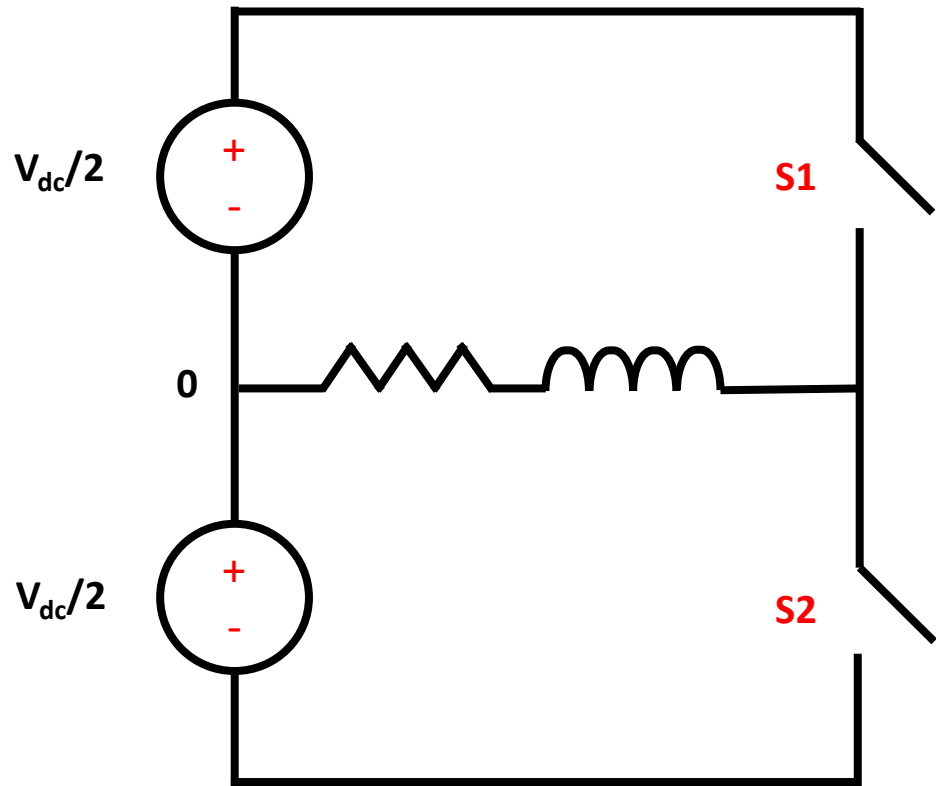

Conducting Switch	Output Voltage
S1	
S2	



Half Bridge Square Inverter

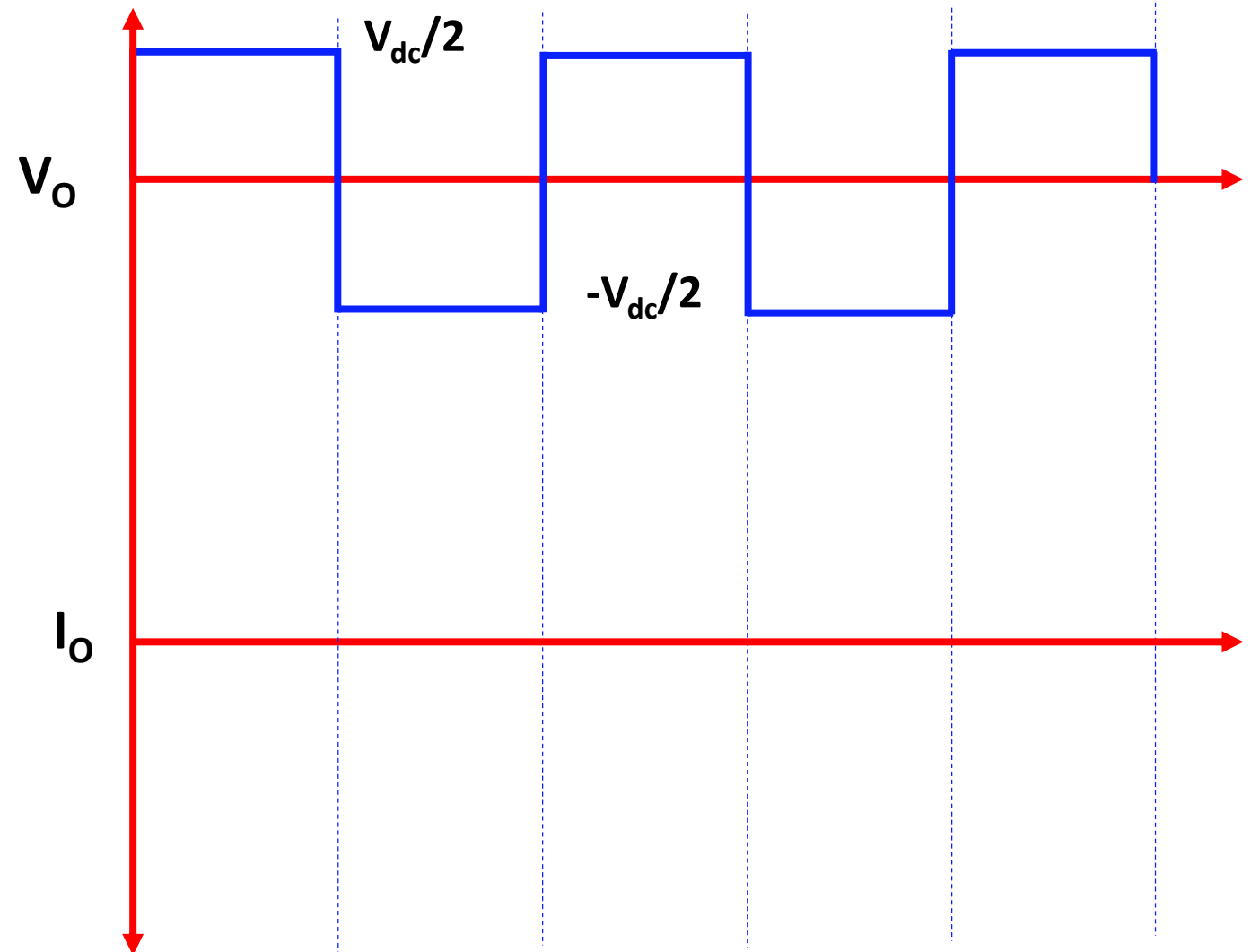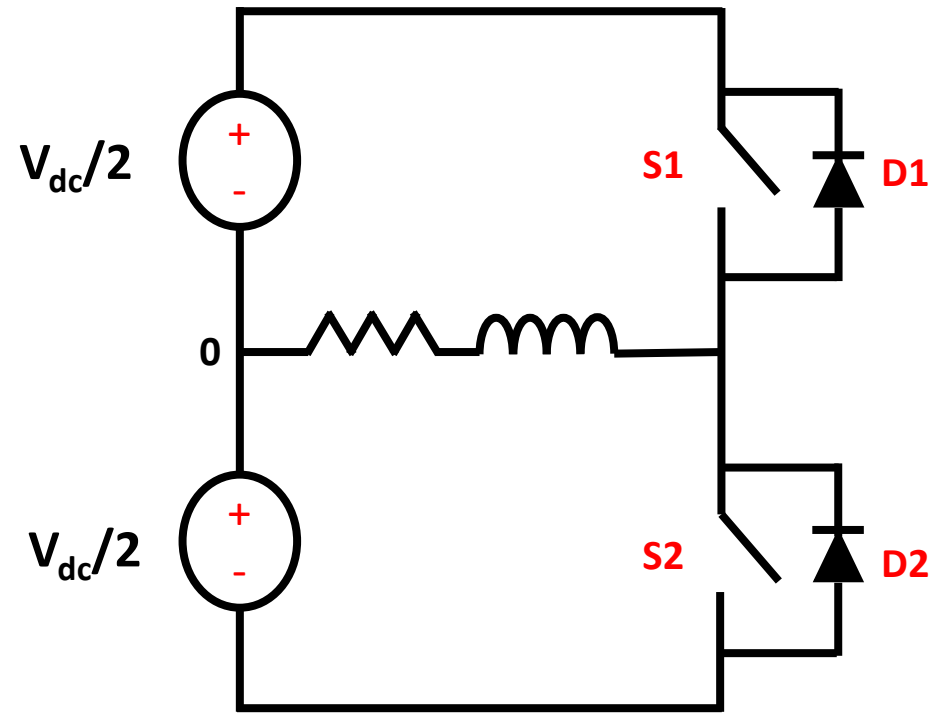

Harmonic Distortion: Square Wave vs Sine Wave

- How Sinusoidal is the Square Wave???
- Express the Square wave as a **Sum of Sine Waves** (Fourier Series Analysis)

$$v_o = \sum_{n, \text{odd}}^{\infty} \frac{4V_{dc}}{n\pi} \sin(n\omega t)$$

$$v_1 = \frac{4V_{dc}}{\pi} \sin(\omega t)$$

$$v_{1,rms} = \frac{4V_{dc}}{\sqrt{2}\pi}$$

- **Total Harmonic Distortion**
- The quality of the ac output voltage can be determined from the Total Harmonic Distortion (THD) factor

- $V_{o,rms} = V_{dc}$ (RMS value of square wave)

- $V_{1,rms} = \frac{4V_{dc}}{\sqrt{2}\pi}$

- $THD_v = \frac{\sqrt{V_{o,rms}^2 - V_{1,rms}^2}}{V_{1,rms}}$

$$= \frac{\sqrt{(V_{dc})^2 - \left(\frac{4V_{dc}}{\sqrt{2}\pi}\right)^2}}{\frac{4V_{dc}}{\sqrt{2}\pi}} = 48.3\%$$





QUESTIONS