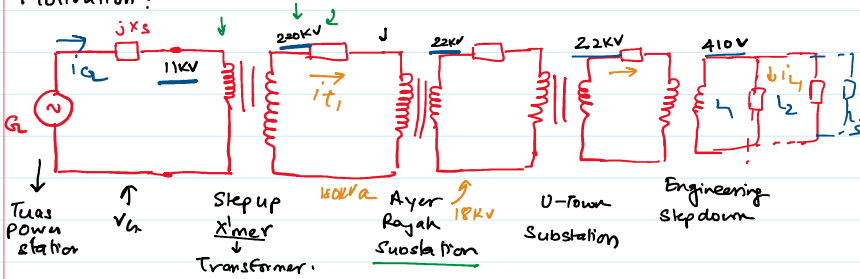



10.1 Per Unit Analysis

Tuesday, 22 March 2022 11:48 am

→ Motivation?



→ Reflected load

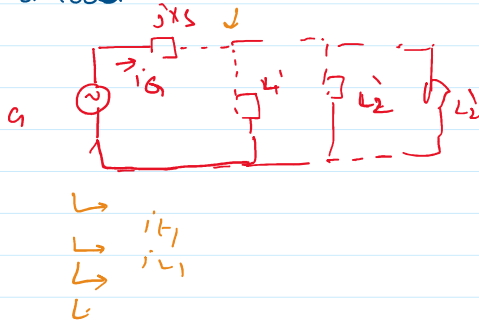

→ Difficult to observe the current situation of the system

→ Decoupling the dependence on transformer ratios


* Per Unit Quantity

$$\text{per unit quantity} = \frac{\text{Actual Quantity}}{\text{Base Value of Quantity.}}$$

→ p.u.

→ All Base values → Real Quantities

S_B
denotes Base value.

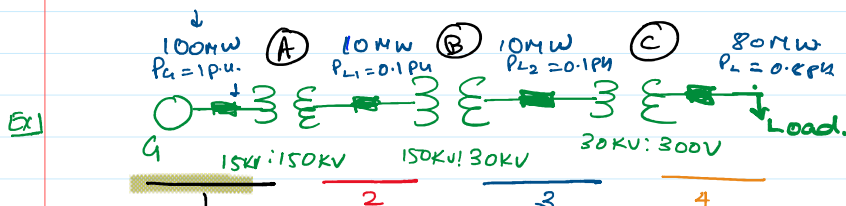

→ Use transformers to differentiate the zones of the system

→ Power Base → Single Base for the whole system

→ Voltage Base →

Example of single voltage Base for the whole system
 → 150kV.
 0.1 : 1 1 : 0.2 0.2 : 0.02
 → Different voltage levels in each zone

At substation A $\text{A-D} \begin{cases} \text{---} \end{cases}$
 15kV : 150kV

$$V_{1B} \rightarrow 15kV$$

$$V_{2B} \rightarrow 150kV$$

At substation B $\text{---} \begin{cases} \text{---} \end{cases}$
 150kV : 30kV

$$V_{3B} \rightarrow 30kV$$


$$V_{2B} \rightarrow 150kV$$

At substation C $\text{---} \begin{cases} \text{---} \end{cases}$
 30kV : 300V


$$V_{3B} \rightarrow 30kV$$

$$V_{4B} \rightarrow 300V$$

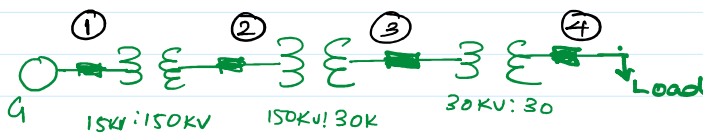p.u. → $\begin{matrix} \downarrow & \downarrow & \downarrow \\ 1pu : 1pu & 1pu : 1pu & 1pu : 1pu \\ 15kV : 150kV & 150kV : 30kV & 30kV : 300V \end{matrix}$



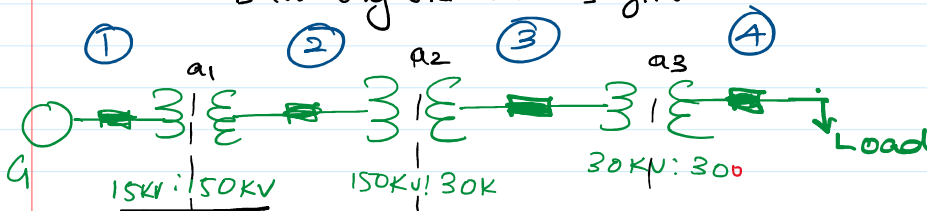① Choose V_B for any one zone.
 or V_B for any one zone is given.



$$\begin{aligned} V_{1B} &= a_1 V_{2B} \\ &= \frac{15}{150} \times 150 \\ &= 15kV \end{aligned}$$

$$\begin{aligned} V_{3B} &= \frac{V_{2B}}{a_2} \\ &= \frac{150kV \times 30}{150} \\ &= 30kV \end{aligned}$$

$$\begin{aligned} V_{4B} &= \frac{V_{3B}}{a_3} \\ &= \frac{30kV \times 300}{30kV} \\ &= 300V \end{aligned}$$

$$\begin{array}{|l|l|l|l|}
 \hline
 = 15 \text{ kV} & & = 150 \text{ kV} \times \frac{30}{150} & = 30 \text{ kV} \\
 & & = 30 \text{ kV} & = 300 \text{ V} \\
 \hline
 V_{1B} = a_1 \cdot V_{2B} & V_{2B} = a_2 \cdot V_{3B} & V_{3B} = 100 \text{ kV} & V_{4B} = \frac{V_{3B}}{a_3} \\
 = \frac{1}{10} \times 500 & = 500 \text{ kV} & & = 100 \text{ kV} \cdot \frac{300}{30 \text{ kV}} \\
 = 50 \text{ kV} & & & = 1000 \text{ V}
 \end{array}$$

→ Given or choose one ^{zone.} voltage Base
 → Use transformer ratios to find Base for other zones

3) Current Base $S_B = V_B I_B \rightarrow I_B = \frac{S_B}{V_B}$

$$\begin{array}{|l|l|l|l|}
 \hline
 I_{1B} = \frac{S_B}{V_{1B}} & I_{2B} = \frac{S_B}{V_{2B}} & I_{3B} = \frac{S_B}{V_{3B}} & I_{4B} = \frac{S_B}{V_{4B}}
 \end{array}$$

4) Impedance Base $Z_B = \frac{V_B}{I_B} = \frac{V_B^2}{S_B}$

$$\begin{array}{|l|l|l|l|}
 \hline
 Z_{1B} = \frac{V_{1B}^2}{S_B} & Z_{2B} = \frac{V_{2B}^2}{S_B} & Z_{3B} = \frac{V_{3B}^2}{S_B} & Z_{4B} = \frac{V_{4B}^2}{S_B}
 \end{array}$$

$$\begin{aligned}
 S_B &= V_B I_B \\
 V_B &= Z_B I_B
 \end{aligned}$$

p.u value = $\frac{\text{Actual value}}{\text{Base value.}}$

→ $S_{pu} \rightarrow V_{pu} \rightarrow I_{pu} \rightarrow Z_{pu}$

$$S_{pu} = V_{pu} \cdot I_{pu}^*$$

$$S_{pu} = P_{pu} + j Q_{pu}$$

$$S = V \cdot I^*$$

$$\begin{aligned}
 &= \frac{P + j Q}{S_B} \\
 &= \frac{P}{S_B} + j \frac{Q}{S_B}
 \end{aligned}$$

$$\frac{S}{S_B} = \frac{V \cdot I^*}{S_B} = \frac{V \cdot I^*}{V_B \cdot I_B}$$

$$S_{pu} = \frac{V}{V_B} \cdot \frac{I^*}{I_B} = \frac{V}{V_B} \cdot \left(\frac{I}{I_B} \right)^*$$

$$\downarrow$$

$$S_{pu} = \frac{V}{V_B} \cdot \frac{I^*}{I_B} = \frac{V}{V_B} \cdot \left(\frac{I}{I_B}\right)^*$$

$$S_{pu} = V_{pu} \cdot I_{pu}^*$$

$$\rightarrow V = I \cdot Z$$

$$\frac{V}{V_B} = \frac{I \cdot Z}{V_B} = \frac{I \cdot Z}{I_B \cdot Z_B}$$

$$V_{pu} = I_{pu} \cdot Z_{pu}$$

$\rightarrow P, Q, S$ all have the same power base.

$$\rightarrow S = V I^*$$

$$\frac{S}{S_B} = \frac{V I^*}{V_B I_B}$$

\downarrow

$$\frac{P + jQ}{S_B} \rightarrow \frac{P}{S_B} + j \frac{Q}{S_B}$$

$$\rightarrow P_{pu} + j Q_{pu}$$

$$\rightarrow 10 \text{ MW} \quad \cos \theta = 0.8 \text{ lag}$$

$$\rightarrow 12.5 \text{ MVA}$$

$$S_B \rightarrow 20 \text{ MVA}$$

$$P_{pu} = \frac{10}{20} = 0.5 \text{ pu}$$


$$S_{pu} = \frac{12.5 \angle 36.87}{20} = 0.625 \angle 36.87 \text{ pu}$$


$$Q_{pu} = \frac{Q_{\text{actual}}}{S_B} = \frac{10 \tan 36.87}{20} = \frac{7.5}{20}$$

$$= 0.375 \text{ pu}$$

\rightarrow KVL & KCL for per unit values

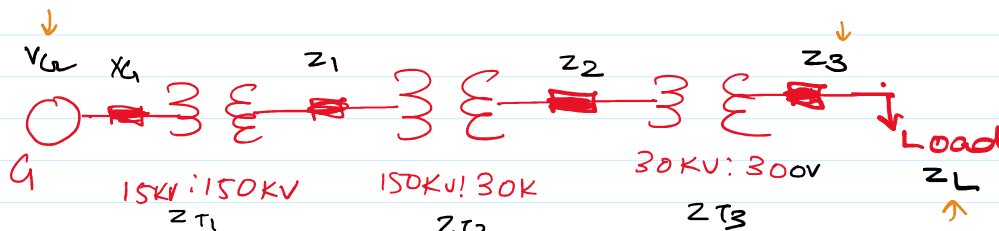\rightarrow Actual quantity is found by multiplying the pu value with the corresponding base value.



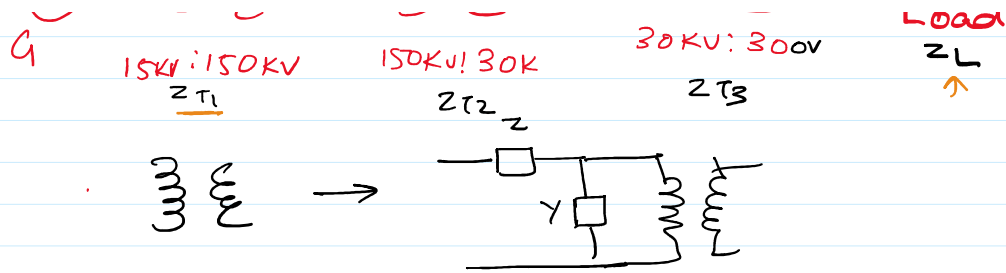

$\leftarrow S_B \rightarrow 10 MW$

$$V_{1B} = 15kV$$

$$V_{2B} = 150kV$$

$$V_{3B} = 30kV$$

$$V_{4B} = 300V$$

$$I_{1B} = \frac{S_B}{V_{1B}}$$

$$I_{2B} = \frac{S_B}{V_{2B}}$$

$$I_{3B} = \frac{S_B}{V_{3B}}$$

$$I_{4B} = \frac{S_B}{V_{4B}}$$

$$Z_{1B} = \frac{V_{1B}^2}{S_B}$$

$$Z_{2B} = \frac{V_{2B}^2}{S_B}$$

$$Z_{3B} = \frac{V_{3B}^2}{S_B}$$

$$Z_{4B} = \frac{V_{4B}^2}{S_B}$$

$$V_{upu} = \frac{V_B}{V_{1B}}$$

$$Z_{1pu} = \frac{Z_1}{Z_{2B}}$$


$$Z_{2pu} = \frac{Z_2}{Z_{3B}}$$

$$Z_{3pu} = \frac{Z_3}{Z_{4B}}$$

$$X_{1pu} = \frac{X_B}{Z_{1B}}$$

$$Z_{Lpu} = \frac{Z_L}{Z_{4B}}$$

eg \Rightarrow

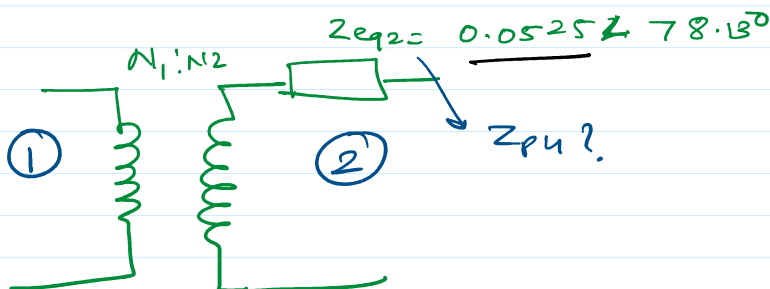

$$480/120V, S = 20kVA, Z_{in p.u.}$$

Transformer rating as Base values

$$S_B = 20kVA$$

$$V_{1B} = 480V$$

$$V_{2B} = \frac{120}{480} \times 480$$

$$= 120V$$

$$Z_{1B} = \frac{V_{1B}^2}{S_B}$$

2

$$Z_{1B} = \frac{V_{1B}^2}{S_B}$$

$$= 11.52 \Omega$$


$$= 120V$$

$$Z_{2B} = \frac{V_{2B}^2}{S_B}$$

$$= 0.72 \Omega$$

$$Z_{pu} = \frac{0.0525 \angle 78.13^\circ}{Z_{2B}}$$
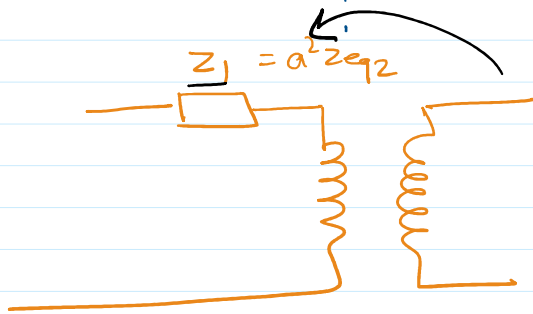
$$= \underline{0.0729 \angle 78.13^\circ \text{ p.u.}}$$





$$Z_1 = \left(\frac{480}{120} \right)^2 \times 0.0525 \angle 78.13^\circ$$

$$= \underline{0.84 \angle 78.13^\circ \Omega}$$

$$Z_{1pu} = \frac{Z_1}{Z_{1B}} = \frac{0.84 \angle 78.13^\circ}{11.52}$$
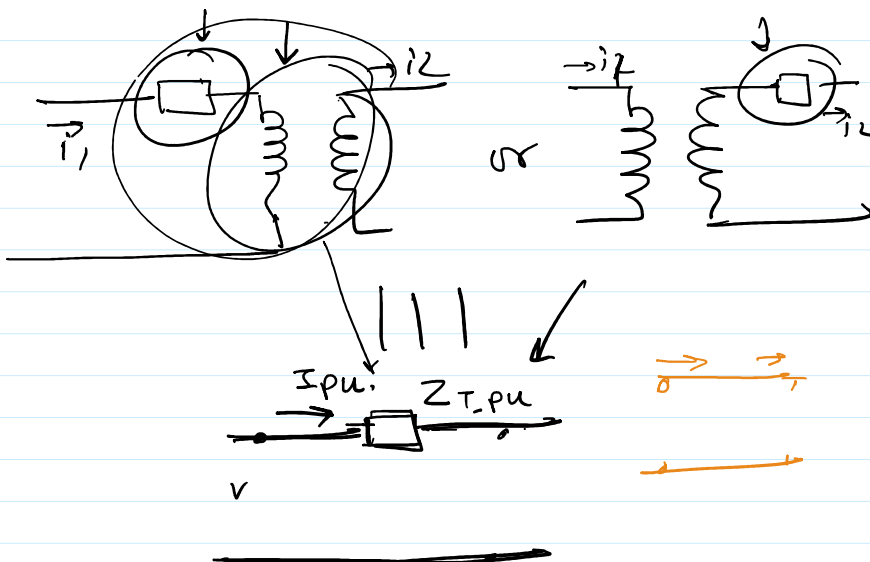
$$= \underline{0.0729 \angle 78.13^\circ \text{ p.u.}}$$



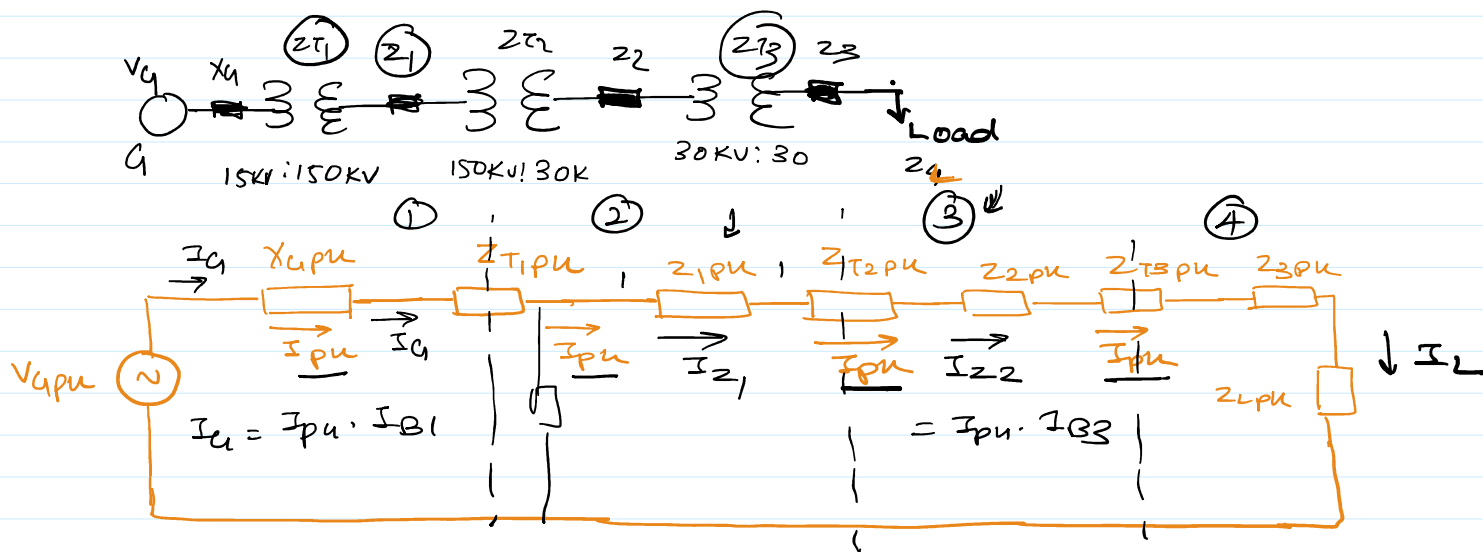

per unit impedance diagram


$$I_{pu} = \frac{V_{Gpu}}{Z_{Totalpu}}$$

$$I_G = I_{pu} \times I_{B1}$$

$$I_{Z1} = I_{pu} \times I_{B2}$$

$$I_{Z2} = I_{pu} \times I_{B3}$$

$$I_L = I_{pu} \times I_{B4}$$

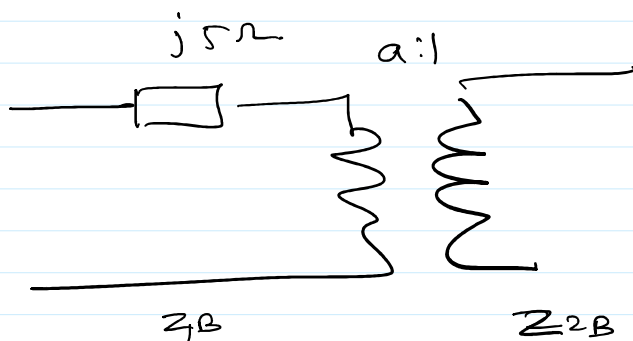

$$Z_{Tpu} = \frac{j5}{Z_{1B}}$$

$$Z_{Tpu} = \frac{j5/a^2}{Z_{2B}}$$

