

## 4.1 Three – Phase Power

Friday, February 04, 2022 1:26 PM



### 4.0 In-Class Lecture - 3-Phase Power - EE2029



## EE2029: Introduction to Electrical Energy System




### 3-Phase Power

Lecturer : Dr. Sangit Sasidhar  
Department of Electrical and Computer Engineering




© Copyright National University of Singapore. All Rights Reserved.  
[PollEv.com/sangitsasidhar](http://PollEv.com/sangitsasidhar)

1

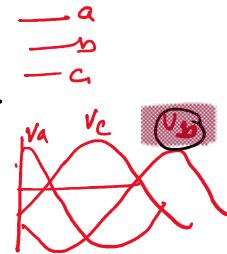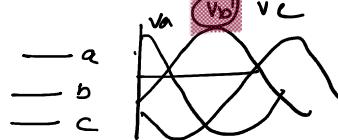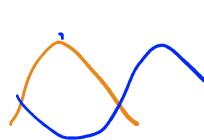

### Three-Phase Voltage Sources

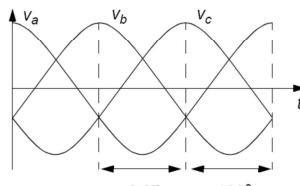

$$v_a + v_b + v_c = 0$$

$$v_a = \sqrt{2}|V| \cos(\omega t)$$
$$v_b = \sqrt{2}|V| \cos\left(\omega t - \frac{2\pi}{3}\right)$$

#### • Positive Sequence

$$\begin{aligned} V_{cn} &= 1 \angle +120^\circ \\ \text{Positive sequence, } abc & \\ V_{an} &= 1 \angle 0^\circ \\ V_{bn} &= 1 \angle -120^\circ \end{aligned}$$

$$\begin{aligned} \bullet \text{ Negative Sequence} \\ V_n &= 1 \angle +120^\circ \end{aligned}$$

$$V_A + V_B + V_C = 0$$

$V_c$   $\leftarrow 120^\circ$

$$v_b = \sqrt{2}|V| \cos\left(\omega t - \frac{2\pi}{3}\right)$$

$$v_c = \sqrt{2}|V| \cos\left(\omega t - \frac{4\pi}{3}\right)$$




© Copyright National University of Singapore. All Rights Reserved.  
PollEv.com/sangitsasidhar

• Negative Sequence

$$\begin{aligned} V_{bn} &= 1 \angle +120^\circ \\ \text{Negative sequence,} \\ \text{acb} \quad V_{an} &= 1 \angle 0^\circ \\ V_{cn} &= 1 \angle -120^\circ \end{aligned}$$

2

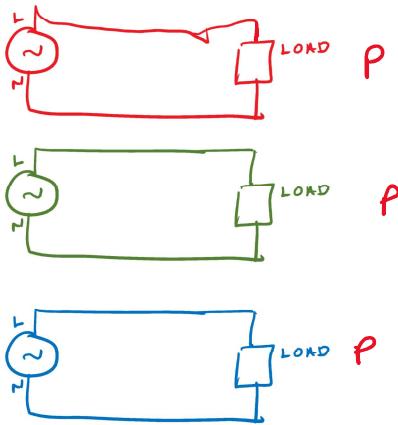
## Three Single Phase vs Three Phase Circuits




PollEv.com/sangitsasidhar

$$G \rightarrow 3P$$

Conc.

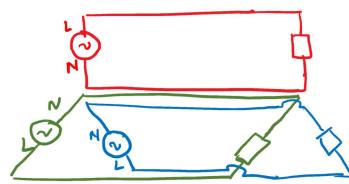
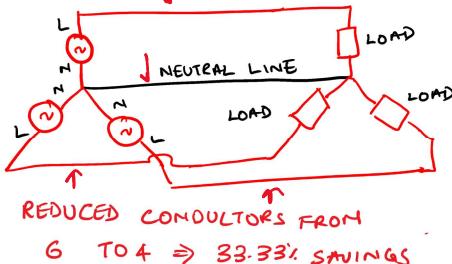
$$\begin{array}{l} 220V \\ 110V \\ 0V \end{array}$$




$$3P \rightarrow 4$$

3


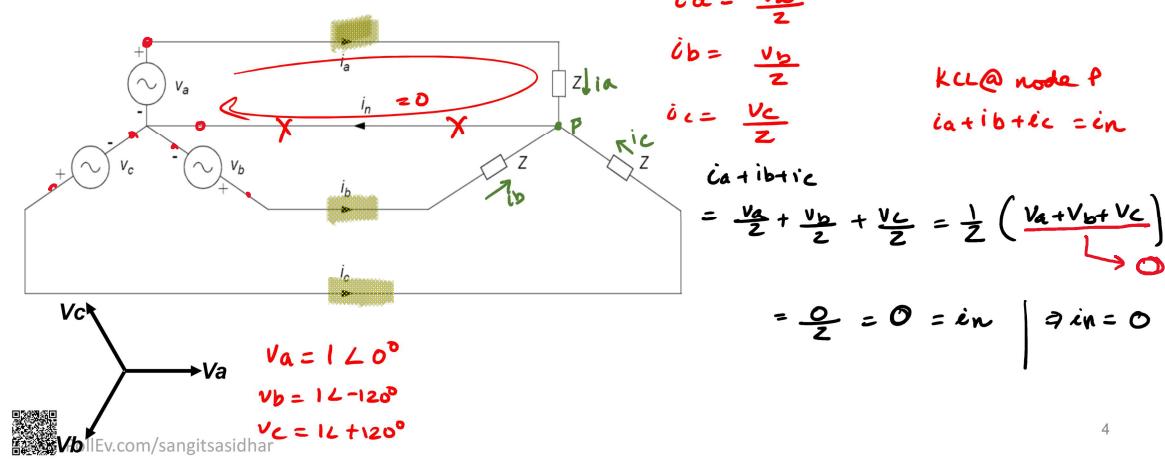
## Balanced Three-Phase Circuit

- Three-phase circuit is said to be balanced when the impedances in the 3 phases are identical



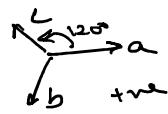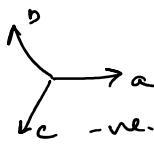
## Example:

- What is the phase sequence?
- Are these balanced three-phase voltage sources?



$$V_{cn} \rightarrow V_c$$
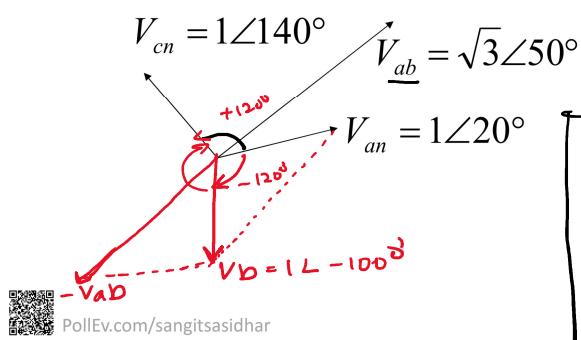
$$V_{ab} \rightarrow V_{an} - V_{bn}. \text{ +ve sequence.}$$



$$V_{cn} \rightarrow V_{an}$$


$$V_{cn} \rightarrow V_{an} \times 1 \angle 120^\circ = 122^\circ \times 1 \angle 120^\circ \\ = 1 \angle 140^\circ$$

$$V_{ab} = V_{an} - V_{bn}$$

$$V_{bn} = \frac{V_{an} - V_{ab}}{} = \frac{V_{an} + (-V_{ab})}{\sqrt{3}} \\ = 1 \angle 20^\circ - \sqrt{3} \angle 50^\circ \\ = 1 \angle -100^\circ$$

5

## How do we Measure Voltage/Current

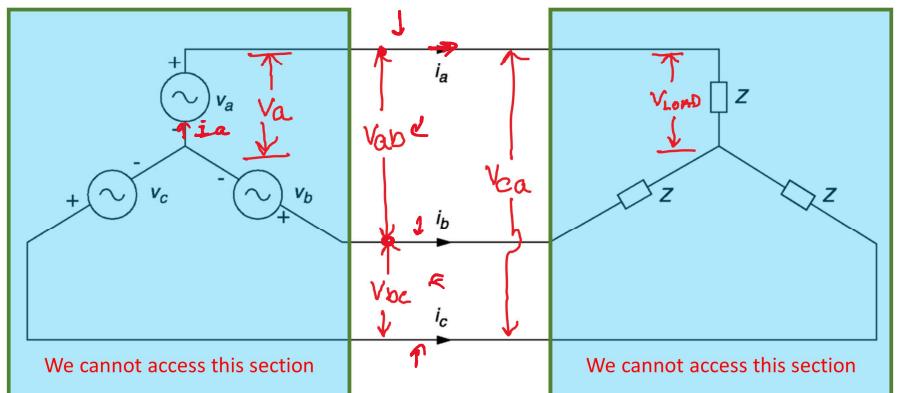

Generator

Measurable values

Induction motor.


Not measurable  $\Rightarrow$  Phase values.



PollEv.com/sangitsasidhar

6

## Line-To-Line Voltage (Line Voltage)

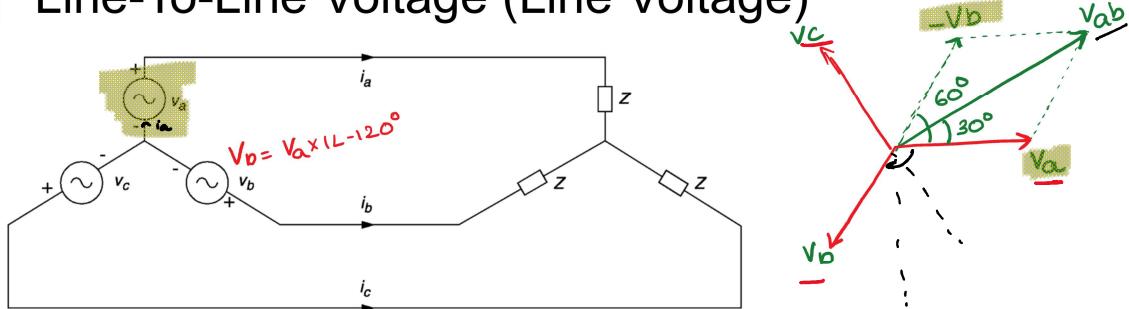

$$\begin{aligned}
 V_{ab} &= V_a - V_b = V_a + C - V_b \\
 &= V_a + V_a L 60^\circ \\
 &= V_a L 0^\circ + V_a L 60^\circ \\
 &= \sqrt{3} V_a L 30^\circ
 \end{aligned}
 \quad \left| \quad \begin{aligned}
 V_{bc} &= V_b + C - V_c \\
 &= \sqrt{3} V_b L 30^\circ \\
 V_{ca} &= V_c + C - V_a \\
 &= \sqrt{3} V_c L 30^\circ
 \end{aligned} \right.$$



PollEv.com/sangitsasidhar

## Line-To-Neutral Voltage (Phase Voltage)

$$V_{ab} = \sqrt{3} V_a \angle 30^\circ$$



$$V_{bc} = \sqrt{3} V_b \angle -30^\circ$$

$$V_{ca} = \sqrt{3} V_c \angle -30^\circ$$

$$|V_{al}| = \frac{|V_{ab}|}{\sqrt{3}}$$

$$|V_{bl}| = \frac{|V_{bc}|}{\sqrt{3}}$$

$$|V_{cl}| = \frac{|V_{ca}|}{\sqrt{3}}$$

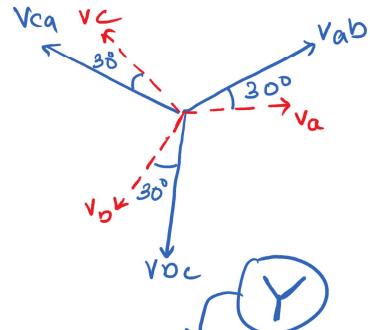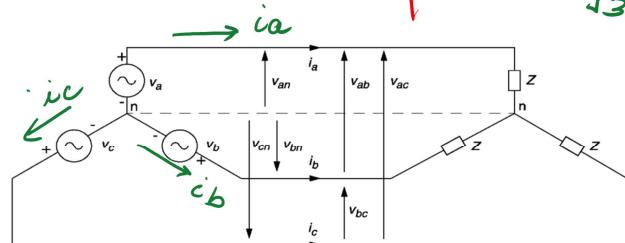


$$|V_{phase}| = \frac{|V_{line}|}{\sqrt{3}}$$




PollEv.com/sangitsasidhar

8

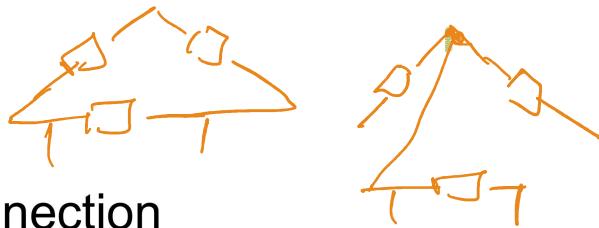


## 3-Phase Circuit Connection

**Wye Connection**

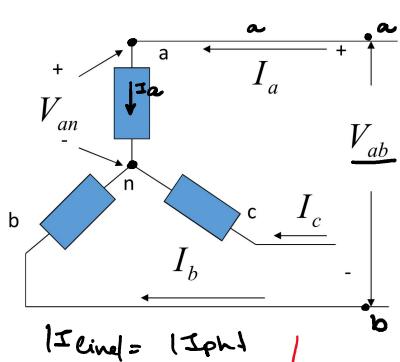

$$|I_{\text{line}}| = |I_{\text{ph}}|$$

**Delta Connection**

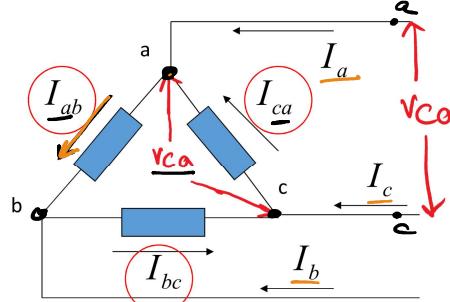

What are these currents?

These two types of connections apply to both three-phase voltage sources and three-phase loads  
 $|V_{\text{line}}| = \sqrt{3}|V_{\text{ph}}|$



© Copyright National University of Singapore. All Rights Reserved.

PollEv.com/sangitsasidhar

$$|V_{\text{line}}| = |V_{\text{ph}}|$$

$$|I_{\text{line}}| = \sqrt{3}|I_{\text{ph}}|$$

9

## Delta-Connected Load

KCL @ JUNCTION A

$$I_{ab} = I_{ca} + I_a$$


$$\Rightarrow I_a = I_{ab} - I_{ca}$$

$$I_a = I_{ab} + (-I_{ca}) \\ = \sqrt{3} I_{ab} \angle -30^\circ$$


$$I_a = \sqrt{3} I_{ab} \angle -30^\circ$$

$$I_b = \sqrt{3} I_{bc} \angle -30^\circ$$
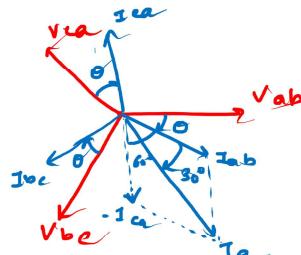
$$I_c = \sqrt{3} I_{ca} \angle -30^\circ$$



$$V_{LINE} = V_{PHASE}$$

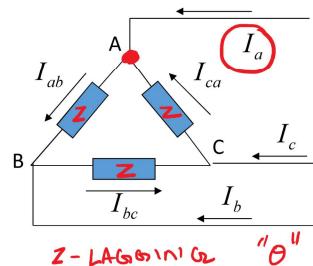

$\Rightarrow$  FOR  $\Delta$  (DELTA)

$$|I_{LINE}| = \sqrt{3} |I_{PHASE}|$$

$$\text{OR } |I_{PHASE}| = \frac{|I_{LINE}|}{\sqrt{3}}$$




© Copyright National University of Singapore. All Rights Reserved.  
PollEv.com/sangitsasidhar

**Example:** For a balanced Y-connected three phase voltage source and Y-connected load system with a line voltage of 440V and three equal resistive loads of 100 Ω per phase, assume positive sequence, what will be the magnitudes of  
 (a) the line-to-neutral voltage, (b) the phase current, (c) the line current?

$$a) V_{line} = 440V \rightarrow V_{ph} = \frac{440}{\sqrt{3}} = 254.04V$$

$$b) |I_{ph}| = \frac{|V_{ph}|}{|Z|} = \frac{254.04}{100} = 2.54A.$$

$$c) |I_{line}| = |I_{ph}| = 2.54A.$$

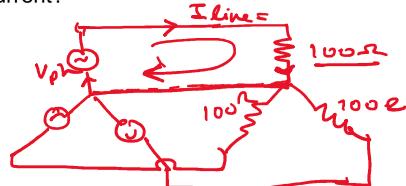


## Balanced Three-Phase Power $S_{3\Phi} = V I^*$

- From three phase power,

$$S_{3\Phi} = V_{an} I_a^* + V_{bn} I_b^* + V_{cn} I_c^*$$

- When the system is balanced, (assume positive sequence) we can write,

$$S_{3\Phi} = V_{an} I_a^* + V_{an} \angle -120^\circ (I_a \angle -120^\circ)^* + V_{an} \angle 120^\circ (I_a \angle 120^\circ)^*$$

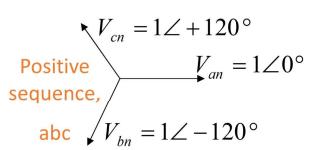Positive sequence,  
abc  


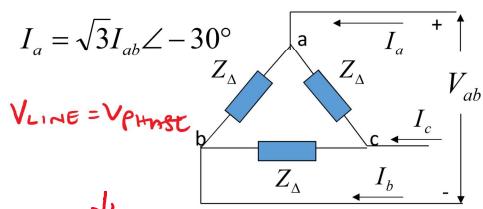
$$S_{3\Phi} = 3V_{an} I_a^* = 3(P + jQ)$$

$$\Rightarrow P_{3\Phi} = 3V_{an} I_a \cos \theta = 3P_{1\Phi}$$


$$Q_{3\Phi} = 3V_{an} I_a \sin \theta = 3Q_{1\Phi}$$



## ■ Delta/Wye Connected 3-Phase Load



$$\begin{aligned}|S_{3\Phi}| &= \frac{3|V_{ab}||I_{ab}|}{\sqrt{3}} \\ &= 3|V_{ab}|\left|\frac{I_a}{\sqrt{3}}\right| \\ &= \sqrt{3}|V_{LINE}||I_{LINE}|\end{aligned}$$

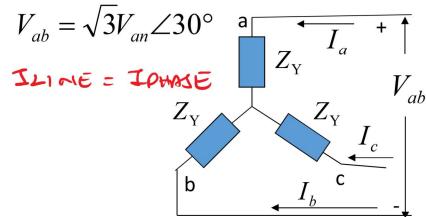

$$\begin{aligned}|S_{3\Phi}| &= 3|V_{an}||I_{an}| \\ &= 3\left|\frac{V_{ab}}{\sqrt{3}}\right||I_{an}| \\ &= \sqrt{3}|V_{LINE}||I_{LINE}|\end{aligned}$$


$$\Rightarrow |S_{3\Phi}| = \sqrt{3}|V_{Line-To-Line}||I_{Line}|$$



PollEv.com/sangitsasidhar

13

## Delta-Wye Load Transformation

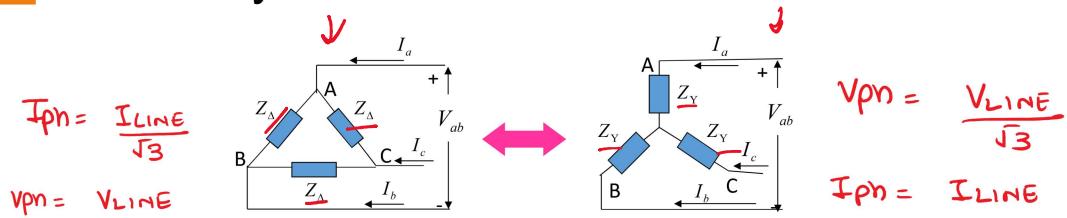

$$Z_\Delta = \frac{V_{pn}}{I_{pn}} = \frac{V_{AB}}{I_{AB}}$$

$$Z_\Delta = \frac{V_{AB}}{I_A/\sqrt{3}} = \frac{\sqrt{3}V_{AB}}{I_A}$$

$$\Rightarrow \frac{V_{AB}}{I_A} = \frac{Z_\Delta}{\sqrt{3}} \quad -①$$

$$Z_Y = \frac{V_{pn}}{I_{pn}} = \frac{V_{AB}}{I_{AB}}$$

$$Z_Y = \frac{V_{AB}/\sqrt{3}}{I_A} = \frac{V_{AB}}{\sqrt{3}I_A}$$

$$\Rightarrow \frac{V_{AB}}{I_A} = \sqrt{3}Z_Y \quad -②$$

① & ②

$$\begin{aligned} \Rightarrow \frac{Z_\Delta}{\sqrt{3}} &= \sqrt{3}Z_Y \\ \Rightarrow Z_\Delta &= 3Z_Y \end{aligned}$$




$$Z_Y = \frac{Z_\Delta}{3}$$



## Per Phase Analysis: Assumption

It must be balanced three-phase circuit

$$I_n = I_a + I_b + I_c = 0$$

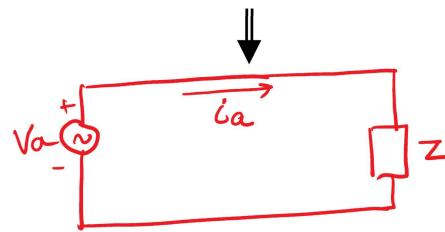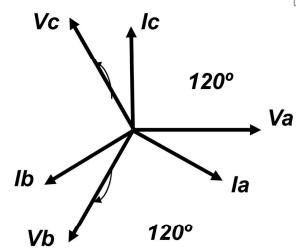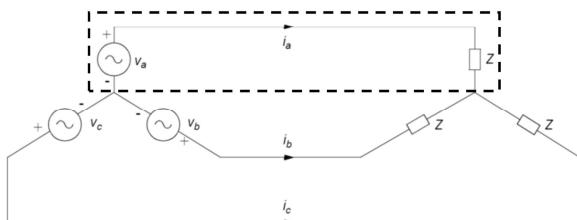

PollEv.com/sangitsasidhar

15

## ■ Steps of Per Phase Analysis


- Make sure that the three-phase system is **balanced**.
  - The three-phase sources need to have the same magnitude with 120 degree phase difference.
  - The three-phase impedances must be of the same value (both phase and magnitude).
- **Convert** all **Delta**-connected sources/loads to **Wye**-connected sources/loads.
- Per phase analysis reduce three-phase circuit to **single-phase** circuit. We can apply the same concept used in single-phase.



PollEv.com/sangitsasidhar

16

## Single-Line Diagram

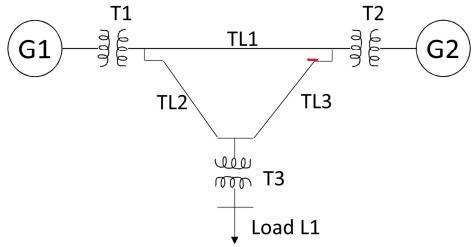


- Show the interconnections of a transmission system
  - Generator
  - Load
  - Transmission line
  - Transformer
- This is a representation of a 3Φ circuit. Each line represents three conductors in three-phase system.



PollEv.com/sangitsasidhar


17

**Example:** Given a one-line diagram, If the voltage source is  $|V_{line}| = \sqrt{3} \text{ V}$ . Find, the current magnitude supplied by source,  $|I_S|$ , and, the current magnitude through a capacitor,  $|I_C|$ .

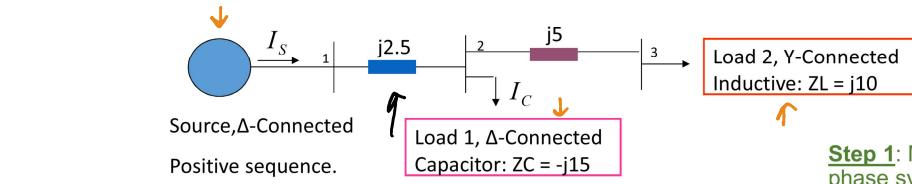

**Step 1:** Make sure that the three-phase system is balanced.

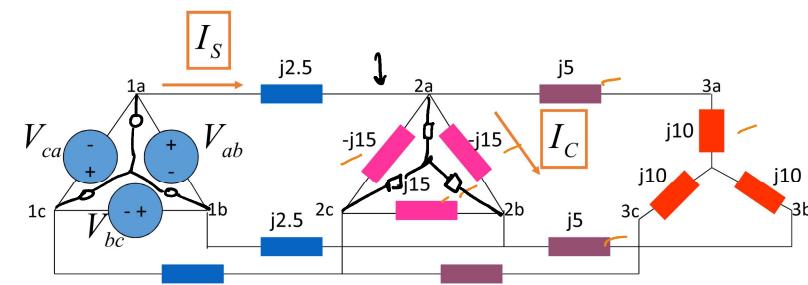- The three-phase sources need to have the same magnitude with 120 degree phase difference.
- The three-phase impedances must be of the same value (both phase and magnitude).




18

$$Z_Y' = \frac{Z_A}{3}$$
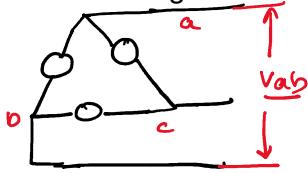
## Step 2: Convert from $\Delta \rightarrow Y$


- Converting the  $Z_\Delta$  to  $Z_Y$ : Load 1  $Z_\Delta = -j15\Omega \Rightarrow Z_Y = \frac{Z_\Delta}{3} = \frac{-j15}{3} = -j5\Omega$

- Converting the Voltage Source from  $\Delta \rightarrow Y$



$$|V_{ab}|_D = \sqrt{3} \text{ V}$$
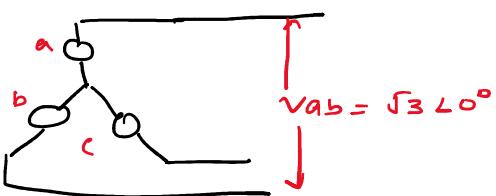
$$V_{ab_D} = \underline{\sqrt{3} \angle 0^\circ}$$



$$V_{ab_Y} = \sqrt{3} \angle 0^\circ$$

$$V_{ab_Y} = V_a - V_b = V_a + (-V_b)$$

$$V_{ab_Y} = V_a + V_a L 60^\circ$$

$$V_{ab_Y} = \sqrt{3} V_a L 30^\circ \quad 19$$

$$60^\circ = \sqrt{3} V_a L 30^\circ$$


$$V_a = \frac{\sqrt{3} L 0^\circ}{\sqrt{3} L 30^\circ}$$

|                        |
|------------------------|
| $V_a = 1 L -30^\circ$  |
| $V_b = 1 L -150^\circ$ |
| $V_c = 1 L 90^\circ$   |



PollEv.com/sangitsasidhar

### Step 3 :Draw the 1-phase Diagram

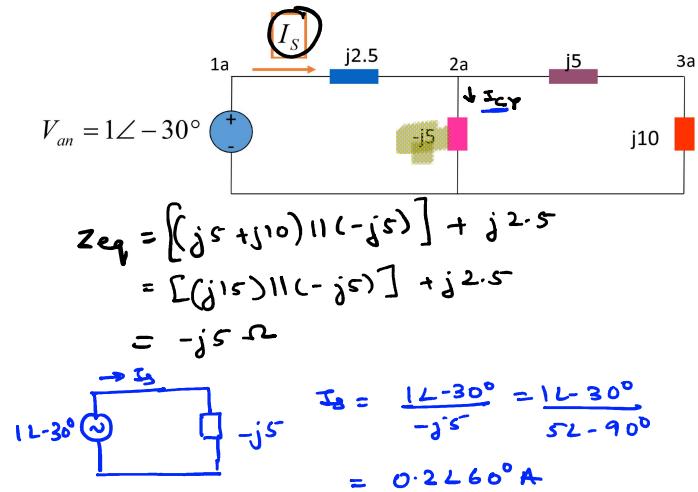

PollEv.com/sangitsasidhar

$$I_C = \frac{V_{2a}}{-j5}$$

$$= \frac{V_a - I_S (j2.5)}{-j5}$$


$$= \frac{1\angle -30^\circ - 0.2\angle 60^\circ (2.5\angle 90^\circ)}{5\angle -90^\circ}$$

$$= 0.3\angle 60^\circ A$$

$I_C = 0.3\angle 60^\circ A$

20

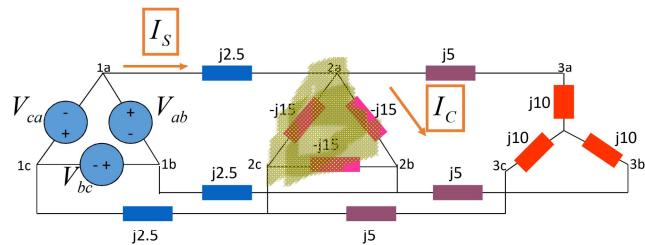
## Step 4: Find the capacitor Current $I_C$



$$I_{ca\Delta} + I_{ba} = I_{ac}$$

$$I_{ca\Delta} = I_{ac} - I_{ba} \\ = \sqrt{3} I_{ac} L - 30^\circ$$
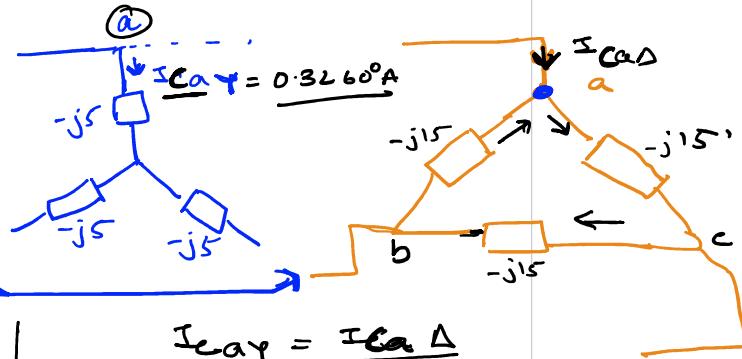
$$I_{ac} = \frac{I_{ca\Delta}}{\sqrt{3} L - 30^\circ}$$



$$\underline{I_{ca\Delta}} = \underline{I_{ca\Delta}}$$

line currents are same.

$$I_{ac} = \frac{0.3260^\circ}{\sqrt{3} L - 30^\circ} \\ = \left| \frac{\sqrt{3}}{10} \right| L + 90^\circ A \\ = 0.1732 L 90^\circ A.$$

$$|I_C| = 0.1732 A,$$



PollEv.com/sangitasidhar