



EE2029: Introduction to Electrical Energy System

AC Fundamentals

Lecturer : Dr. Sangit Sasidhar (elesang)
Department of Electrical and Computer Engineering



Why AC and not DC???

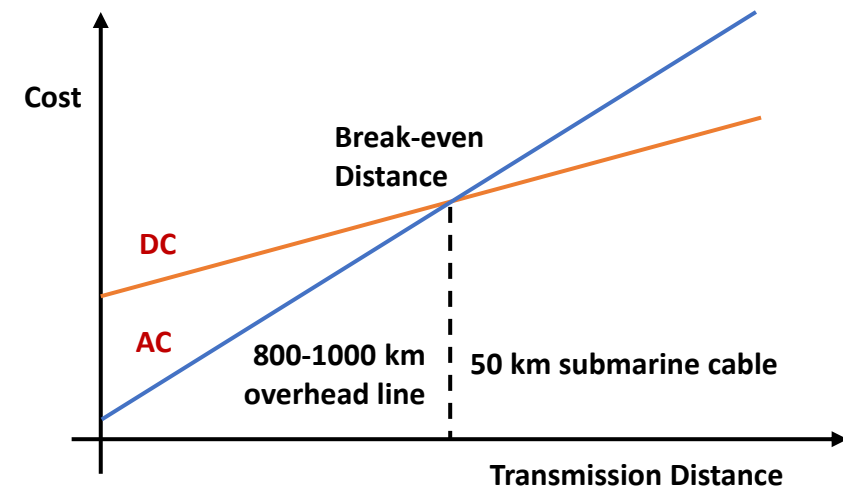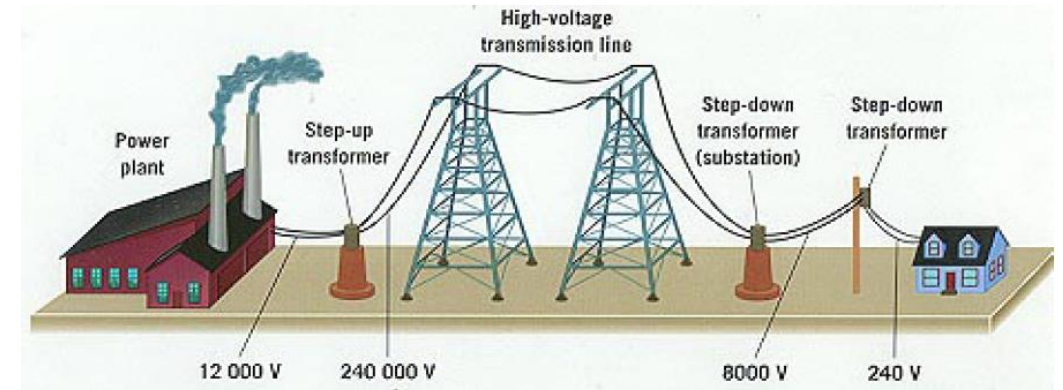- Transformers allow easy transformation of voltage
- Break-even distance for high voltage direct current (HVDC)




Why a Sinusoidal Alternating Voltage?

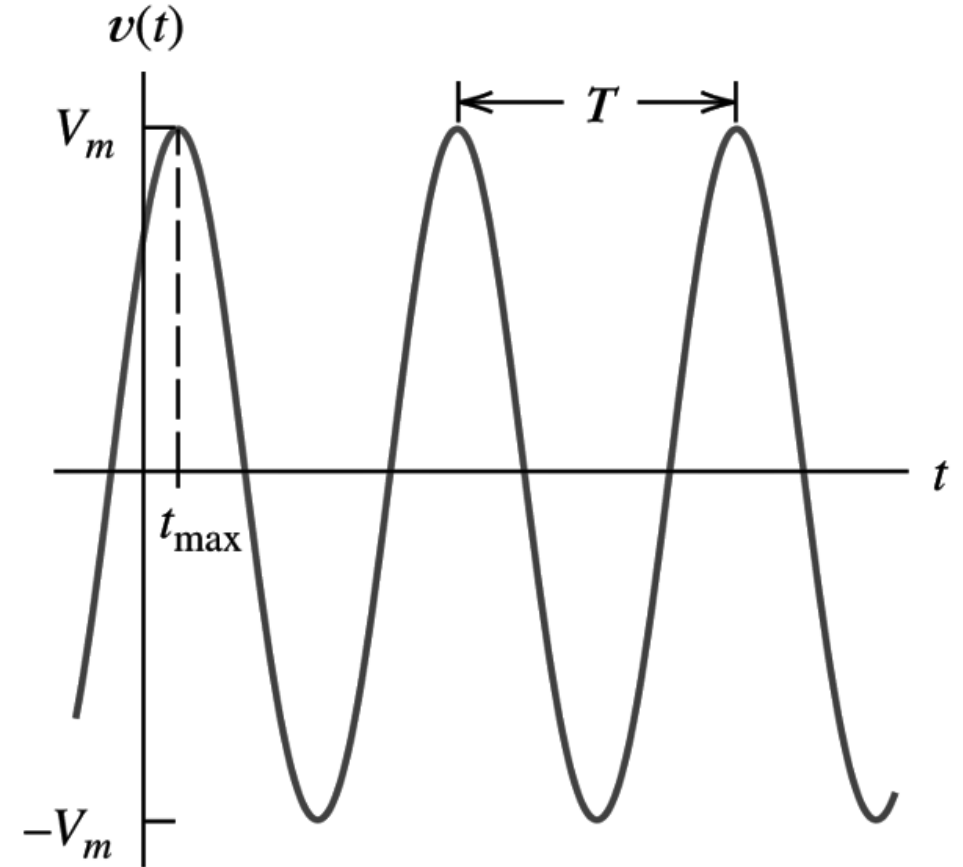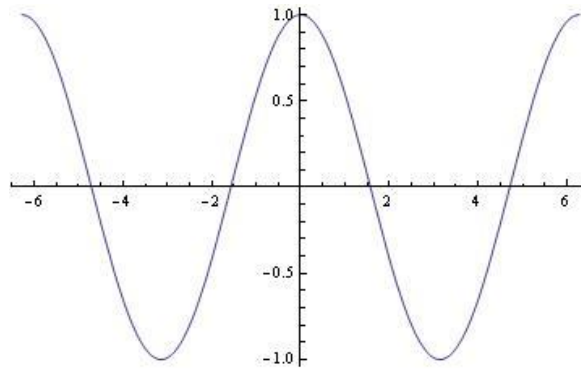- Easily generated using the synchronous generator
- Basic operations: +, -, x, division, differentiation, integration
 - These operations will result in another sinusoid of same frequency and shape
 - Any signal can be represented by a linear combination of sinusoidal waveforms (remember Fourier Series!!!)



Choice of Supply Frequency

- 50 Hz and 60 Hz
- Today :
 - 60 Hz in North America, Brazil and Japan (which also uses 50 Hz!!) etc
 - 50 Hz in other countries
- Exceptions:
 - 25 Hz Railways (Amtrak)
 - $16\frac{2}{3}$ Hz Railways
 - 400 Hz Oil rigs, ships and airplanes
- A too low frequency like 10 Hz or 20 Hz causes flicker
- A too high frequency
 - Increases cable and line impedance
 - Increases the hysteresis losses
 - Increases eddy current losses

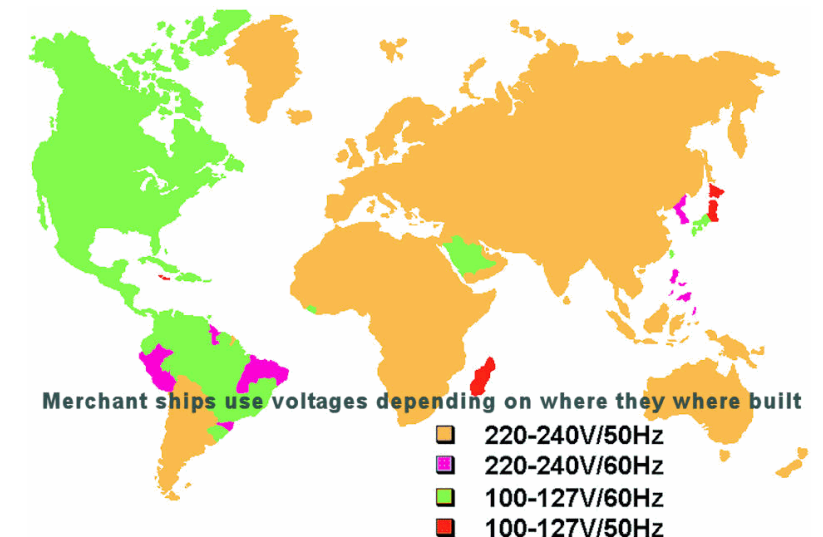



Plot the following curves

- $20 \cos(\omega t - 45^\circ)$


- $35 \sin(\omega t - 135^\circ)$

- $141.2 \cos(\omega t + 45^\circ)$

- $12 \sin(\omega t + 135^\circ)$

How do we represent AC Signals? SINUSOID - NO SINGLE VALUE


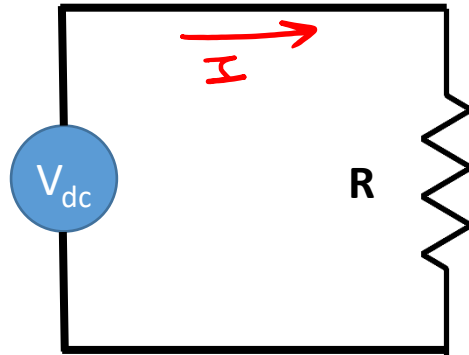
- It is desirable to have same form of equation for power in both a.c. and d.c. circuits mainly because of
 - Convenience
 - Consistence
- For a DC Circuit with a resistance R and voltage source V



$$I_{dc} = \frac{V_{dc}}{R} \quad \text{--- (1)}$$

$$P_{dc} = V_{dc} \cdot I_{dc} \Rightarrow P_{dc} = \frac{(V_{dc})^2}{R} \quad \text{--- (2)}$$

How do we represent AC Signals?

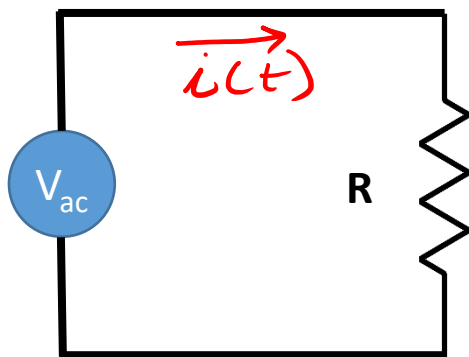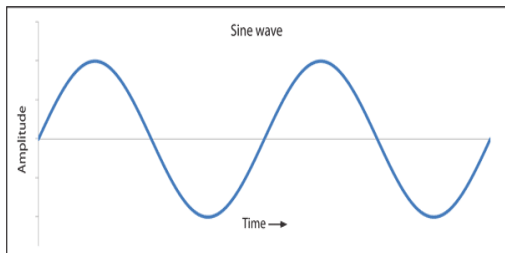

AVERAGE
VALUE = 0


$$i(t) = \frac{V_{ac}}{R}$$

$$V_{ac} = V_m \sin \omega t$$

$$\Rightarrow i(t) = \frac{V_m \sin \omega t}{R}$$

$$= \left(\frac{V_m}{R} \right) \sin \omega t \quad \text{--- (3)}$$
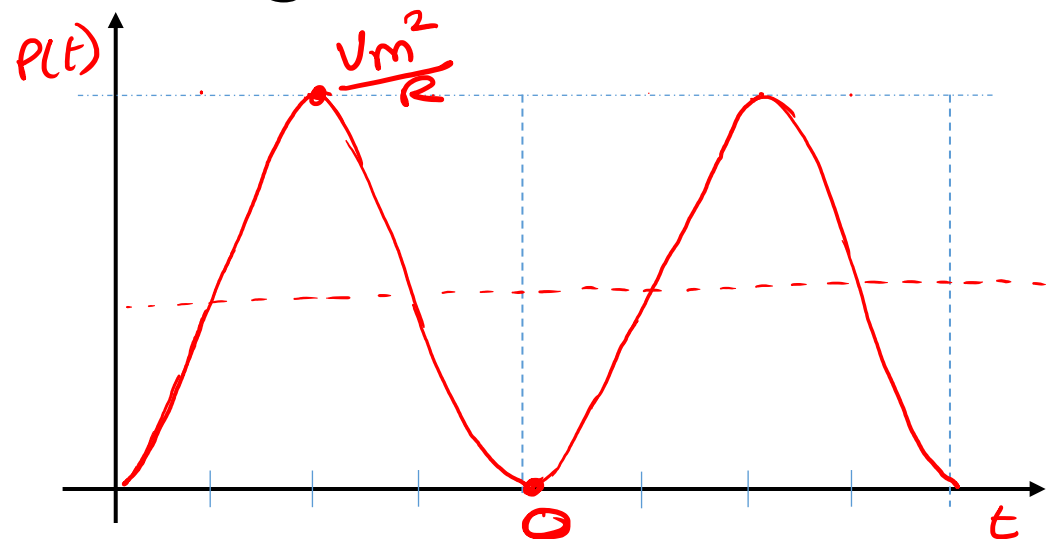
$$P_{ac} = V_{ac} \cdot i(t) = \frac{V_m^2}{R} \sin^2 \omega t \quad \text{--- (4)}$$



$$P_{avg} = \left(\frac{V_m^2}{R} + 0 \right) / 2 = \frac{V_m^2}{2R}$$

$$P_{avg} = \frac{V_m}{\sqrt{2}} \cdot \frac{V_m}{\sqrt{2} R} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}}$$

ROOT MEAN SQUARE OF A SINUSOID

$$\Rightarrow \boxed{P_{ac} = V_{rms} \cdot I_{rms}}$$

RMS values in AC circuits

- The use of the RMS value gives us the DC equivalent AC power equation i.e.


$$P_{ac} = V_{rms} \cdot I_{rms}$$

- An AC voltage source's value is the RMS value by default
 - In Singapore, the voltage supply at households is mentioned as 230V/50Hz

$$V_{rms} = 230V$$

$$\begin{aligned} V_{max} &= \sqrt{2} V_{rms} = \sqrt{2} \cdot 230 \\ &= 325V \end{aligned}$$

A Typical AC circuit Analysis

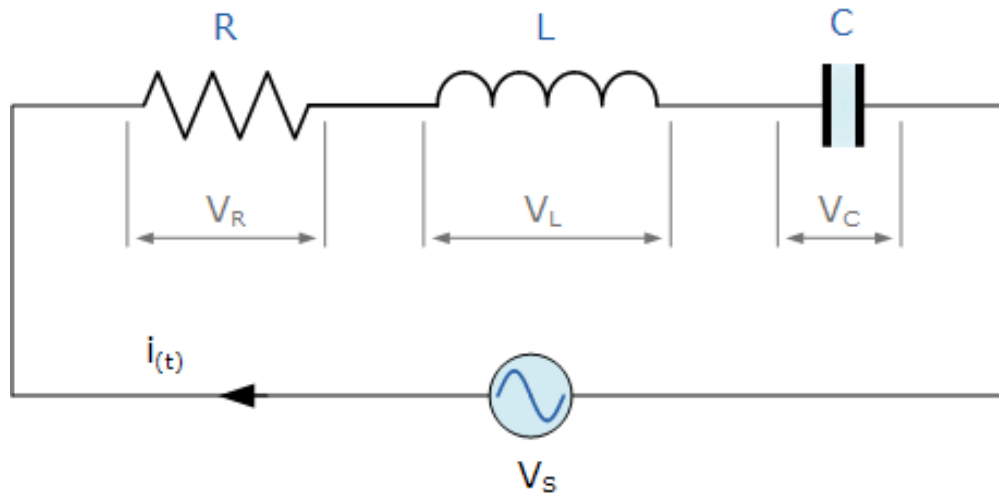

$$V_R = i \cdot R$$

$$V_s = V_m \cos(\omega t + \theta)$$

$$V_L = L \frac{di}{dt}$$

$$V_C = \frac{1}{C} \int i dt$$

KVL FOR THIS CIRCUIT

$$V_s = V_R + V_L + V_C$$

$$V_m \cos(\omega t + \theta) = iR + L \frac{di}{dt} + \frac{1}{C} \int i dt$$



DIFFERENTIAL EQUATIONS?

COMMON PARAMETER - FREQUENCY

PHASE AND AMPLITUDE CHANGE

Phasor Representation of a Sinusoid

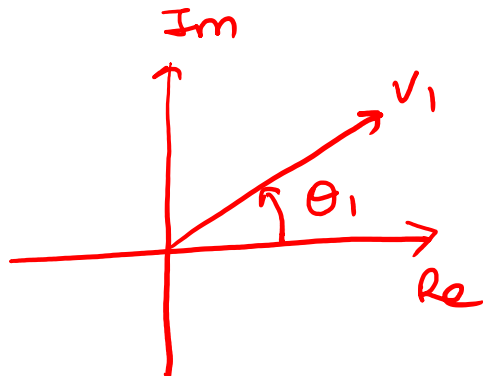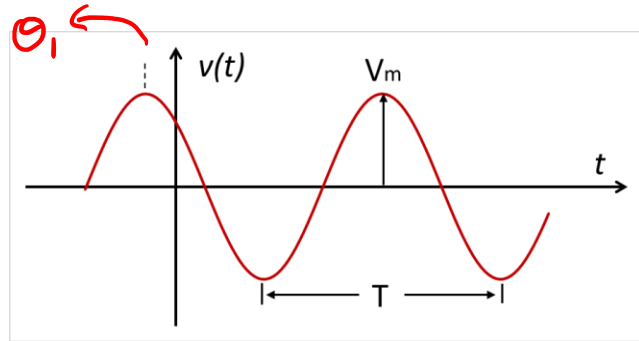- Time Function: $v_1(t) = V_m \cos(\omega t + \theta_1)$
- Phasor: $\mathbf{V}_1 = V_1 \angle \theta_1$, here V_1 is the RMS value of the voltage



$\curvearrowright +$ COUNTER
CLOCKWISE

$\curvearrowleft -$ CLOCKWISE

- Rotating Vector with
 - Length representing the rms value of the waveform
 - Angle representing the phase of the waveform
- The phasor for a sinusoid is a snapshot of the corresponding rotating vector at $t=0$ with its rms values
- Time domain signal is expressed as cosine function



Find and draw the phasors of the following curves



- $20 \cos(\omega t - 45^\circ)$

- $35 \sin(\omega t - 135^\circ)$

- $141.2 \cos(\omega t + 45^\circ)$


- $12 \sin(\omega t + 135^\circ)$

Phase Relationships between Sinusoids

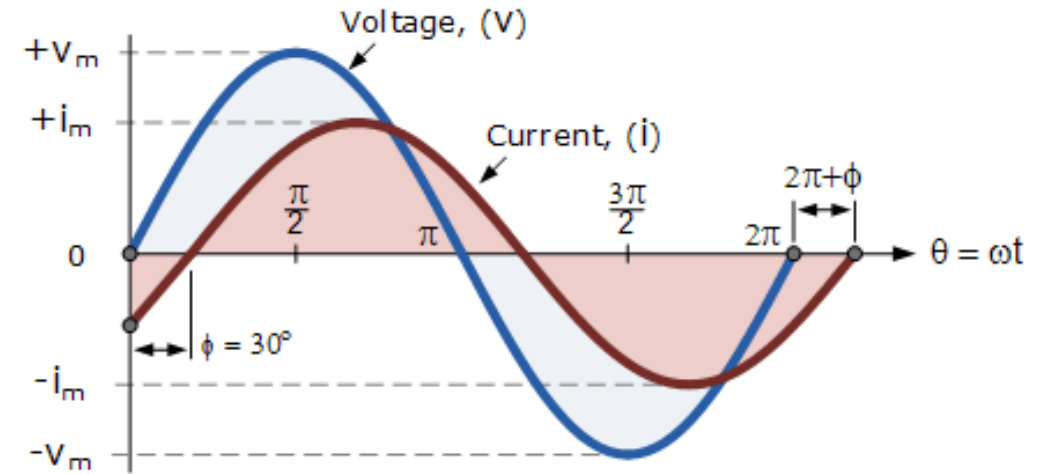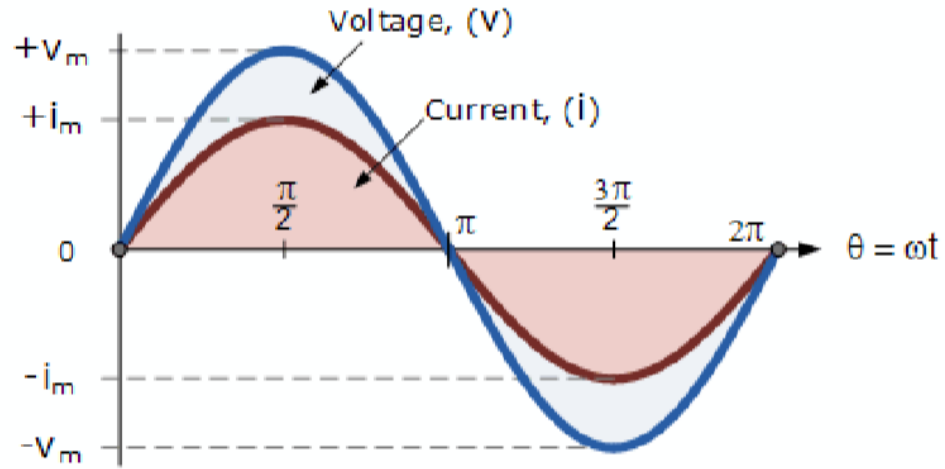


Find and draw the time domain and the phasor of the $141.2 \cos(\omega t - 90^\circ)$, $70.7 \sin(\omega t - 30^\circ)$ & $100 \cos(\omega t + 30^\circ)$ curves on the same axis!!!

- Time domain

 










- Phasors!!!

 

Impedance → Complex Resistance

- *DC: Resistance (R) = $\frac{\text{Voltage (V)}}{\text{Current (I)}}$*
- *AC: Impedance (Z) = $\frac{\text{Voltage Phasor (V)}}{\text{Current Phasor (I)}}$*


Time ↔ Phasor

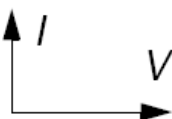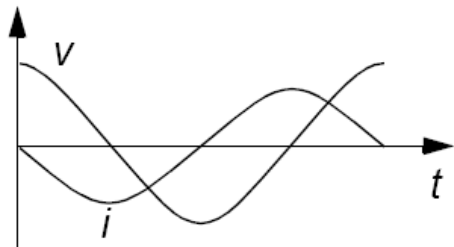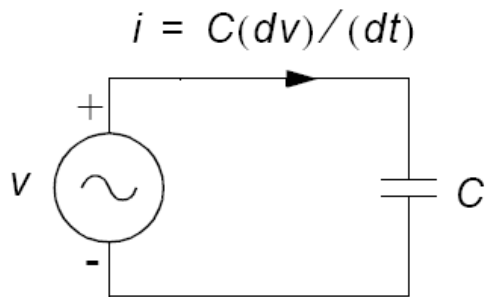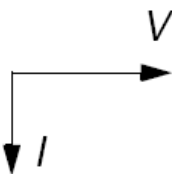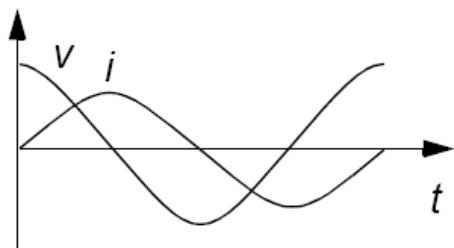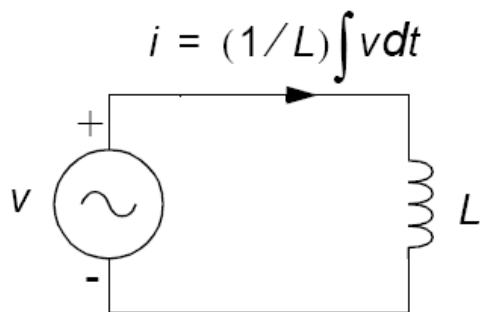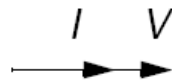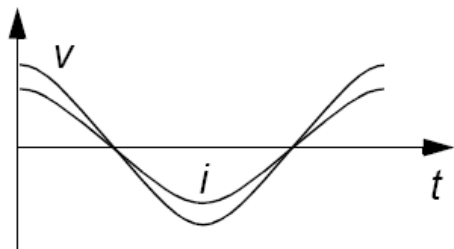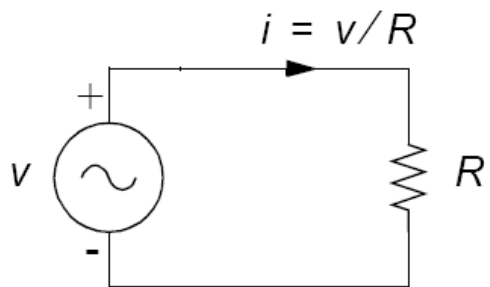


Element	Voltage	Current	Impedance
R			
L			
C			

Complex Impedance

- RL Load

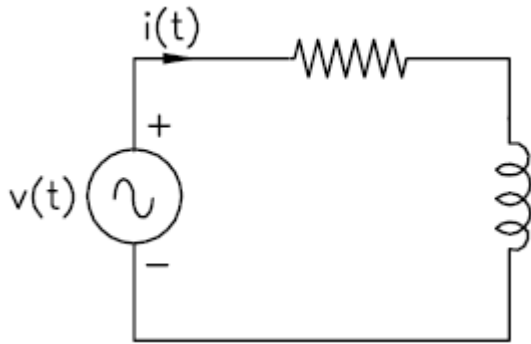


- RC Load

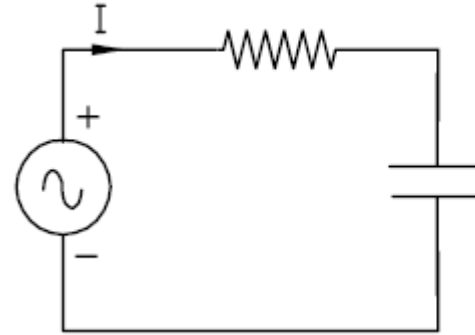


Series RLC Circuit

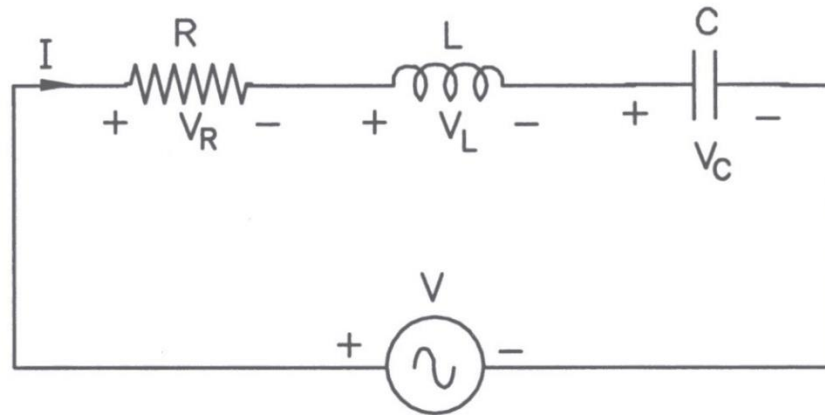- Find the impedance of the following circuit. Draw the impedance diagram. What is the current if $Z_L = Z_C$?



Series RLC Circuit

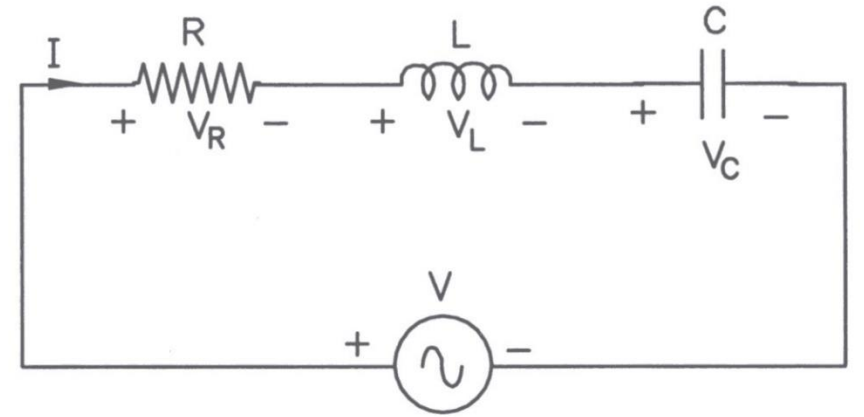



Voltage Phasors and KVL