

11.1 Per Unit Analysis - Examples

Tuesday, 29 March 2022 11:33 am



Steps of 1Φ Per Unit Analysis

1. Choose $S_B^{1\Phi}$ for the system.
2. Select V_B for different zones (usually follows transformer voltage ratings).
→ Choose or given V_B for one of the zones
→ calculate V_B for other zones using transformer ratio.
3. Calculate Z_B for different zones.
→ $Z_B = \frac{V_B^2}{S_B}$
4. Express all quantities in p.u.
4.1
5. Draw impedance diagram and solve for p.u. quantities.
6. Convert back to actual quantities if needed.


→ 4.1 → Find new p.u. impedance values if manufacturer has given impedance in p.u. instead of ohms.

13

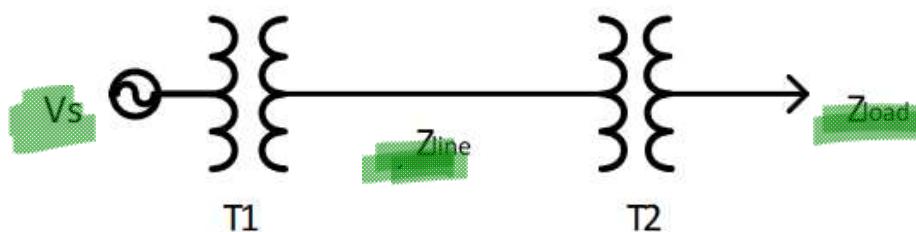
- d) Draw the per unit impedance diagram for the following single-phase system and find out the load voltage and load power consumed using per unit analysis. Use a power base of 10MVA.

(10 marks)

T1: 12 MVA, 12kV/180kV, Leakage Reactance: 5%, $\rightarrow Z_{T1} = 0.05 \text{ pu}$
T2: 8 MVA, 160kV/80kV, Leakage Reactance: 12%, $\rightarrow Z_{T2} = 0.12 \text{ pu}$
Line Impedance $Z_{line} = 128 + j256 \Omega$
Load Impedance $Z_{load} = 1024 \Omega$
 $V_S = 8 \text{kV}$



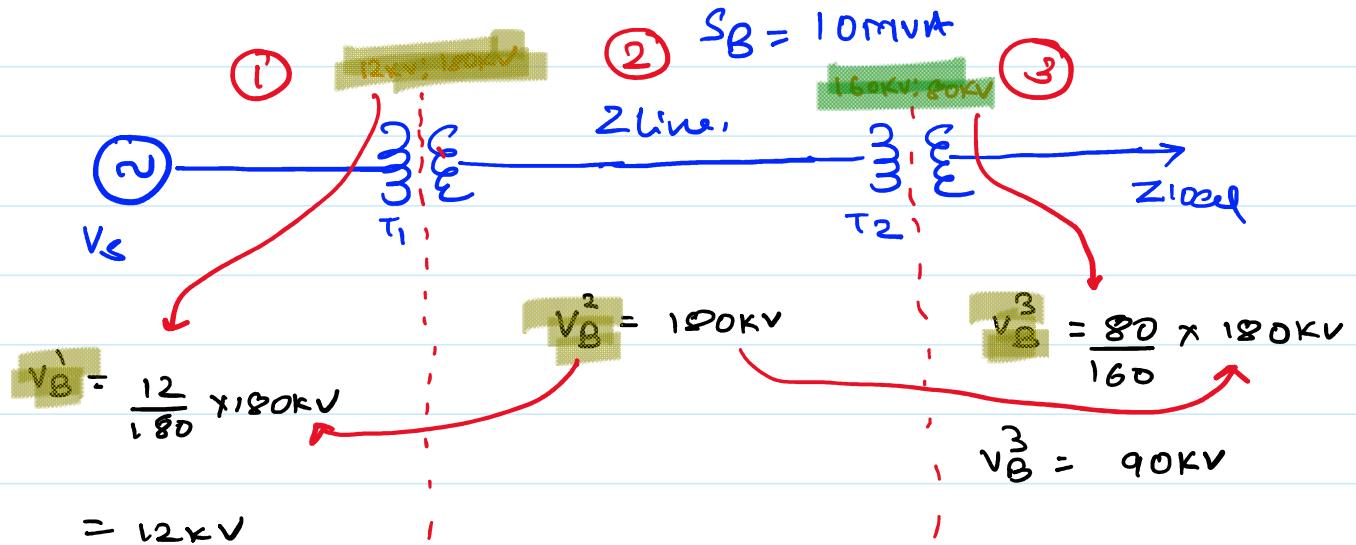- a) Per Unit Impedance Diagram
 - b) ✓ Load Voltage
 - c) ✓ Load Power



$$Z_B = \frac{(V_B)^2}{S_B}$$

$$= \frac{(12 \times 10^3)^2}{10 \times 10^6}$$

$$= 14.4 \Omega$$

$$z_B^2 = \frac{(180 \times 10^3)^2}{10 \times 10^6}$$

$$z_B = \frac{(90\pi \cdot 10^3)^2}{10\pi \cdot 10^6} = 810 \Omega$$

$$V_{S,pu} = \frac{8KV}{12KV}$$

$$= 0.6667L$$

$$= 0.6667L$$

$$Z_{linepu} = \frac{128 + j256}{3240}$$

$$= 0.0395 + 0.079 j$$

$$= 0.823 \angle 63.43^\circ \text{ p.u.}$$

$$Z_{\text{bond, p.u.}} = \frac{1024}{810}$$

\Rightarrow Transform change in Base Value

Transform T_1

12 MVA, 12 kV / 180 kV

$$Z_{T_1\text{dig}} = j0.05 \text{ p.u.}$$

$$Z_{T_1, \text{old}} = j 0.05 \text{ p.u.}$$

$$Z_{\text{Actual}} = \frac{Z_{B, \text{old}}^T \times Z_{T_1, \text{old}}}{12 \text{ kV}^2 / 12 \text{ MVA}}$$

$$\begin{aligned} Z_{T_1, \text{new}}^{\text{pu}} &= \frac{Z_{B, \text{old}}^T \times Z_{T_1, \text{old}}^{\text{pu}}}{Z_B'} \xrightarrow{\text{Base using transformer ratings}} \\ &= \frac{j 0.05 \times \frac{(12 \times 10^3)^2}{12 \times 10^6}}{14.4} \rightarrow \frac{(V_{B, \text{old}}')^2}{(S_{B, \text{old}})} \\ &= j 0.042 \text{ p.u.} \end{aligned}$$

$$Z_{\text{pu}}^{T_1, \text{new}} = \frac{Z_{\text{Actual}}^T}{Z_B'}$$

Transformers T_2

8 MVA, 160 kV / 80 kV


$$12\% \rightarrow Z_{T_2} = j 0.12 \text{ p.u.}$$

Primary of T_2 is in zone ②

$$\begin{aligned} Z_{\text{pu}, T_2}^{\text{new}} &= \frac{Z_{B, \text{old}}^{\text{primary}} \times Z_{\text{pu}}^{\text{old}}}{Z_B'^2} \\ &= \frac{(160 \times 10^3)^2}{8 \times 10^6} \times j 0.12 \\ &\quad \underline{\hspace{10em}} \\ &= j 0.118 \text{ p.u.} \end{aligned}$$

Per unit impedance diagram

Per unit impedance diagram

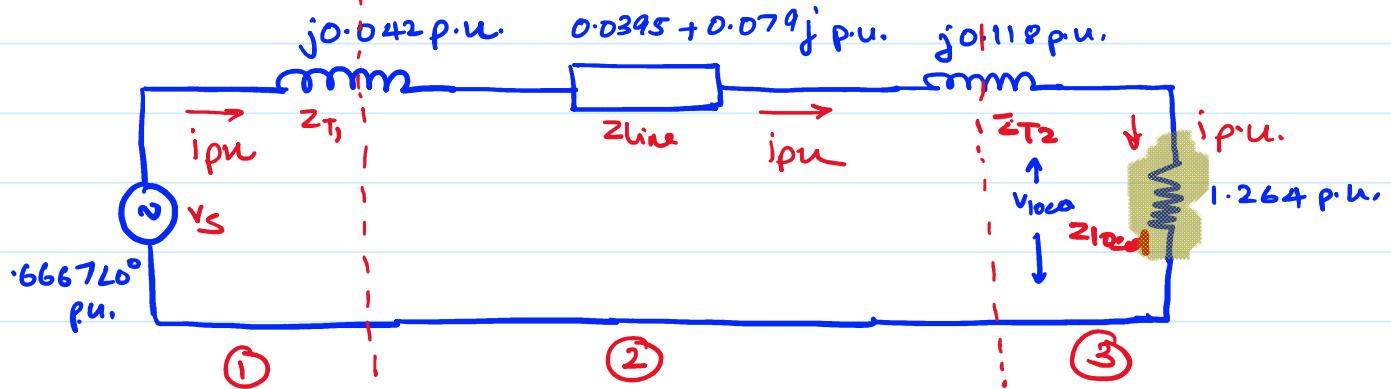

$$I_{pu} = \frac{V_{s, pu}}{Z_{Total, pu.}} = \frac{0.6667 L 0^\circ}{j0.042 + j0.118 + 1.264 + 0.0395 + j0.079}$$

$$= \frac{0.6667 L 0^\circ}{1.325 L 10.39^\circ}$$

$$I_{pu.} = 0.5031 L -10.39^\circ \text{ p.u.}$$

$$V_{load\ pu} = I_{pu} \times Z_{load\ pu}$$

$$= 0.5031 L -10.39 \times 1.264$$

$$= 0.6359 L -10.39^\circ \text{ p.u.}$$

$$S_{load\ pu} = (V_{load\ pu})(I_{pu}^*)$$

$$= (0.6359 L -10.39)(0.5031 L -10.39)^*$$

$$= (0.6359 L -10.39)(0.5031 L 10.39)$$

$$S_{load\ pu} = 0.3199 L 0^\circ \text{ p.u.}$$

$$V_{load} = V_{load\ pu} \times V_B$$

$$= 0.6359 L -10.39 \times 90 \times 10^{-3}$$

$$= 57.221 L -10.39^\circ \text{ V.V}$$

$$= 0.6359 L - 10.39 \times 90 \times 10^{-3}$$

$$= 57.231 L - 10.39^\circ \text{ kV}$$

$$S_{load} = S_{load, \text{pu}} \times S_B$$

$$= 0.3199 L 0^\circ \times 10 \times 10^6$$

$$= 3.199 L 0^\circ \text{ MVA}$$

$$P_{load} = 3.199 \text{ MW}$$

$$\downarrow$$

$$S = P + j Q$$

$$= |S| \cos \theta + j |S| \sin \theta$$

Casio → fx-991MS

fx-991ES



Steps of Calculation: 3Φ Case

1. Choose $S_B^{3\Phi}$ for the system.
2. Select $V_B^{\text{line-to-neutral}}$ or $V_B^{\text{line-to-line}}$ for different zones.
3. Calculate Z_B for different zones.
4. Express all quantities in p.u.
5. Draw impedance diagram and solve for p.u. quantities.
6. Convert back to actual quantities if needed.

Note that the **per unit circuit** is the circuit in **per-phase analysis** with normalization of the voltage magnitude at different locations. This means that the **phase of voltage** in per unit analysis **refers to the line-to-neutral voltage**.


- b) Draw the per unit impedance diagram for the following three-phase system and find out the voltage across the transmission line and the transmission line losses using per unit analysis. Use a power base of 10MVA. Find out the voltage across the transmission line.

T₁: 14 MVA, 11kV/220kV, Leakage Reactance: 7%, Y-Δ

T₂: 7 MVA, 240kV/120kV, Leakage Reactance: 14%, Δ- Y

Line Impedance $Z_{\text{line}}: 140+j280 \Omega$

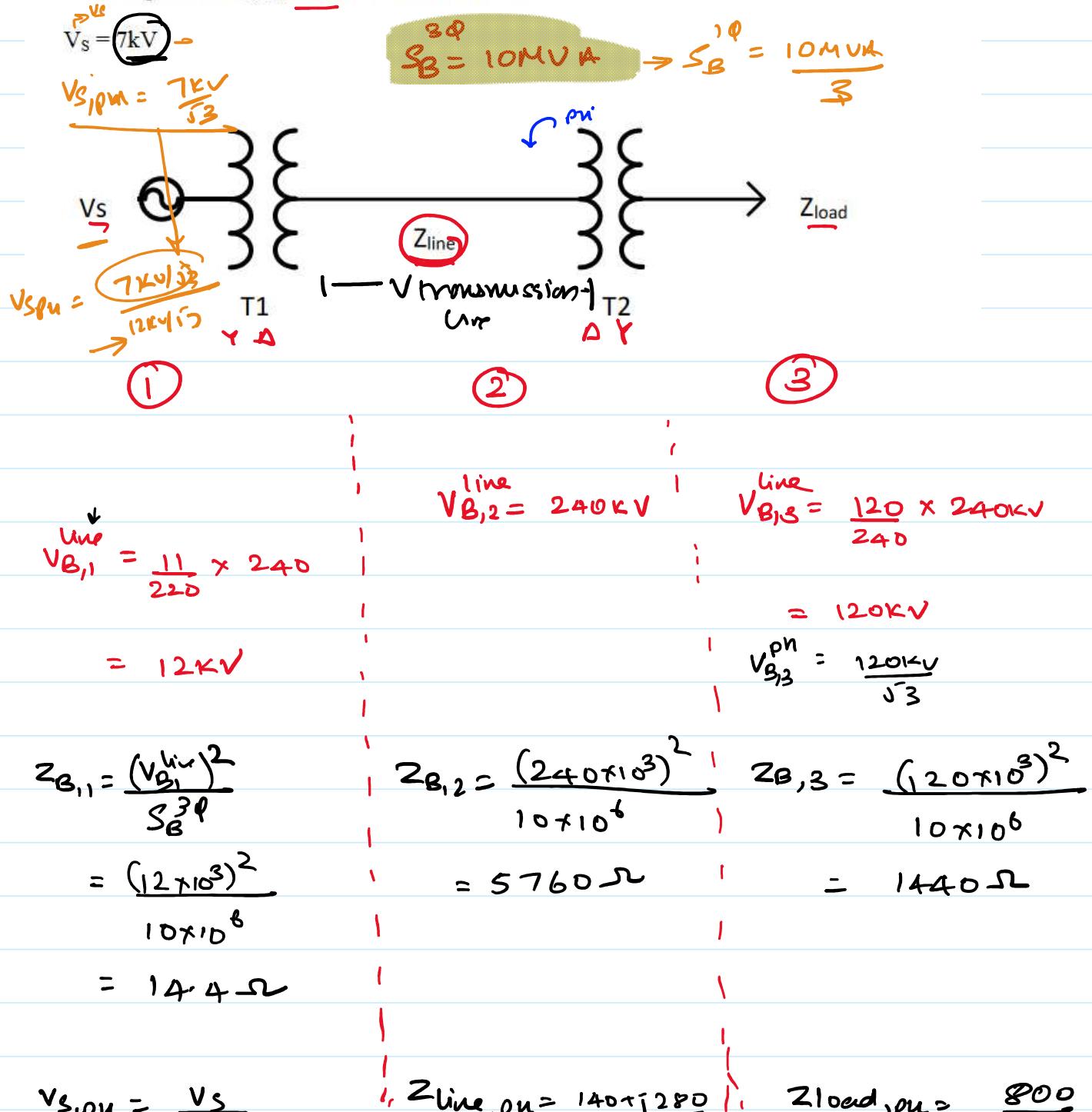Load Impedance $Z_{\text{load}}: 800 \Omega$ Y connected load



$$V_{S,pu} = \frac{V_S}{V_{B,1}}$$

$$= \frac{7}{12}$$

$$= 0.5833 \angle 0^\circ \text{ p.u.}$$

$$Z_{\text{line},pu} = \frac{140 + j280}{5760}$$

$$= 0.0243 + j0.0486 \text{ p.u.}$$

$$= 0.0543 \angle 63.43^\circ \text{ p.u.}$$

$$Z_{\text{load},pu} = \frac{800}{1440}$$

$$= 0.556 \text{ p.u.}$$

→ Transformer change of base values.

Transformer T₁

14MVA, 11kV / 220kV, $Z_{T_1,old}^{pu} = j0.07 \text{ p.u. Y-A.}$

$$Z_{T_1,new} = \frac{Z_{actual}^{T_1}}{Z_B^1}$$

$$= \frac{Z_{pu,old}^{T_1} \times Z_{B,old}^{T_1,prim}}{Z_B^1}$$

$$Z_{B,old}^{T_1,prim} = \frac{V_{B,old}^{prim}}{S_{B,old}} = \frac{(11 \times 10^3)^2}{14 \times 10^6}$$

$$Z_{T_1,new} = \frac{j0.07 \times \frac{(11 \times 10^3)^2}{14 \times 10^6}}{14 \cdot 4}$$

$$= j0.042 \text{ p.u.}$$

Transformer T₂

7MVA, 220kV / 120kV, $Z_{T_2} = j0.14 \text{ p.u. } \Delta Y$

$$Z_{T2, \text{new}} = \frac{\underline{Z_{\text{actual}}}}{\underline{Z_B^2}}$$


$$= \frac{Z_{T2, \text{old}} \times Z_{B, \text{old}}^{T_2, \text{primary}}}{Z_B^2}$$

$$Z_{B, \text{old}}^{T_2, \text{primary}} = \frac{(240 \times 10^3)^2}{7 \times 10^6}$$

$$Z_{T2, \text{new}} = \frac{j 0.14 \times \frac{(240 \times 10^3)^2}{7 \times 10^6}}{5760}$$

$$= j 0.2 \text{ p.u.}$$

Per unit impedance diagram

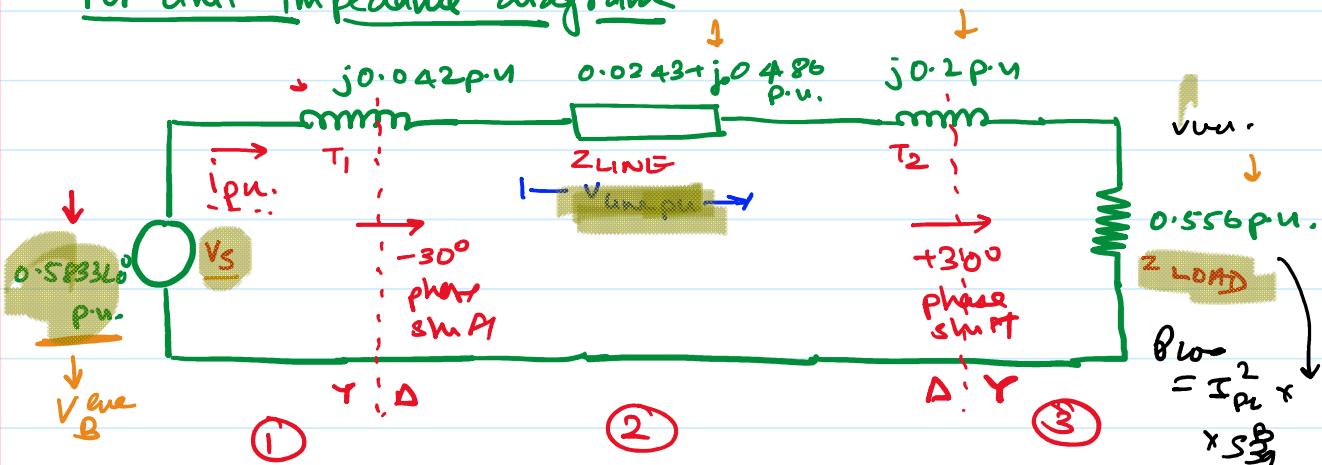

$$i_{pu} = \frac{V_{pu}}{Z_{Total \text{ p.u.}}} = \frac{0.5833 \angle 0^\circ}{j 0.042 + j 0.2 + 0.0243 + j 0.486 + 0.556}$$

$$= \frac{0.5833 \angle 0^\circ}{0.649 \angle 26.60^\circ} = 0.8988 \angle -26.60^\circ \text{ p.u.}$$

$$i_{pu} \approx 0.8988 \angle -26.60^\circ \text{ p.u.}$$

$$i_{pu} \approx 0.8988 \angle -26.60^\circ \text{ p.u.}$$

$$i_{pu,gen} = 0.8988 \angle -26.60^\circ \text{ pu.}$$

$$\begin{aligned} i_{pu,line} &= 0.8988 \angle -26.60^\circ - 30^\circ \\ &= 0.8988 \angle -56.60^\circ \text{ pu.} \end{aligned}$$

$$i_{pu,load} = 0.8988 \angle -26.60^\circ \text{ pu.}$$

$$V_{pu,line} = i_{pu,line} + Z_{line} pu$$

$$\begin{aligned} &= 0.8988 \angle -56.60^\circ \times 0.0543 \angle 63.43^\circ \\ &= 0.0488 \angle 6.83^\circ \text{ p.u.} \end{aligned}$$

$$\begin{aligned} P_{line}^{pu} &= (I_{line}^{pu})^2 (R_{line}^{pu}) \\ &= 0.8988^2 \times 0.0243 \\ &= 0.0196 \text{ p.u.} \end{aligned}$$

$$\begin{aligned} P_{line} &= 0.0196 \times S_B^{30} \\ &= 196.305 \text{ kW} \end{aligned}$$

$$S_{line}^{pu} = (V_{pu,line})(I_{pu,line})$$

$$\begin{aligned} &= 0.0488 \angle 6.83^\circ \times 0.8988 \angle 56.60^\circ \\ S_{line}^{pu} &= 0.0196 + 0.037j \text{ p.u.} \end{aligned}$$

↓ ↓
P_{pu,line} Q_{pu,line},

$$P_{line}^{30} = 0.0196 \times 10 \times 10^6 = 196.305 \text{ kW},$$


$$P_{\text{line}} = 0.0196 \times 10 \times 10^6 = 196.305 \text{ kW}$$

$$V_{\text{pu, line}} = 0.0498 \angle 6.83^\circ$$

$$|V_{\text{transmission line}}| = 0.0498 \times \frac{240 \text{ kV}}{\sqrt{3}}$$

$$= 6761.93 \text{ V}$$
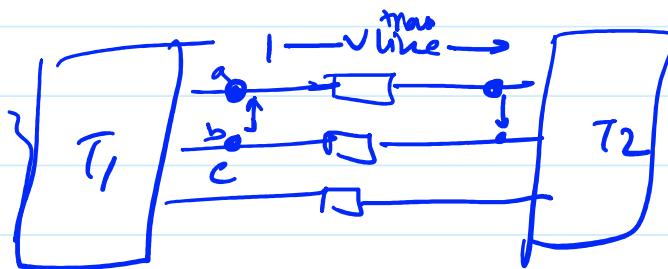
$$V_{B, \text{line}}^2 = V_{B, \text{phase}}^2 = \frac{V_{B, \text{line}}^2}{\sqrt{3}}$$



$$S_B = 3 S_{1, \text{ph}}$$

$$i_B = \frac{S_B^{3\phi}}{\sqrt{3} V_{\text{line-to-line}}}$$

$$S = \sqrt{3} V_{\text{line}} \cdot I_{\text{line}}$$

$$S = 3 V_{\text{ph}} \cdot I_{\text{ph}}$$

$$I_{\text{ph}} = \frac{S_{1, \text{ph}}^{3\phi}}{3 \cdot V_{\text{ph}}}$$

$$Z_B = \frac{V_{\text{ph}}}{\frac{S_{1, \text{ph}}^{3\phi}}{3 \cdot V_{\text{ph}}}} = \frac{V_{\text{ph}}^2}{S_{1, \text{ph}}^{3\phi}}$$

$$Z_B = \frac{3 V_{\text{ph}}^2}{S_{1, \text{ph}}^{3\phi}}$$

$$= \frac{(f_3 V_{ph}^B)^2}{S_{3d}^B}$$

$$Z_B = \frac{(V_{ph}^B)^2}{S_{2d}^B}$$

$$I_{load, ph} = \text{--- p.u.}$$

$$Z_{line} = \text{--- p.u.}$$

$$S_{load, ph} = V \cdot I^R = \underline{\underline{Z}} \quad \text{p.u.}$$

$$I_{load} = I \cdot Z^R \cdot Z$$

$$S_{load}^{3d} = \frac{S_{load, ph}}{Z} \times S_{3d}^B =$$

$$S_{load}^{1\phi} = S_{load, ph} \times S_{1\phi}^B$$