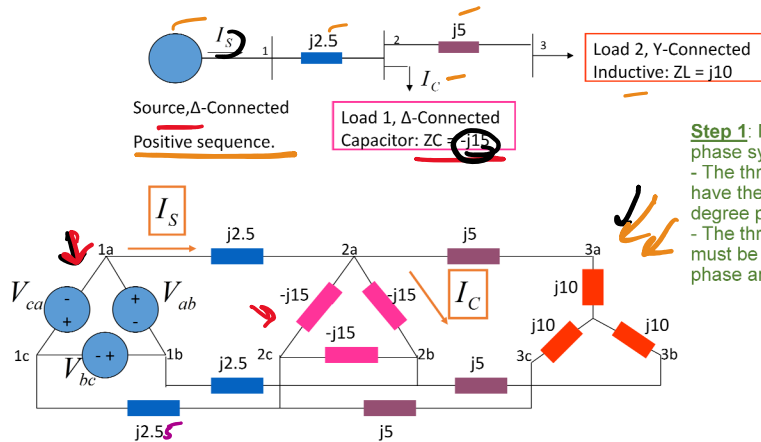


4.1 3- Phase Power : In-Class Zoom Notes

Tuesday, 2 February 2021 11:58 am

Example: Given a one-line diagram, If the voltage source is $|V_{line}| = \sqrt{3} V$. Find, the current magnitude supplied by source, $|I_S|$, and, the current magnitude through a capacitor, $|I_C|$.



Step 1: Make sure that the three-phase system is balanced.

- The three-phase sources need to have the same magnitude with 120 degree phase difference.
- The three-phase impedances must be of the same value (both phase and magnitude).


2)a) Convert From $\Delta \rightarrow Y$


$$Z_{\Delta} \rightarrow Z_Y$$

Load 1 \rightarrow Δ connected load $Z_{\Delta} = -j15'$


$$\Delta \rightarrow Y \text{ load, } Z_Y = \frac{Z_{\Delta}}{3} = \underline{\underline{-j5 \Omega}}$$

b) Convert Voltage From Δ to Y line voltage = $|\sqrt{3}| V$

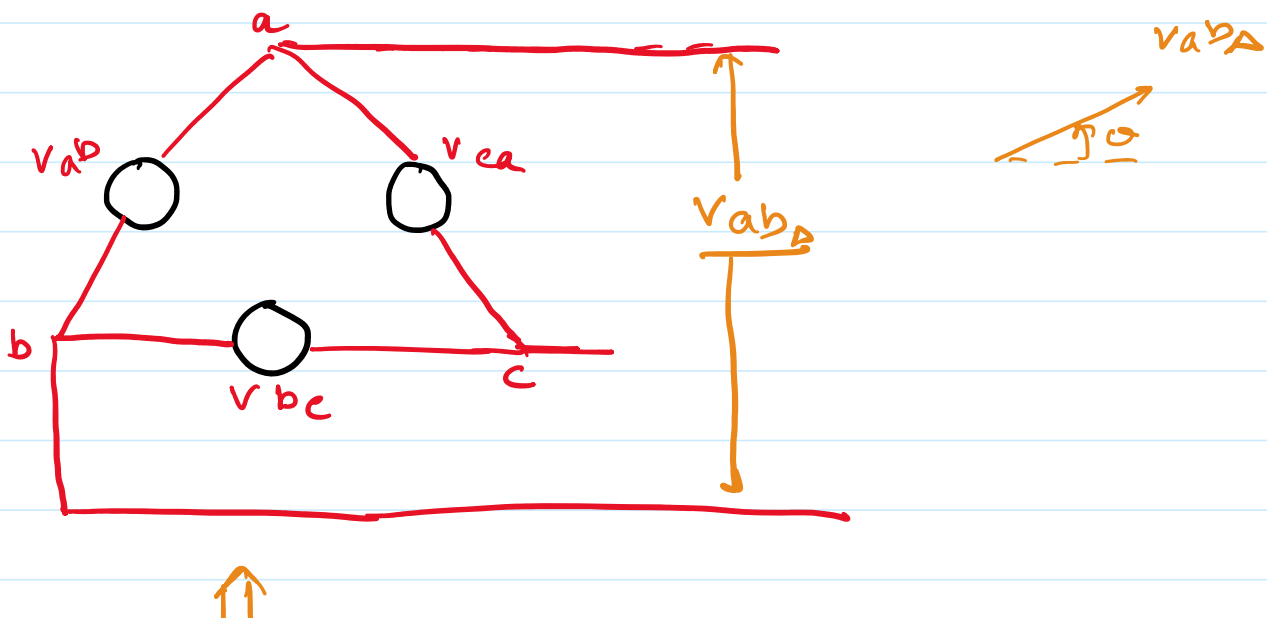

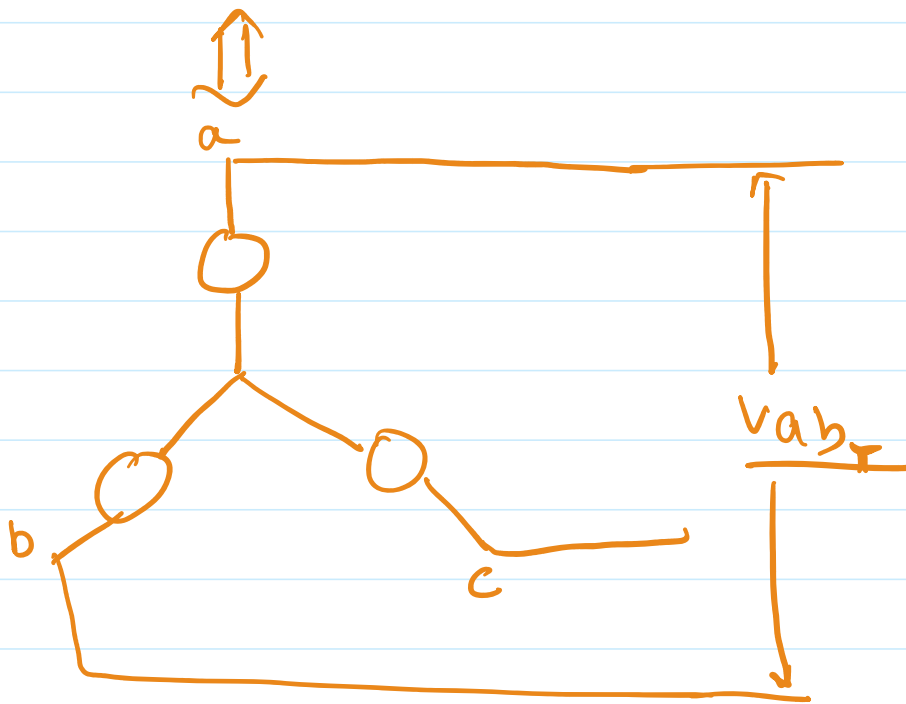
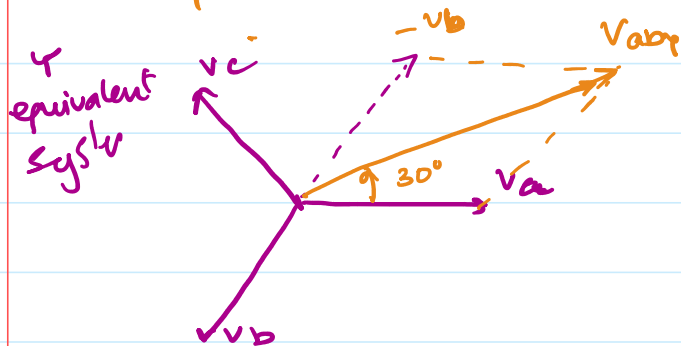
$$V_{ab\gamma} = V_a - V_b = V_a + (-V_b)$$



$$\begin{aligned} V_{ab\gamma} &= V_a + (-V_b) \\ &= V_a + V_a \angle 60^\circ \end{aligned}$$

$$V_{ab\Delta} = |\sqrt{3}| \angle 0^\circ$$

$$V_{ab\gamma} = \sqrt{3} V_a \angle 30^\circ \quad \text{--- (A)}$$

$$V_{ab\gamma} = V_{ab\Delta} \quad \text{--- (B)}$$

$$\sqrt{3} V_a \angle 30^\circ = V_{ab\Delta}$$

$$\begin{aligned} V_a &= \frac{V_{ab\Delta}}{\sqrt{3} \angle 30^\circ} \\ &= \sqrt{3} \angle 0^\circ \end{aligned}$$


$$\frac{43 \angle 30^\circ}{\frac{\sqrt{3} \angle 0^\circ}{\sqrt{3} \angle 30^\circ}}$$

$$V_a = 1 \angle (-30^\circ)$$


Assuming $V_{ab\Delta}$ angle ($\theta = 0^\circ$)

$$\underline{V_a = 1 \angle -30^\circ}$$

Drawing the 1-phase diagram

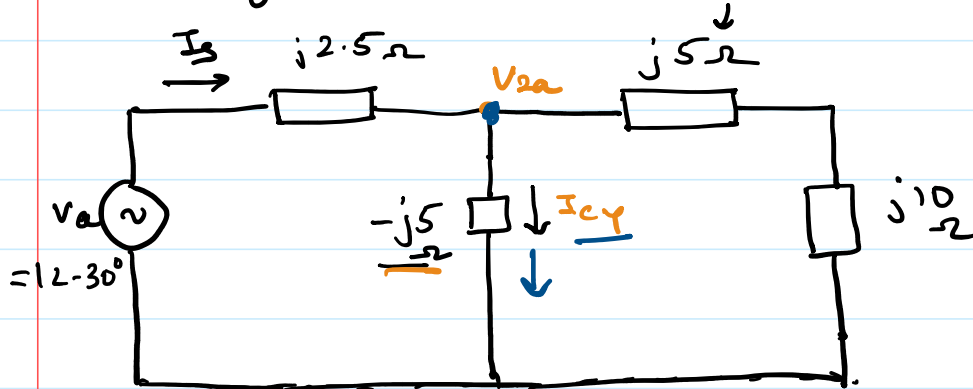

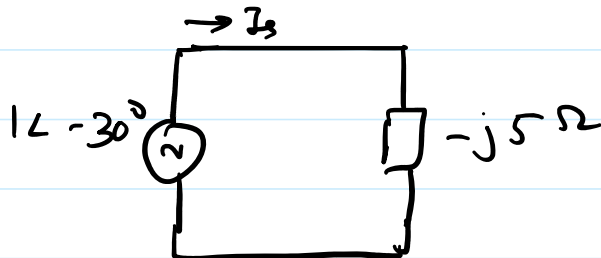
$$\begin{aligned} Z_{eq} &= (j5 + j10) \parallel -j5 + j2.5 \\ &= (j15 \parallel -j5) + j2.5 \\ &= -j5 \Omega \end{aligned}$$




$$\begin{aligned} I_s &= \frac{1 \angle -30^\circ}{-j5} = \frac{1 \angle -30^\circ}{5 \angle -90^\circ} \\ &= 0.2 \angle 60^\circ \text{ A} \end{aligned}$$

$$|I_s| = 0.2 \text{ A}$$

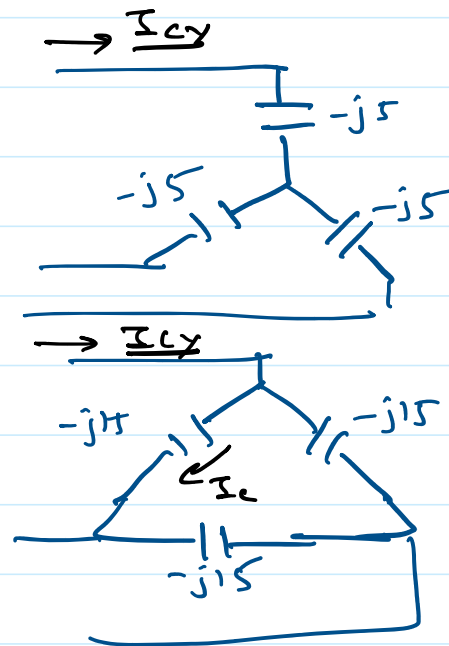
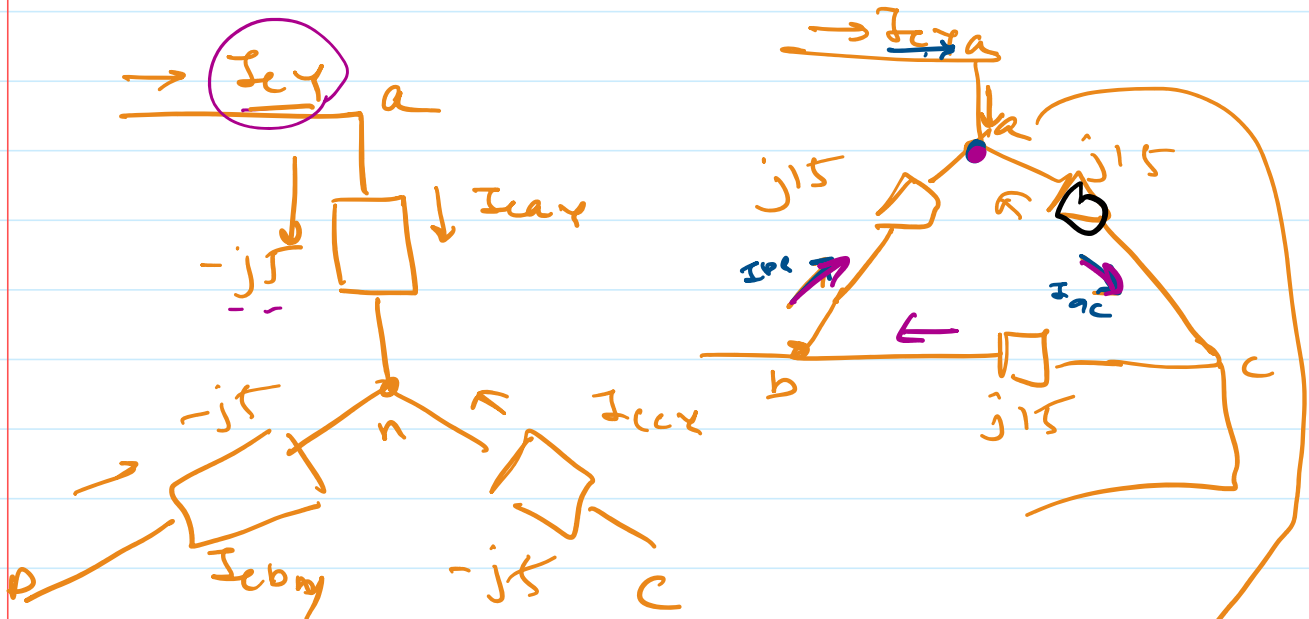
$$\begin{aligned}
 I_{cy} &= \frac{V_{2a}}{-j5} = \frac{V_a - I_s(j2.5)}{-j5} \\
 &= \frac{1 \angle -30^\circ - 0.2 \angle 60^\circ (2.5 \angle 90^\circ)}{5 \angle -90^\circ} \\
 &= \frac{1.5 \angle -30^\circ}{5 \angle -90^\circ} = \underline{0.3 \angle 60^\circ \text{ A}}
 \end{aligned}$$



$$I_{cy} + I_{ba} = I_{ac} \quad (\text{Apply KCL @ } a)$$

$$I_{cy} = I_{ac} - I_{ba}$$

$$\Rightarrow \underline{I_{ac}} = \frac{I_{cy}}{\sqrt{3} \angle -30^\circ}$$

$$I_{ac} = I_c = \frac{0.3 \angle 60^\circ}{\sqrt{3} \angle -30^\circ}$$

$$I_c = \left| \frac{\sqrt{3}}{10} \right| \angle 90^\circ \text{ A.}$$

$$\underline{\underline{|I_c| = \frac{\sqrt{3}}{10} \text{ A}}}$$

$$3(V_c \cdot I_c^*) = \dots \rightarrow -j15$$

$$I_{ab} - I_{ca} = \sqrt{3} I_{ab} \angle -30^\circ$$

$$I_{ac} - I_{ba} = \sqrt{3} I_{ac} \angle -30^\circ$$