Matric number: A01998062 R=06=61 C= (019) X2 = 38 MF $\approx \frac{230}{6-1486\cdot31579} \approx \frac{230}{486\cdot3528} \frac{20^{\circ}}{200}$ ≈ 0.4729289.29314° = 0.473289.3°A (3s.f.) b. 1c=12=1R=1= 0.4729 L89.29314°=0.473489.3°A Vs = 230 LO°V $V_c = I_c(-\frac{3}{400}) = (0.4729189.293/4°)(\frac{50\times38\times10^{-6}}{50\times38\times10^{-6}})$ = 24912-0.707° V (354) $V_1 = I_1(j_0 \chi L) = (0.4729189.29314°)(j_50 \chi 0.8) = 18.9 L 179° V (3s.f.)$ $V_R = I_R R = (0.4729189.29314°)(6) = 2.84189.3° V (3s.f.)$ 1c=1c=1g=1s 1790

C. I is max when 7 is min and 7 = Rt jwc t jw2

is min when

jwc t jw2=0

jwc = jw2

jwc = jw2 $\omega^{2} 2C = 1$ $\omega = \sqrt{\frac{1}{2C}} = \sqrt{\frac{1}{0.8(38 \times 10^{-6})}}$ = 181 Hz (3s.f.)

2 Minter Number A0194806L

Number 18: e0406737

A = 87 X2 = 124 kW

B = 0.7

a. Virginity =
$$\frac{|V_{lorize}|}{\sqrt{3}}$$
 20° = $\frac{420}{\sqrt{3}}$ 20°
 $\approx 242^{\circ}$ 48720° V

Local | $\frac{23^{\circ}}{24^{\circ}}$ = $\frac{15620^{\circ}}{\sqrt{3}}$ = 5620° 2
 $1_{1} = \frac{V_{lorize}}{24^{\circ}}$ = $\frac{15620^{\circ}}{5620^{\circ}}$ = $48.49742 - 20^{\circ}$ A

Significant Significa

Z= 6+8; 12 = 10253.13° 12 12 = Vive-neutral - 242.48760°
Z2 10653.13° - 24.2487 L-53.13° A Szc. 2 = 3 / Mire-neutral 12 = 3 (242.48.7 20°) (24. 248.7 653.13°) ≈ 17-63998 253.13° KVA 1530,21 = 17.6 KVA (35.4) 0 = 53.1° (3s.1) P30,2 = 17.63998 (05(53.13°) = 10.6 kW (3s.1) Q3012 = 17-63998 ain (53.13°) = 14.1 kvar (3s.f.) 15,2/=17.6 KVA Q30,2 = 14.1 kvar Bos = 10. (kw

Loads P30,3 = 174/cw P. S = 0.7 0 = cos' 0.7 ~ 45.573° = 45.6° (35.f.) Q36,3 P36,3 tand = 174 tan(45.573°) ~ 177.5155 k var = 178 kvar (3s.f.) |S30,3| = 1742 + 177.51552 = 248 KVA (3s.f.) 15,31 = 248 kVA 20,3 = 178 kvar 45.6° 130,3= 174kW

$$Q_S = Q_{30,1} + Q_{30,2} + Q_{30,3} = |2.1 + |4.1 + |78$$

= 204.2 kvor

$$S_s = \sqrt{217.8^2 + 204.2^2} \ L \ ton^{-1} \left(\frac{204.2}{217.8} \right)$$

$$Q_{C,30} = -Q_s = -204.2 \text{kvar}$$

$$X_{c,10} = \frac{1 \text{ Vine-line } 1^2}{Q_{c,10}} = \frac{420^2}{-68-06667 \times 10^3} \approx 2.591577\Omega$$