

EE2029 – Introduction to Electrical Energy Systems (Tutorial #1 AC Fundamentals)

(Tutorial #1 solutions)

Solution Q1:

$$(a) V_1 = \frac{40}{\sqrt{2}}\angle -90^\circ + \frac{60}{\sqrt{2}}\angle -45^\circ + \frac{30}{\sqrt{2}}\angle 0^\circ = \frac{109.72}{\sqrt{2}}\angle -48.69^\circ$$

$$\text{Hence, } v_1(t) = 109.72 \cos(628t - 48.69^\circ)$$

$$(b) V_2 = \frac{20}{\sqrt{2}}\angle -90^\circ + \frac{10}{\sqrt{2}}\angle 60^\circ + \frac{5}{\sqrt{2}}\angle 70^\circ = \frac{9.44}{\sqrt{2}}\angle -44.71^\circ$$

$$\text{Hence, } v_2(t) = 9.44 \cos(314t - 44.71^\circ)$$

Solution Q2:

The current through the resistor and capacitor are respectively,

$$i_1(t) = \frac{v(t)}{R} = 7.071 \cos(314.16t + 10^\circ)$$

$$i_2(t) = C \frac{dv}{dt} = -12.247 \sin(314.16t + 10^\circ)$$

So, the current supplied by the source is

$$\begin{aligned} i(t) &= i_1(t) + i_2(t) \\ &= 7.071 \cos(314.16t + 10^\circ) - 12.247 \sin(314.16t + 10^\circ) \end{aligned}$$

In phasor form, this current can be written as:


$$I = 5\angle 10^\circ + 8.66\angle 100^\circ = 10\angle 70^\circ$$

The time domain expression for the current is

$$i(t) = 14.14 \cos(314.16t + 70^\circ)$$

Solution Q3:

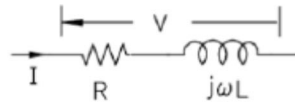Current $i(t) = 2\sqrt{2}\cos(5000t + 30^\circ) \text{ mA}$




The impedance and voltage phasors can be determined as follows:

$$I = 2 \times 10^{-3} \angle 30^\circ \text{ A}$$

$$Z = R + j\omega L = 2309 + j5000 \times 0.8 = 2309 + j4000 \Omega$$


$$V = Z I = (2309 + j4000) \times 2 \times 10^{-3} \angle 30^\circ = 9.24 \angle 90^\circ \text{ V}$$
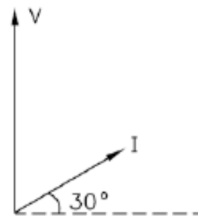
$$v(t) = 9.24 \sqrt{2} \cos(5000t + 90^\circ) \text{ V}$$



Solution Q4:

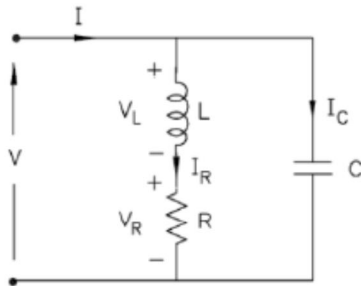$L = 2\text{H}$, $R = 3\Omega$, $C = 0.2\mu\text{F}$ and $v_R = 6\sqrt{2}\cos 2t$ volts.



As $v_R = 6\sqrt{2}\cos 2t$, we have $V_R = 6\angle 0^\circ$. Hence,

$$I_R = \frac{V_R}{R} = \frac{6\angle 0^\circ}{3} = 2\angle 0^\circ \text{ A}$$


$$V_L = j\omega L I_R = j2 \times 2 \times 2\angle 0^\circ = 8\angle 90^\circ \text{ V}$$

$$V = V_R + V_L = 6\angle 0^\circ + 8\angle 90^\circ = 6 + j8 = 10\angle 53.13^\circ \text{ V}$$

$$I_C = j\omega C V = j2 \times 0.2 \times (6 + j8) = -3.2 + j2.4 = 4\angle 143.13^\circ \text{ A}$$


$$I = I_L + I_C = 2 - 3.2 + j2.4 = -1.2 + j2.4 = 2.68\angle 116.57^\circ \text{ A}$$

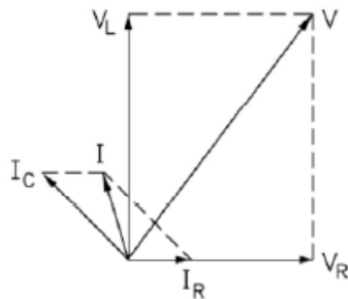The phasor diagram can be drawn as follows:



Solution Q5:

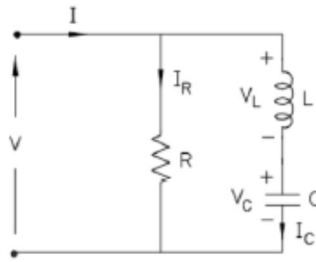$R = 2\Omega$, $L = 3.25\text{mH}$ and $C = 100\mu\text{F}$, $v_C = 100\sqrt{2}\cos(2000t - 90^\circ)$ volts



(a) As $v_C = 100\sqrt{2}\cos(2000t - 90^\circ)$ volts, we get

$$V_C = 100\angle -90^\circ$$

$$I_C = j\omega C V_C = j2000 \times 10^{-4} \times 100\angle -90^\circ = 20\angle 0^\circ \text{ A}$$

$$V_L = j\omega L I_C = j2000 \times 3.25 \times 10^{-3} \times 20\angle 0^\circ = 130\angle 90^\circ \text{ A}$$


(b) So, the voltage V across the circuit and hence currents I_R and I are

$$V = V_C + V_L = 100\angle -90^\circ + 130\angle 90^\circ = -j100 + j130 = j30 \text{ V}$$

$$I_R = \frac{V}{R} = \frac{j30}{2} = 15\angle 90^\circ \text{ A}$$


$$I = I_C + I_R = 20\angle 0^\circ + 15\angle 90^\circ = 20 + j15 = 25\angle 36.9^\circ \text{ A}$$

(c) Phasor diagram:

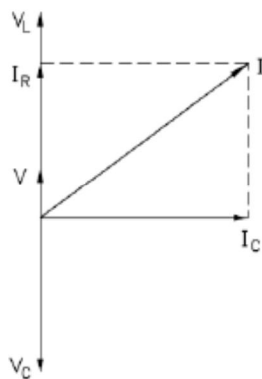

(d) $i(t) = 25\sqrt{2}\cos(2000t + 36.9^\circ) \text{ A}$

Solution Q6:

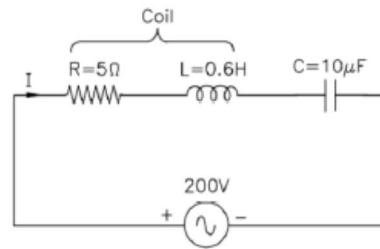

$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$I = \frac{V}{Z}$$

Current flow in the circuit will be maximum when the impedance is minimum. Hence,

$$\omega L = \frac{1}{\omega C}$$

$$\omega = \frac{1}{\sqrt{LC}} = 408.248 \text{ rad/s}$$

$$f = \frac{\omega}{2\pi} = 64.97 \text{ Hz}$$

$$I = \frac{V}{R} = \frac{200}{5} = 40 \text{ A}$$

$$|V_L| = \omega LI = 9798 \text{ V}$$

$$|V_C| = \frac{I}{\omega C} = 9798 \text{ V}$$

$$\frac{|V_L|}{|V|} = \frac{\omega LI}{RI} = \frac{\omega_o L}{R} = \frac{244.95}{5} = 48.99$$

Solution Q7.

(a)

$$P = V_{rms} I_{rms} \Rightarrow I_{rms} = \frac{120 \text{ W}}{200 \text{ V}} = 0.6 \text{ Amp}$$

(b)

$$R_{lamp} = \frac{200 \text{ V}}{0.6 \text{ A}} = 333.33 \Omega$$

(c)

With the capacitor connected in series, the total impedance is $Z = R_{lamp} - jX_c$.

When connected to 240 V source, we still want the voltage across the lamp to the rated value of 200 V, and hence 0.6A current through the lamp.

$$|Z| = \frac{240 \text{ V}}{0.6 \text{ A}} = 400 \Omega$$

$$Z = \sqrt{R_{lamp}^2 + X_c^2} \Rightarrow X_c^2 = Z^2 - R_{lamp}^2$$

$$X_c = \sqrt{400^2 - (333.33)^2} = 221.11 \Omega$$

$$X_c = \frac{1}{\omega C} \Rightarrow C = \frac{1}{\omega X_c} = \frac{1}{(2\pi \times 50)(221.11)} = 14.4 \mu\text{F}$$