

EE2029 Introduction to Electrical Energy Systems

Dr. Sahoo S.K.

elesahoo@nus.edu.sg

Learning Outcomes

Upon completion of this module, students should be able to :

- analyse ac circuits using phasor and impedance ✓
- explain active, reactive, complex power, and power factor – its impact on losses and need for power factor correction. ✓
- examine power in single-phase and three-phase balanced systems.
- model key components of power systems including generator, transmission line, transformer and induction motor load.
- analyse the working of a complete power system from generation to load.

Syllabus

1. Review of AC circuit analysis (3 hours)
 - Use of phasor and impedance in AC circuit analysis.
2. Structure of Electrical Power Systems (3 hours)
 - Introduction to power generation, transmission and distribution systems.
3. Three-Phase systems (6 hours)
 - Revise active power, reactive power and apparent power. Concept of harmonics and how it influences power factor. Introduction to phasor diagrams and complex power. Balanced three-phase systems and their single-phase equivalents. Power factor correction. Relationship between phase and line quantities Concept of regulation.
4. Generating sources (3 hours)

Gas Turbine: basic energy conversion model, IEC symbol, and conversion efficiencies, and concept of rotating prime mover applied to other similar sources. Photovoltaic array: basic model, and conversion efficiencies.

Syllabus

4. Transmission System (6 hours)

Three-phase-four-wire system, three-phase-three-wire system, and three-phase circuit analysis. Modelling and sizing of cables. Circuit breaker and its sizing. Grounding and earth followed by safety and earthing.

5. Transformers (6 hours)

Ideal transformer, Magnetic circuits, magnetizing current and saturation, real transformers. Equivalent circuits with short-circuit and open circuit. Phasor diagram, regulation (applied to transformer) and efficiency. Three-phase transformer connections, including with wye and delta connections.



6. Loads (6 hours)

Static loads: Lighting, heating, resistive, and inductive. Three-phase induction machine: Operating principle, equivalent circuits, torque-speed characteristics, losses and efficiency.

Schedule for EE2029 (First half) in Sem 1 AY2021/22

Week	Date	Time	Lecture	Topic
1	10 Aug 2021	16:00- 18:00	Lec1	Topic 1 AC Fundamentals
	13 Aug 2021	12:00-14:00	Tutorial 1	Tutorial 1 AC Fundamentals
2	17 Aug 2021	16:00- 18:00	Lec2	Topic 2 AC Power
	20 Aug 2021	12:00-14:00	Tutorial 2	Tutorial 2 AC Power
3	24 Aug 2021	16:00- 18:00	Lec3	Topic 3 Three phase analysis
	27 Aug 2021	12:00-14:00	Tutorial 3	Tutorial 3 Three phase analysis
4	31 Aug 2021	16:00- 18:00	Lec4	Topic 4 Generation
	3 Sep 2021	12:00-14:00	Tutorial 4	Tutorial 4 – Generation
5	7 Sep 2021	16:00- 18:00	Lec5	Topic 5 Renewable generation
	10 Sep 2021	12:00-14:00	Tutorial 5	Tutorial 5 – Renewable generation
6	14 Sep 2021	16:00- 18:00	Summary	Doubt clearing
	17 Sep 2021	12:00-14:00		Midterm Quiz 1

Modelling of complete power system

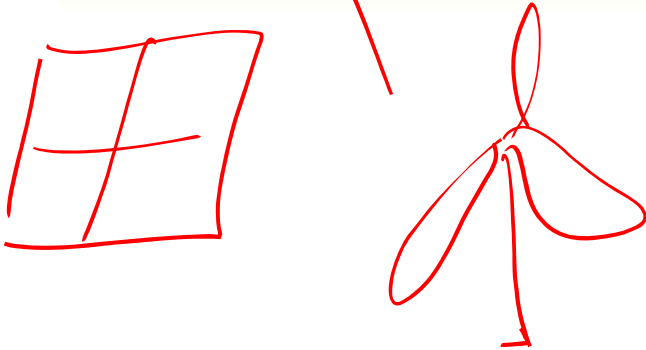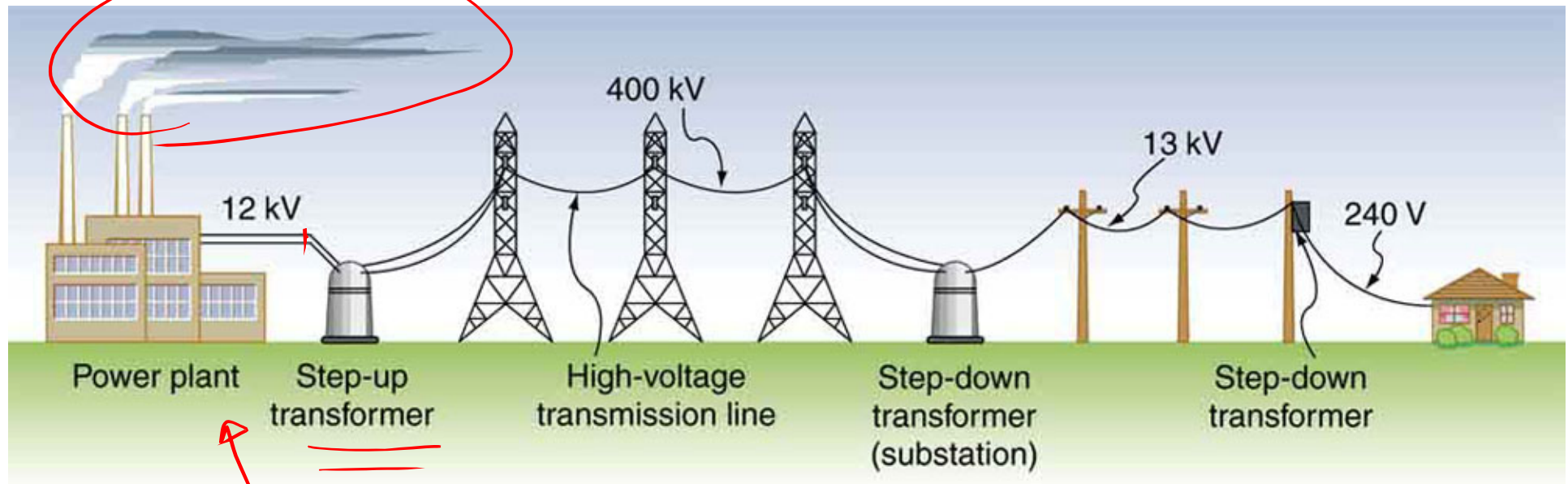

Key concepts and formula in AC fundamentals

time domain

- $V_m \sin(\omega t + \theta) \rightarrow \frac{V_m}{\sqrt{2}} \angle \theta$

*Complex domain
Phasors*


- $R \rightarrow Z_R = R$

- $L \rightarrow Z_L = j\omega L$ ✓


- $C \rightarrow Z_C = \frac{1}{j\omega C} = -j \frac{1}{\omega C}$ ✓

Impedance

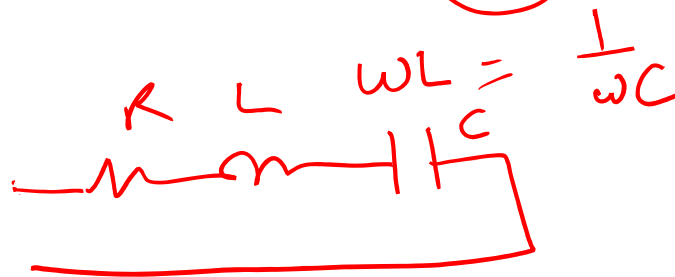- Resonance frequency $\omega_0 = \frac{1}{\sqrt{LC}} \frac{\text{rad}}{\text{sec}}; f_0 = \frac{\omega_0}{2\pi} \text{ Hz}$



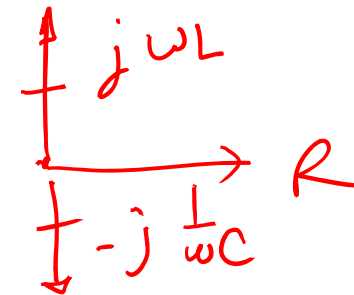$\omega = 2\pi f$ if $f = 50 \text{ Hz}$
angular frequency (rad/sec).




Key concepts and formula in AC power

- Average power (real power) in resistor R $\rightarrow P_{avg} = V_{rms} I_{rms} = I_{rms}^2 R = \frac{V_{rms}^2}{R}$
- Average power (real power) in inductor L $\rightarrow P_{avg} = 0$
- Average power (real power) in capacitor C $\rightarrow P_{avg} = 0$
- Power in general AC load $Z = R + jX \rightarrow P = VI \cos \theta, Q = VI \sin \theta$
 - where V, I are RMS values for voltage and current; θ is the impedance angle

$L: I = \frac{V}{Z} = \frac{V}{j\omega L} = -j(\quad)$


$$\theta = \tan^{-1} \left(\frac{X}{R} \right)$$

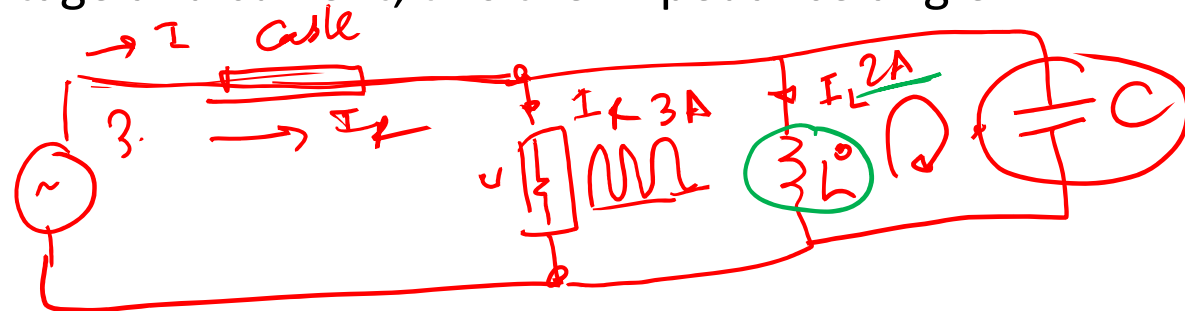$I = I_L + I_R$
 $= 3 - j2$
 $= \sqrt{13} \angle -36.9^\circ$



Key concepts and formula

- Complex power $S = VI^* = P + jQ$,
 - where V is voltage phasor, I^* is conjugate of current phasor
- Apparent power $|S| = VI$ in VA
- Real power $P = \text{Real part of } (S)$ in Watt
- Reactive power $Q = \text{Imaginary part of } (S)$ in VAr

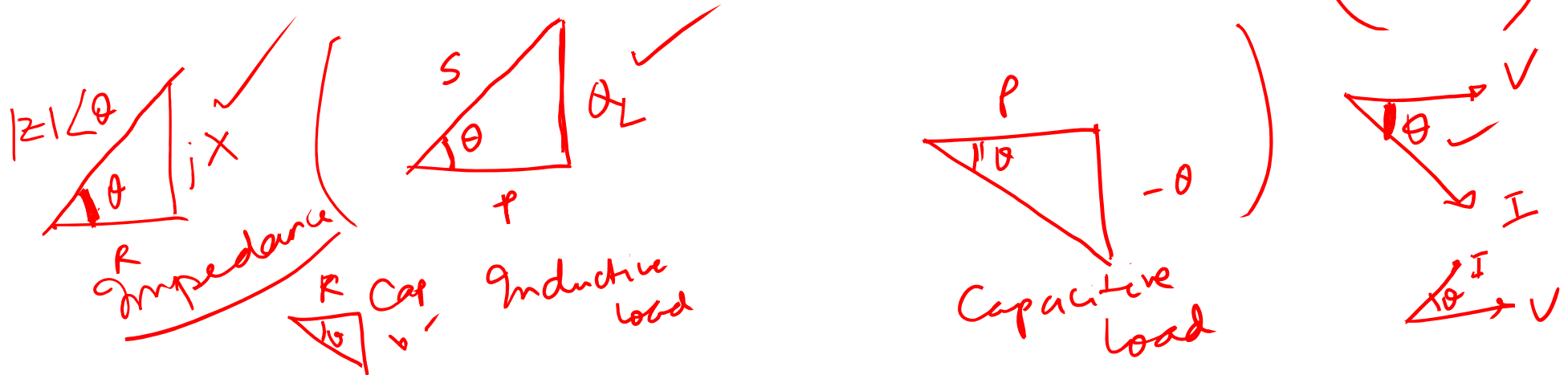

Key concepts and formula

- Power Factor = $\frac{\text{Real power}}{\text{Apparent power}} = \frac{P}{|V||I|} = \cos(\theta)$
 - Where θ is the impedance angle, it is the phase difference between voltage and current phasors
- Power factor is lagging for inductive load
- Power factor is leading for capacitive load
- Low power factor leads to increased current for the same power
 - Leads to increased loss
- Capacitor can be connected across inductive load to improve power factor


Assume V is ref

$$I = \frac{P}{|V| \times \text{p.f.}} \angle -\cos^{-1}(0.8)$$

1-phase AC load consumes
 P. 2000W at 0.8 lagging
power factor at 230V.
 p.f.

$$I = \frac{2500}{230} \angle +\cos^{-1} 0.8$$

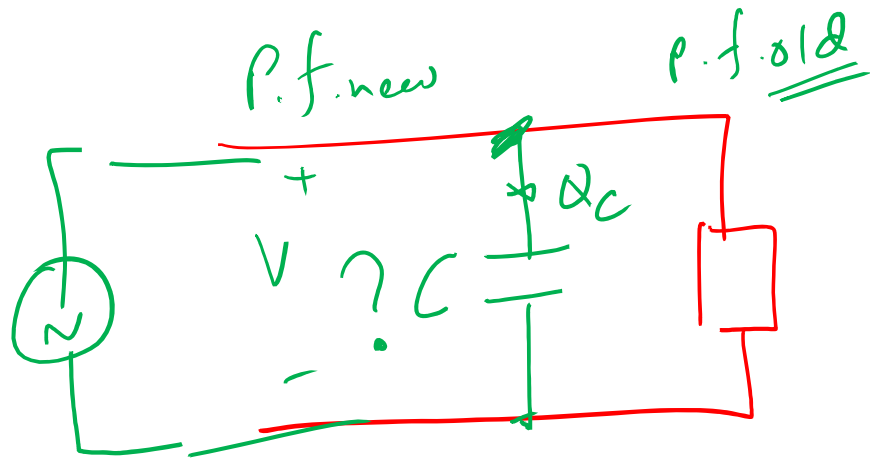1 ph AC load draws
 151 2500 VA, 0.8 leading
 p.f. at 230V.



If $P.f._{new} = 1,$
 $Q_{new} = 0$
 $Q_c = - Q_{old}$

Old : P.f. and the load

New P.f.

Q_{old} from the load

$$S_{old} = P_{old} + j Q_{old}$$

$$S_{new} = P_{old} + j Q_{new}$$

$$Q_{new} = Q_{old} + Q_c$$

$$Q_c = - V^2 \omega C \rightarrow C$$


Key concepts and formula in Three-phase

- Balanced three-phase supply with 'abc' (positive) phase sequence

- $v_a(t) = V_m \sin(\omega t), v_b(t) = V_m \sin(\omega t - 120^\circ), v_c(t) = V_m \sin(\omega t + 120^\circ)$

- Balanced three-phase supply with 'acb' (negative) phase sequence

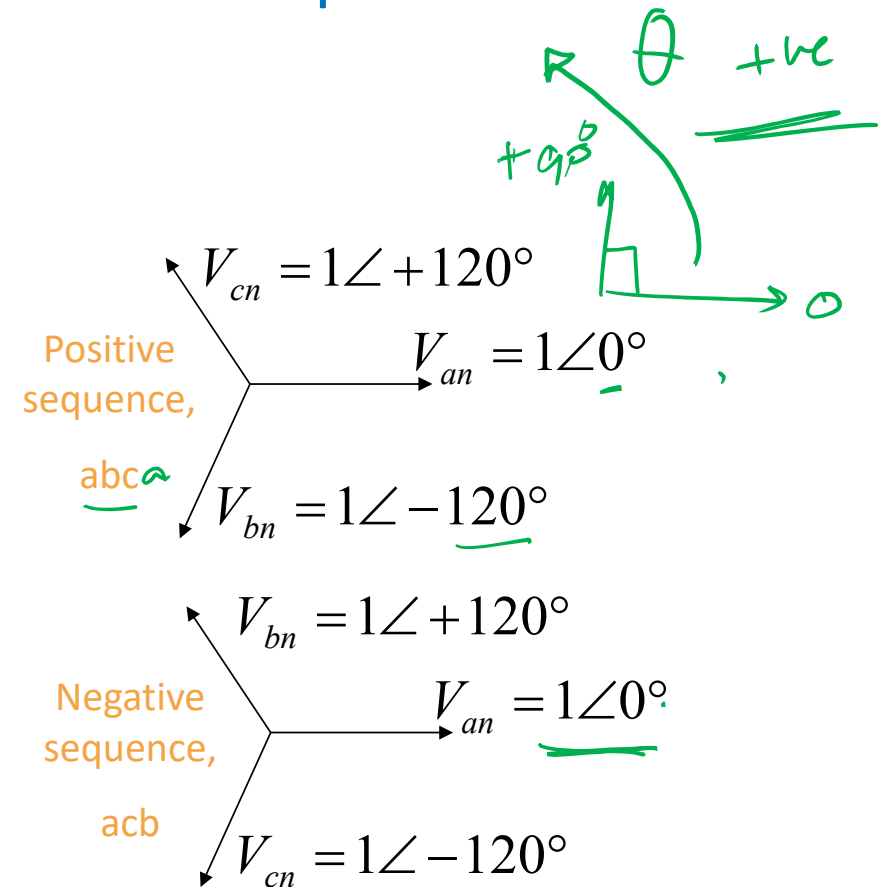
- $v_a(t) = V_m \sin(\omega t), v_c(t) = V_m \sin(\omega t - 120^\circ), v_b(t) = V_m \sin(\omega t + 120^\circ)$



Key concepts and formula



- In a balanced three phase system
 - $V_a + V_b + V_c = 0$
 - $I_a + I_b + I_c = 0$
- For positive sequence system
 - $V_{ab} = \sqrt{3}V_{an} \angle 30^\circ$

$$|V_{\text{Line-Line}}| = \sqrt{3} |V_{\text{Line-neutral}}|$$

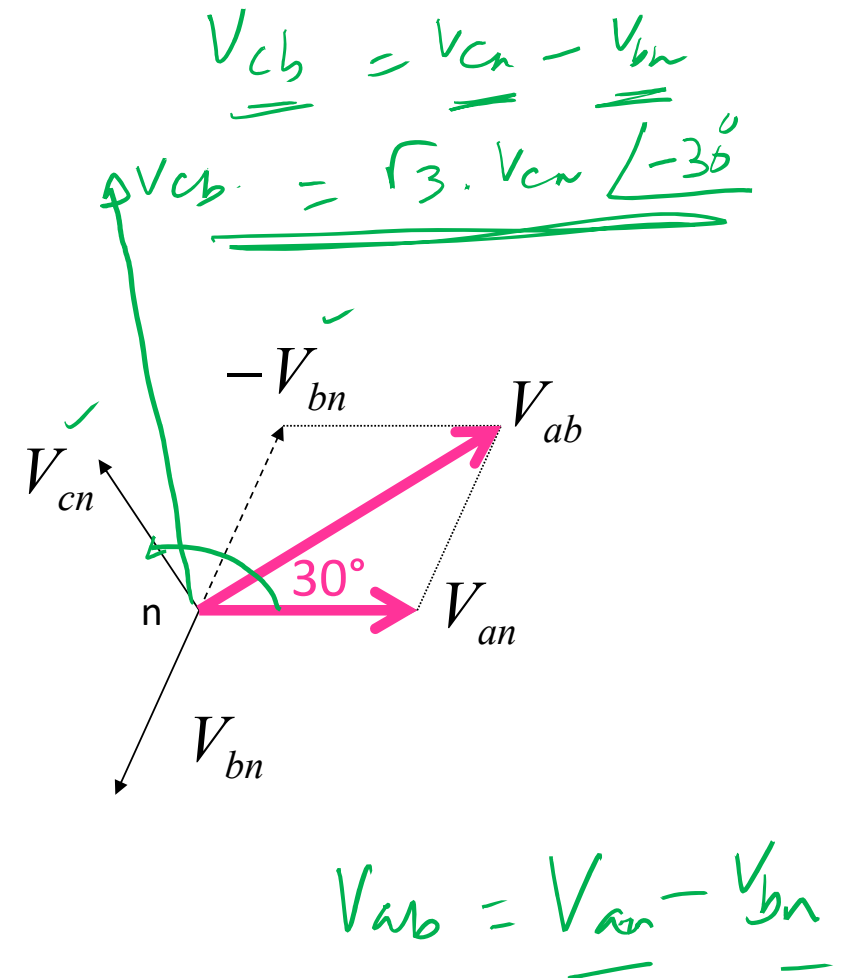

Key concepts and formula

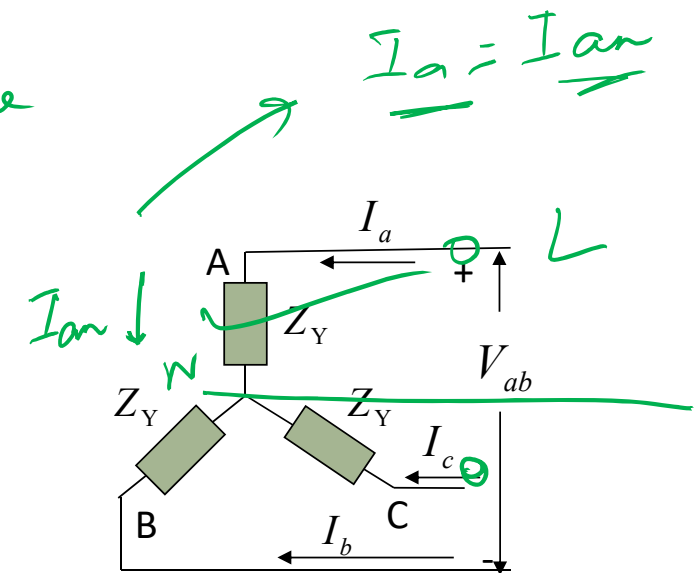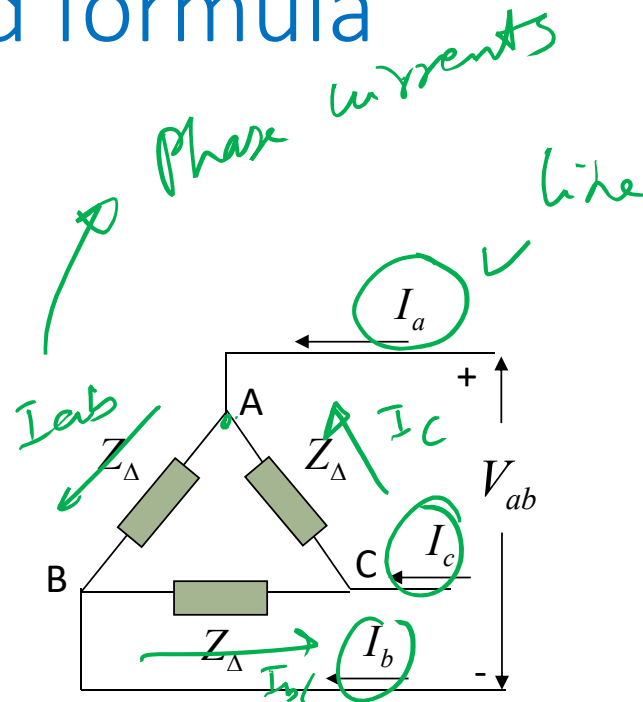- Balanced three phase load can be connected as Wye or Delta
- We can convert a Wye connected to equivalent Delta connected load
 - $Z_{\Delta} = 3 Z_Y$
- We can convert a Delta connected to equivalent Wye connected load
 - $Z_Y = \frac{Z_{\Delta}}{3}$



Key concepts and formula

$\sqrt{3}$, V , I

- Balanced three-phase power $s_{3\phi} = 3V_{an}I_{an}^* = \sqrt{3}V_{\text{line-to-line}}I_{\text{line}}$
- Balanced three-phase power transfer to load constant

Ask me anything

- Consultation session before midterm

