

#### EE2029: Introduction to Electrical Energy System

# Per Unit Analysis: Three Phase Transformers

Lecturer : Dr. Sangit Sasidhar (elesang)

Department of Electrical and Computer Engineering

© Copyright National University of Singapore. All Rights Reserved.



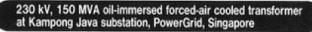
## Three-Phase Transformers



Three-phase transformers at substations

Pole-mounted three single-phase transformers.






Source: http://www.meidensg.com.sg






# Three-Phase Transformer Nameplate

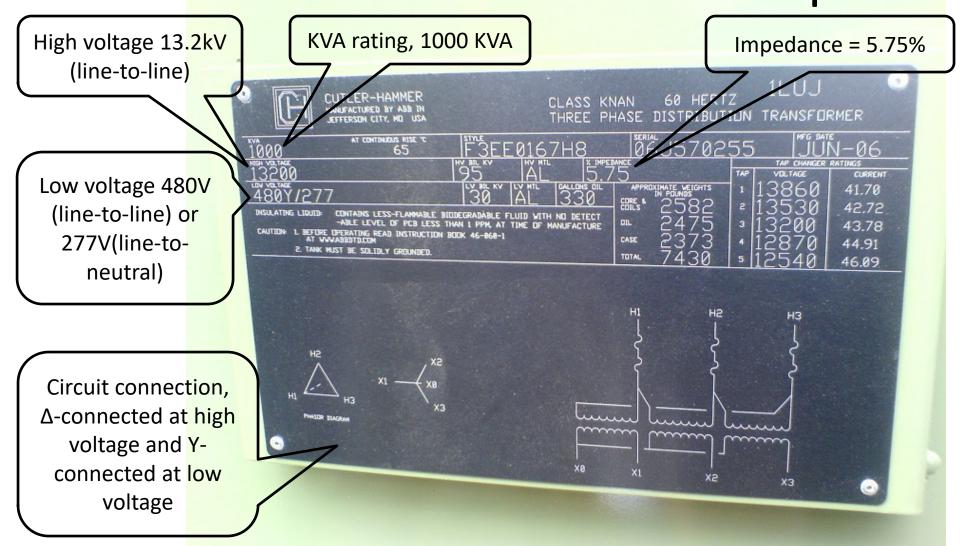



# Three Single-Phase Transformers

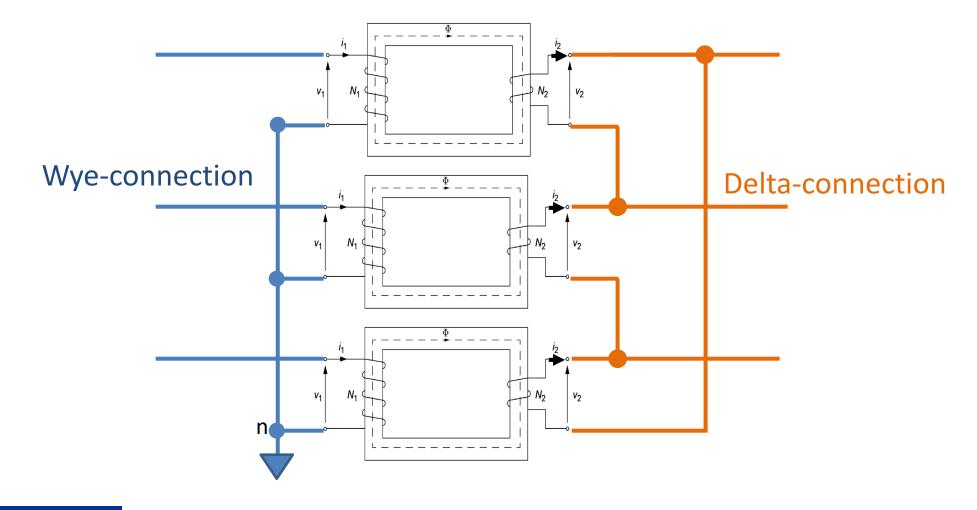



#### **3Ф Transformer Connections**


designation	winding connection	single-phase equivalent
Yy		$ V_{LN} $
Yd	VLN VIN VIN VIN VIN VIN VIN VIN VIN VIN VI	$ V_{LN} $ $ V_{ln} $
Dy	· VLN EMIVIN	$ V_{LN} $
Dd	V <sub>LN</sub>    V <sub>In</sub>	$ V_{LN} $


- The voltage rating of a three phase transformer is the ratio between **line-to-line** voltage at the primary side and **line-to-line** voltage at the secondary side.
- The single-phase equivalent shows line-to-neutral voltage.
- For Y-Y and  $\Delta$ - $\Delta$  transformers, voltage and current in both primary and secondary are in phase. The ratio of the voltage and current follows the turn ratio of the transformer.
- The same does not apply to Y- $\Delta$  and  $\Delta$ -Y connections.




#### **3Ф Transformer Connections**


designation	winding connection	single-phase equivalent
Yy		
Yd	VLN VIN VIN	$ V_{LN} $
Dy	$\frac{1}{2}  V_{LN}  = \frac{1}{2}  V_{In} $	
Dd	V <sub>LN</sub>  V <sub>In</sub>	

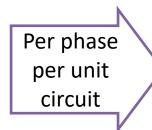

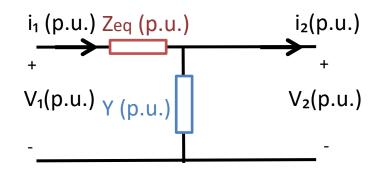

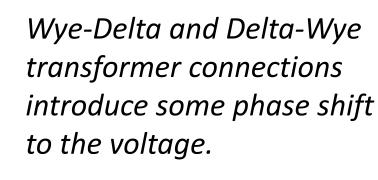

Per phase per unit circuit

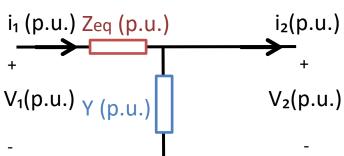





# Wye-Delta 3Ф Transformers

#### Wye-connected

#### **Delta-connected**

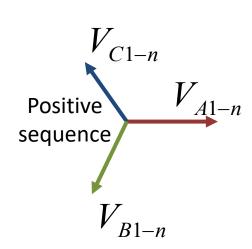

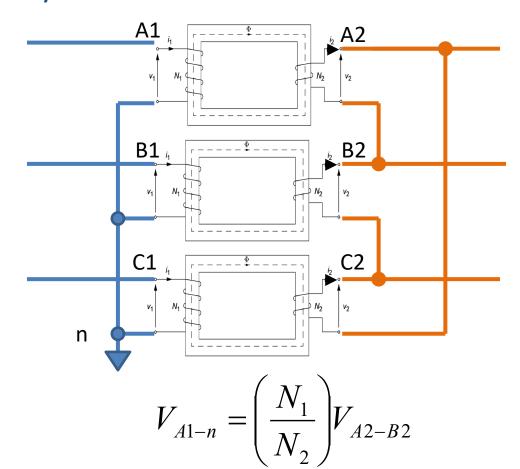


 $V_{A2-B2}$ 

Line-to-neutral voltage

**Line-to-line** voltage!!



# Wye-Delta 3Ф Transformer

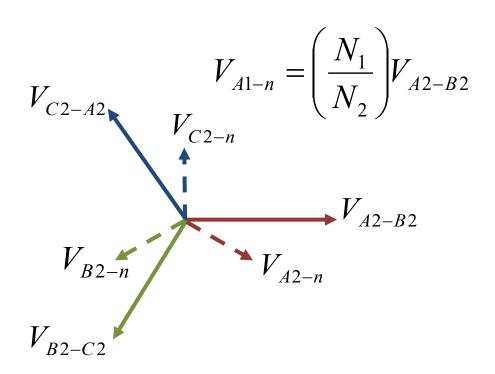




## Y-Δ 3Φ Transformer: Per Phase Model

For a positive sequence voltage source,

$$V_{A1-n} = \left(\frac{N_1}{N_2}\right)\sqrt{3}V_{A2-n} \angle 30^{\circ}$$
  $\angle V_{A1-n} : \angle V_{A2-n} = 1\angle 30^{\circ} : 1$ 


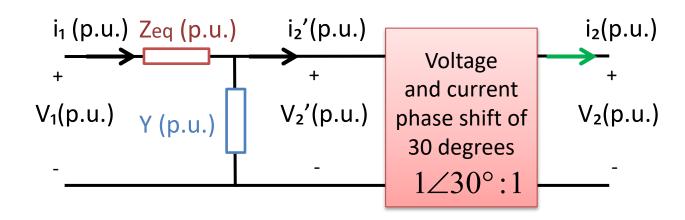
$$\angle V_{A1-n}: \angle V_{A2-n} = 1\angle 30^{\circ}: 1$$




$$i_2 = i_2' \angle -30^{\circ}$$


$$V_2 = V_2' \angle -30^{\circ}$$



## 3Ф Transformer Per Unit Model

designation	winding connection
Yy	
Yd	V <sub>LN</sub> V <sub>In</sub> V <sub>In</sub>
Dy	· VLN EM  VIN
Dd	V <sub>LN</sub>    V <sub>In</sub>

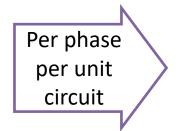

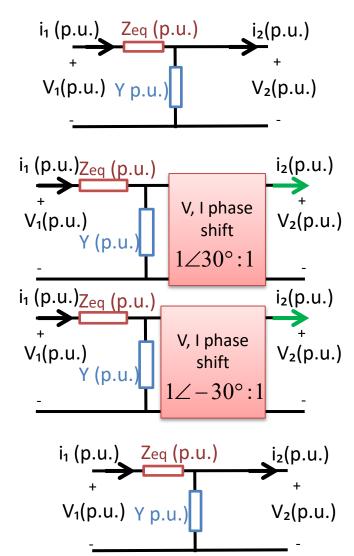



# Summary